



**B.E. DEGREE EXAMINATIONS: NOV/DEC 2022**

(Regulation 2018)

Third Semester

**AERONAUTICAL ENGINEERING**

**U18EEI3202: Aircraft Electrical and Electronics Systems**

**COURSE OUTCOMES**


- CO1:** Discuss the fundamentals of DC circuits and its applications in aircraft systems.
- CO2:** Explain the relationships among current, voltage and power in AC circuits and their role in aircraft systems.
- CO3:** Explain the construction, working principle of electrical machines and their applications in aircraft systems.
- CO4:** Explain the working of semiconductor devices and their role in aircraft systems.
- CO5:** Apply the fundamentals of digital electronics to digital circuits.

**Time: Three Hours**

**Maximum Marks: 100**

**Answer all the Questions:-**  
**PART A (10 x 2 = 20 Marks)**  
**(Answer not more than 40 words)**

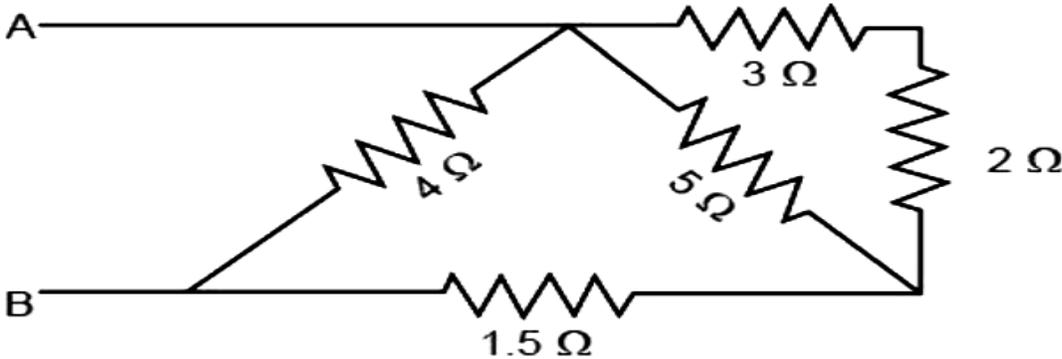
- 1. Differentiate Linear elements and nonlinear elements. CO1 [K<sub>2</sub>]
- 2. What is the equivalent resistance between A and B? CO1 [K<sub>3</sub>]



- 3. Define form factor in AC circuit and mention the value of form factor for sine wave. CO2 [K<sub>1</sub>]
- 4. Draw Power triangle of AC circuit? CO2 [K<sub>2</sub>]
- 5. Why is aircraft electrical system important? CO3 [K<sub>2</sub>]
- 6. How the generator control system works on aircraft electrical systems? CO3 [K<sub>2</sub>]
- 7. Mention the application of BJT in aircraft system. CO4 [K<sub>3</sub>]
- 8. State the disadvantages of Half wave rectifiers. CO4 [K<sub>2</sub>]

9. Write the logical expression for the given circuit shown in figure.1

CO5 [K<sub>2</sub>]

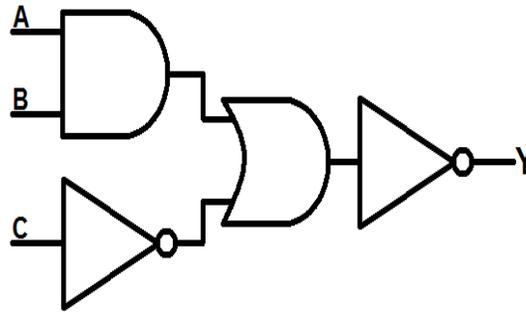

10. Mention the function of multiplexer?

CO5 [K<sub>2</sub>]

**Answer any FIVE Questions:-**

**PART B (5 x 16 = 80 Marks)**

**(Answer not more than 400 words)**

11. a) (i) Explain the Kirchoff's laws with example.

6 CO1 [K<sub>2</sub>]

(ii). Determine the equivalent resistance between points A and B.

4

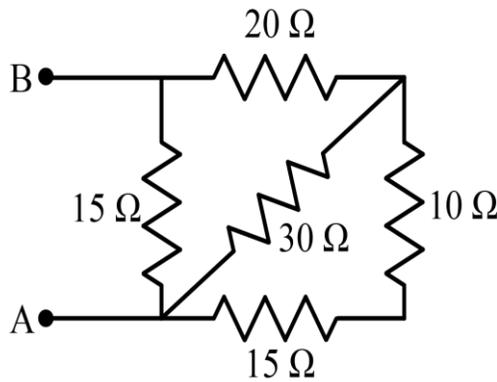


Figure 2

b) Using Kirchoff's laws of current and voltage, find the current in 2 Ω resistor in the given circuit.

6 CO1 [K<sub>2</sub>]

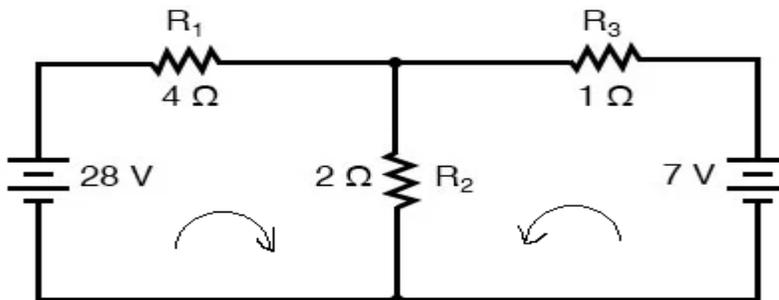


Figure 3

12. a) Find the average value, rms value and formfactor of the given figure. 10 CO2 [K<sub>3</sub>]

From figure:

$$V(t) = 4 * t \quad 0 \leq t \leq 1$$

$$= 4 - 4(t - 1) \quad 1 \leq t \leq 2$$

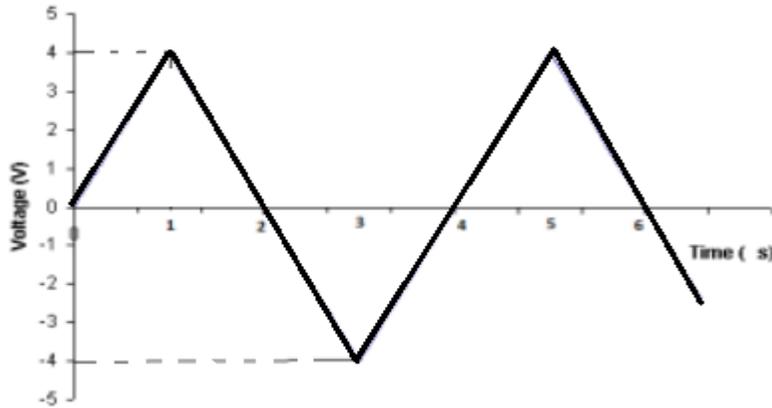


Figure 4

- b) Explain about the alternating current through the pure capacitor circuit and draw its waveforms and vector diagram. 6 CO2 [K<sub>3</sub>]
13. a) Describe the construction of DC machine with neat diagram. 10 CO3 [K<sub>2</sub>]
- b) Explain the construction and principle of operation of single-phase transformer. 6 CO3 [K<sub>2</sub>]
14. a) Explain the working of PN junction diode and draw its V-I characteristics. 8 CO4 [K<sub>2</sub>]
- b) Discuss about the operation of Full wave rectifier with waveforms. 8 CO4 [K<sub>2</sub>]
15. a) Explain the full adder circuits with truth table and logic diagram. 8 CO5 [K<sub>2</sub>]
- b) Describe about working of 1 to 4 multiplexer with block diagram and truth table. 8 CO5 [K<sub>2</sub>]
16. a) Explain the Construction of an alternator with neat diagram. 8 CO3 [K<sub>2</sub>]
- b) Derive an expression for average and RMS value of sine wave voltage. 8 CO4 [K<sub>2</sub>]

\*\*\*\*\*