



B.TECH. DEGREE EXAMINATIONS: NOV/DEC 2022

(Regulation 2018)

Third Semester

FASHION TECHNOLOGY

U18EEI3206: Basic Electrical and Electronics Engineering

COURSE OUTCOMES

- CO1:** Acquire basic knowledge on DC and AC circuits.
CO2: Understand the construction, working principle and applications of DC machines
CO3: Understand the construction, working principle and applications of AC machines and transformers.
CO4: Acquire basic knowledge on logic gates, semiconductor devices and their applications.
CO5: Identify electronic components and use them to design simple circuits.

Time: Three Hours

Maximum Marks: 100

**Answer all the Questions:-
PART A (10 x 2 = 20 Marks)
(Answer not more than 40 words)**

- | | | |
|---|-----|-------------------|
| 1. Define current and resistance. | CO1 | [K ₁] |
| 2. State Ohm's law and mention its limitations. | CO1 | [K ₁] |
| 3. Define frequency and time period. | CO2 | [K ₁] |
| 4. Specify the range of power factor. | CO2 | [K ₂] |
| 5. State Faraday's laws of electromagnetic induction. | CO3 | [K ₂] |
| 6. List few applications of single phase induction motor. | CO3 | [K ₂] |
| 7. Define knee voltage. | CO4 | [K ₂] |
| 8. Sketch the symbol of NPN transistor and mark the current directions. | CO4 | [K ₂] |
| 9. Convert (2234) ₁₀ to its binary | CO5 | [K ₃] |
| 10. Differentiate de-multiplexer and decoder. | CO5 | [K ₂] |

**Answer any FIVE Questions:-
PART B (5 x 16 = 80 Marks)
(Answer not more than 400 words)**

- | | | | |
|--|----|-----|-------------------|
| 11. a) Compare series and parallel circuits. | 06 | CO1 | [K ₃] |
| b) Obtain the current in each branch of the network shown in figure.1 using mesh current method. | 10 | CO1 | [K ₄] |

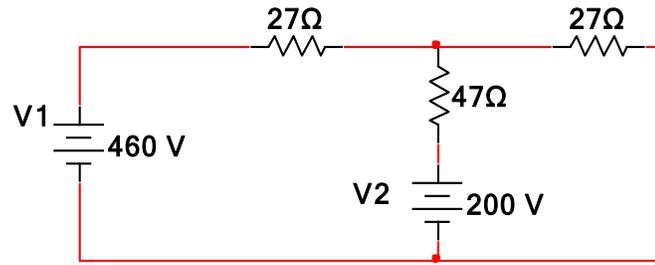


Figure 1

- | | | | | | |
|-----|----|--|----|-----|-------------------|
| 12. | a) | Derive the expression for impedance, power factor and current of a RL series circuit supplied with single phase AC voltage source. Also draw the phasor diagram. | 08 | CO2 | [K ₂] |
| | b) | A resistance of 120 Ω and a capacitive reactance of 250 Ω are connected in series across a A.C voltage source. If a current of 0.9 A is flowing in the circuit, find out (i) Power factor, (ii) Supply voltage (iii) Voltages across resistance and capacitance. | 08 | CO2 | [K ₃] |
| 13. | a) | Describe the working of DC generator with relevant diagram. | 08 | CO3 | [K ₂] |
| | b) | Explain the constructional details of a three phase induction motor with relevant diagrams. | 08 | CO3 | [K ₂] |
| 14. | a) | With neat circuit and waveform, explain how an alternating voltage is rectified using half-wave rectifier. | 08 | CO4 | [K ₃] |
| | b) | Sketch and explain the drain characteristics of N channel JFET. | 08 | CO4 | [K ₂] |
| 15. | a) | Design a full subtractor using logic gates. | 08 | CO5 | [K ₆] |
| | b) | Draw the logic diagram of JK flip flop and explain its operation through its characteristic table and equation. | 08 | CO5 | [K ₂] |
| 16. | a) | Design and implement 4 to 1 multiplexer using appropriate gate circuits. | 08 | CO5 | [K ₆] |
| | b) | Show how a Zener diode can be used to regulate the output voltage. | 08 | CO4 | [K ₃] |
