

**M.E. DEGREE EXAMINATIONS: MAY / JUNE 2010**

Second Semester

**APPLIED ELECTRONICS**

ANE504: Analysis and Design of Analog Integrated Circuits

**Time: Three Hours**

**Maximum Marks: 100**

**Answer All the Questions:-**

**PART A (10 x 2 = 20 Marks)**

1. What is tunneling?
2. Define emitter injection efficiency.
3. Draw the schematic of a simple bipolar current mirror.
4. What is bootstrap? Where it is used?
5. Define Common-Mode Rejection Ratio.
6. What is superbeta transistor?
7. What are the advantages of MOS technology?
8. What is a telescopic-cascode operational amplifier? Mention any one advantage of the same.
9. Define Lock range and Capture range of a PLL.
10. Define noise spectral density.

**PART B (5 x 16 = 80 Marks)**

11. (a) (i) Derive an expression for the depletion region of a P-N junction. (8)  
(ii) An abrupt PN junction in silicon has doping densities  $N_A = 10^{15}$  atoms/cm<sup>3</sup> and  $N_D = 10^{16}$  atoms/cm<sup>3</sup>. Calculate the junction built-in potential, the depletion-layer depths and the maximum field with 10V reverse bias. (8)

**(OR)**

- (b) (i) Derive the general form of Ebers-Moll equations for a npn transistor. (8)  
(ii) Explain the short-channel effects in MOS transistors. (8)

12. (a) (i) With Schematic, explain the Bipolar Cascode current mirror and its I-V characteristics. (12)  
(ii) Find the output resistance of the double-cascode current mirror. Assume all the transistors operate in the active region with  $I_D = 10\mu\text{A}$ ,  $V_A = 50\text{V}$  and  $g_m r_o = 50$   
(Neglect body effect) (4)

(OR)

- (b) Explain in detail Wilson Current mirror and derive an expression for its output resistance  $R_o$ .

13. (a) Explain in detail the most important deviations from ideality in practical operational amplifiers and their effects in applications.

(OR)

- (b) Discuss in detail the dc analysis of 741 operational amplifiers.

14. (a) (i) With schematic explain the Widlar current source. (8)

- (ii) Explain the MOS folded Cascode operational amplifier and its advantages. (8)

(OR)

- (b) (i) Explain the basic two-stage MOS operational Amplifiers. (8)

- (ii) With schematic explain the MOS high-swing current mirror. (8)

15. (a) With DC analysis, explain the use of Gilbert Cell as an analog Multiplier. Also derive a complete four-quadrant multiplier and explain its characteristics.

(OR)

- (b) With block diagram explain the operation of a PLL and derive the closed loop transfer function for the first order loop.

\*\*\*\*\*