

Register Number (_____)

B.E DEGREE EXAMINATIONS Nov / Dec 2009

III SEMESTER

BRANCH MCE

U07MH303 & Digital Electronics

Time : Three Hours

Maximum Marks : 100

**Answer ALL Questions: -
PART A (10 X 1 = 10 Marks)**

1. A K-map of five Variable will have _____ cells.
a) 64 b) 28 c) 32 d) 31
2. Gray code is _____ code.
a) Weighted code b) Non Weighted code c) Reflective d) Sequential
3. A decoder with 64 output line has _____ select lines.
a) 5 b) 6 c) 4 d) 8
4. In a 4 bit parallel adder each full adder is considered to have a propagation delay of 30 ns then S_3 (MSB) will reach _____ time.
a) 120 ns b) 120 ps c) 120 & d) 120ms.
5. Refresh circuit require for _____ RAM
a) Dynamic b) Static c) Volatile d) Non-Volatile
6. In which flip-flop race around condition will take place?
a) SR b) D c) T d) JK.
7. Hazard may occur in _____ circuits
a) Synchronous Sequential b) Asynchronous sequential c) Combinational Circuit
d) Transistor Circuit
8. A _____ occurs when an asynchronous circuit makes a transition through a series of unstable states.
a) Non-critical race b) Critical race c) Cycles d) Races
9. The programmable array logic has programmable _____ gates and fixed _____ gates.
a) NAND, NOR b) OR,AND c) AND, OR d) NOR,NAND
10. The output of the moor model is a function of
a) Both the present state & input b) Only present state
c) Both the next state & input d) Only next state

**Answer ALL Questions: -
PART B (10 X 2 = 20 Marks)**

11. Define redundancy theorem
12. What are the drawbacks of K-map method?
13. Implement the logic function $f = AB + \overline{A} \overline{B}$ using a suitable multiplexer.
14. What is meant by an “Essential-Prime-Implicant”?
15. Derive the characteristics of a D-flip flop.
16. What is a binary counter?
17. What is meant by critical race?
18. What are static 1 and static 0 hazards?
19. Define ASM chart ?
20. Draw the block diagram of meely and moore model of FSM.

PART C (5 X 14 = 70 Marks) (One Question from each unit)


21. a) (i) Simplify the boolean function $F(A,B,C,D) = \Sigma m(1,3,7,11,15) + \Sigma d(0,2,5)$. If don't care conditions are not taken care, what is the simplified boolean function? What are your comments on it? Implement both circuits.
ii) Implement $Y = (A+C)(A+D)(A+B+C)$ using NOR gates only.
(OR)
- b) What is the advantage of using tabulation method? Determine the prime implicants of the following function using tabulation method.
 $F(w,x,y,z) = \Sigma(1,4,6,7,8,9,10,11,15)$.
- 22 a) i) Implement the following function using with a (8:1) multiplexer.
 $F(a,b,c,d) = \Sigma(0,1,5,7,10,14,15)$ (8)
ii) Design a full Subtractor. (6)
(OR)
- b). Design a network to convert 8421 BCD code to EX-3 code. (14)
23. a) i) Draw and explain 4-bit parallel in serial out shift register. (8)
ii) Design and explain the working of a synchronous mod-3 counter. (6)
(OR)
- b). Design a synchronous counter for $4 \rightarrow 6 \rightarrow 7 \rightarrow 3 \rightarrow 1 \rightarrow 4 \dots$ avoid lockout condition. Use JK type design. (14)
- 24 a) Find a static and dynamic hazard free realization for the following function using NAND gates and NOR gates.
 $F(a,b,c,d) = \Sigma m(1,5,7,14,15)$
(OR)
- b) Develop the state diagram and primitive flow table for a logic system that has 2

inputs, x and y and output z and reduce primitive flow table. The behaviour of the circuit is stated as follows. Initially $x=y=0$. whenever $x=1$ and $y=0$ then $z=1$, whenever $x=0$ and $y=1$ then $z=0$. When $x=y=0$ or $x=y=1$ no change in z it remaind in the previous state. The logic system hqas edge triggered inputs without having a clock. The logic system changes state on the rising edge of the inputs. Static input values are not to have any effect in changing the z output.

- 25 a) Draw the ASMD charts for the following state transitions:
- If $x=1$, control goes from state s1 to state s2: if $x=0$, generate a conditional operation $R \leq R+2$ and go from s1+s2.
 - If $x=1$, control goes from s1 to s2 and then to s3; if $x=0$, R is cleared to zero and controlled goes from s1 to s3.
 - State from state s1; then if $xy=00$,go to s2; if $xy=10$, go to s3; and if $xy=01$, go to s1; otherwise, go to s3.

(OR)

 - b) Design the control circuit of the binary multiplier specified by the state diagram of the fig shown below, using multiplexers, a decoder, and a register.



State Transition		Register Operation
From	To	
S_idle		Initial State
S_idle	S_add	$A \leftarrow 0, c \leftarrow 0, p \leftarrow dp_width$
S_add	S_shift	$P \leftarrow p-1$
S_shift		If($q[0]$)then ($A \leftarrow A+B, C \leftarrow C_{out}$)
		Shift right {CAQ}, $C \leftarrow 0$.