

**B.E. / B. TECH. DEGREE EXAMINATIONS: APRIL/MAY 2009**

Third Semester

**U07CS305 DIGITAL PRINCIPLES AND SYSTEM DESIGN**(Common to B.E. Computer Science and Engineering and  
B. Tech. Information Technology Branches)

Time: Three Hours

Maximum Marks: 100

Answer ALL the Questions:-

**PART A (20 x 1= 20 Marks)**

1.  $x+x' =$ 
  - a. 0
  - b. 1
  - c. x
  - d.  $x'$
2.  $(x+y)(x+y') =$ 
  - a.  $x+y$
  - b. xy
  - c. 0
  - d. 1
3. The algebraic function for NAND gate is
  - a.  $F=(x+y)'$
  - b.  $F=(x'+y')$
  - c.  $F=xy$
  - d.  $F=(xy)'$
4. n variable can be combined to form \_\_\_\_\_ minterms
  - a. 2n
  - b. n+2
  - c.  $2^n$
  - d. n
5. Fanout is
  - a. Maximum Number of load that can be connected in the input
  - b. Maximum Number of load that can be connected in the output
  - c. Minimum Number of load that can be connected in the input
  - d. Minimum Number of load that can be connected in the output
6. Schottky Transistor has
  - a. A schottky diode between base and collector
  - b. A schottky diode between collector and Emitter
  - c. A schottky diode between base and emitter
  - d. A schottky diode between base and emitter in reverse bias
7. Emitter coupled logic is
  - a. non saturated digital logic family
  - b. saturated digital logic family
  - c. saturated register logic family
  - d. non saturated diode logic family
8. Field effect transistor is a
  - a. Uni-polar Transistor
  - b. Bipolar transistor
  - c. Tri-polar Transistor
  - d. Uni-polar Diode
9. Half adder adds
  - a. Carry bit
  - b. 2bits
  - c. 3 bits
  - d. 2 bits + carry bit

10. Decoder is
- N input to  $2^n$  output
  - N input to  $2^n$  output
  - $2^n$  input to  $2^n$  output
  - $2^n$  input to n output
11. High impedance state behaves like a
- Open Circuit
  - Closed Circuit
  - Logical High
  - Logical Low
12. The number of output from a 4 bit carry look ahead adder is
- $S_1S_2S_3S_4+C$
  - $S_1S_2S_3+C$
  - $S_1S_2S_3S_4S_5+C$
  - $S_1S_2S_3S_4$
13. Sequential Circuit is a combination of
- Combination Circuit + Sequential Elements
  - Combination Circuit + memory Elements
  - Digital circuit + sequential Elements
  - Digital Circuit + Combination Elements
14. A flip flop can maintain its state
- Indefinitely
  - For 5 seconds
  - For 10 Seconds
  - Will not maintain
15. Every Flip flop in a register can store up to
- 8 bits
  - 4 bits
  - 2 bits
  - 1 bit
16. A decimal counter follows a sequence of
- 0 to A
  - 0 to 9
  - 0 to 7
  - 0 & 1
17. CPLD is a
- Complex Programmable Logic Device
  - Combination Programmable Logic Display
  - Complex Preventable Logic Display
  - Combined programmable Logic Device
18. Hamming code is used to
- Detect the error
  - Correct the error
  - Detect and Correct the error
  - Correct any no of Errors
19. In SRAM Content will be available
- Till the power goes
  - Till the refreshing is done
  - Even after the power goes
  - Even after the refreshing is not done
20. The type of RAM use in Computers are
- SRAM
  - DRAM
  - KRAM
  - PLD

**PART B (5 x 16 = 80 Marks)**

21. a. i, Express the Boolean function  $F=A+B'C$  in sum of min terms (8)  
ii. Express the Boolean function  $F=xy+x'z$  in product of max terms (8)

(OR)

- b. Discuss the Levels in NAND implementation with example (16)

22. a. Explain the special characteristics of digital integrated circuits (16)

(OR)

- b. Discuss in detail about the complementary MOS circuits (16)

23. a. i. Explain the concept of full adder (4)

- ii. Draw and Explain 4 bit adder subtracter (12)

(OR)

- b. Draw and Explain quadruple 2 to 1 line multiplexer (16)

24. a. i. Discuss the various latches with diagram (8)

- ii. Draw and Explain the edge triggered Master Slave D Flip-flop (8)

(OR)

- b. Explain the concept of 4 bit binary counter with parallel load with diagram. (16)

25. a. Elucidate the write and read operation in RAM with the timing diagram(16)

(OR)

- b. Explain in detail about the sequential programmable devices (16)

\*\*\*\*\*