

B.E. DEGREE EXAMINATIONS: APRIL / MAY 2009

Fourth Semester

ELECTRICAL AND ELECTRONICS ENGINEERING**U07EE402 Electronic Circuits****Time: Three Hours****Maximum Marks: 100****Answer ALL the Questions:-****PART A (20 x 1 = 20 Marks)**

1. A BJT operating in the active region has the magnitude at the reverse bias is increases, the effective base width
 - a) Remains unaltered
 - b) increases
 - c) decreases
 - d) may increase or decrease depending on the nature of transistor material
2. When a BJT is fully switches ON, it is said to be
 - a) shorted
 - b) saturated
 - c) open
 - d) cutoff
3. Input resistance of FET common source amplifier in its low frequency small signal operation is
 - a) very small
 - b) medium
 - c) high
 - d) almost infinite
4. In class AB amplifier with sinusoidal input signal, output current flow for
 - a) full cycle
 - b) more than half cycle
 - c) half cycle
 - d) less than half cycle
5. In a single tuned tapped capacitance coupled amplifier, tapping on the coil is used to
 - a) permit use of smaller coil
 - b) permit use of smaller tuning capacitor
 - c) permit maximum transfer of power
 - d) permit adjustment of 3 dB band width
6. The difference between the two input voltage signals
 - a) differential amplifier
 - b) feed back amplifier
 - c) small signal amplifier
 - d) small and large signal amplifiers
7. If $I_{B1} = 85 \mu\text{A}$ and $I_{B2} = 750 \mu\text{A}$ through the base resistor of differential amplifier. Its input offset and input bias currents are
 - a) $600 \mu\text{A}$ and $500 \mu\text{A}$
 - b) $625 \mu\text{A}$ and $625.5 \mu\text{A}$
 - c) $400 \mu\text{A}$ and $500 \mu\text{A}$
 - d) $665 \mu\text{A}$ and $471.5 \mu\text{A}$
8. The multistage amplifier with tuned circuit which are tuned at different frequencies
 - a) stagger tuned amplifier
 - b) double tuned amplifier
 - c) single tuned amplifier
 - d) synchronously tuned amplifier
9. In negative feedback amplifier use of series mixing causes the input resistance to
 - a) decrease
 - b) increase
 - c) zero
 - d) unaltered
10. The common source amplifier using unbypassed resistor in the source lead is a negative feedback amplifier using
 - a) current series feedback
 - b) voltage series feedback
 - c) current shunt feedback
 - d) voltage shunt feedback

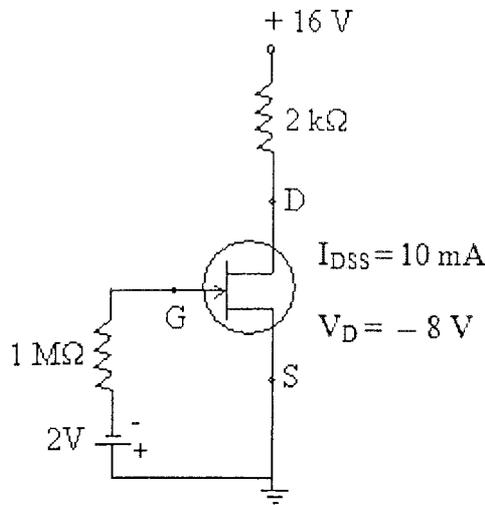


Fig 1

(OR)

21. b) With a neat sketch explain the working of push pull class B amplifier and derive the equation for efficiency. How cross over distortion can be rectified? (16)

22. a) Draw the circuit diagram of a differential amplifier. Explain the operation in difference mode and common mode. (16)

(OR)

22. b) With a neat diagram explain the characteristics of signal tuning amplifier. Also explain the expressions for Gain. What are the advantages? (16)

23. a) Discuss in detail the characteristics of negative feed back amplifier. (16)

(OR)

23. b) Draw and explain the Hartley oscillator circuit and mention the Crystal oscillator applications. (16)

24. a) Calculate the component values of mono stable multi vibrator and developing an output pulse of $500\mu\text{s}$, duration. Assume the h_{fe} (min), $I_{ce}=5\text{ma}$, $V_{cc}=10\text{v}$, and $V_{bb}=-4\text{v}$ (16)

(OR)

24. b) Explain the various types of clipper and clamper circuit with its examples. (16)

25. a) Describe the working principles of full wave rectifier with LC filter and derive its ripple factor. (16)

(OR)

25. b) Give a short note on (i) Series voltage regulator (ii) . SMPS (8+8)
