

Reg. No. :

A 1214

B.E./B.Tech. DEGREE EXAMINATION, NOVEMBER/DECEMBER 2008.

Third Semester

Electronics and Communication Engineering

EC 231 — NETWORK ANALYSIS AND SYNTHESIS


Time : Three hours

Maximum : 100 marks

Answer ALL questions.


PART A — (10 × 2 = 20 marks)

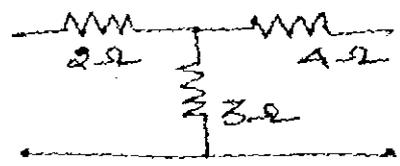1. What is Transfer function?
2. Find the Z parameters for the circuit.




3. What are the advantages of PSPICE?
4. Compute e^{AT} for $\begin{bmatrix} 0 & 2 \\ -1 & 0 \end{bmatrix}$.
5. What are zeros of Transmission?
6. List out the properties of LC network.
7. What is the use of frequency transformation?
8. List out the ideal characteristics of OP-Amp.
9. What is normalization in filter design?
10. Compare the passive filters and active filters.

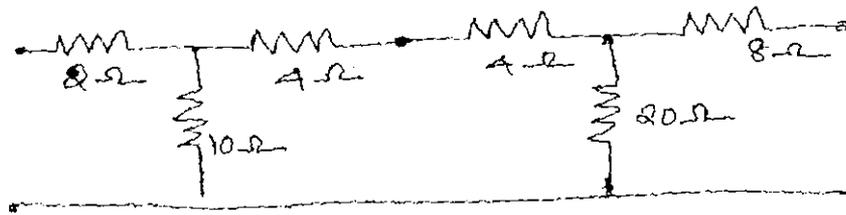11. (a) Find the transmission parameters for the cascaded network



Or

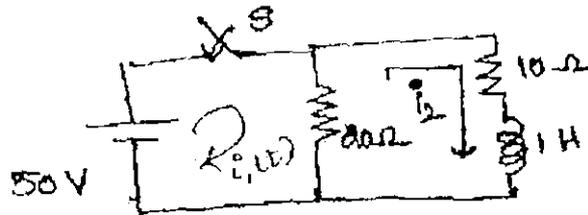- (b) Obtain the equations for $i_1(t)$ and $i_2(t)$ when the switch is closed at $t = 0$ for the given circuit.




12. (a) Find the time response for unit step input of a system.

$$\dot{X}(t) = \begin{bmatrix} 0 & 1 \\ -2 & 3 \end{bmatrix} X(t) + \begin{bmatrix} 0 \\ 5 \end{bmatrix} u(t)$$

$$Y(t) = \begin{bmatrix} 0 & 1 \\ -2 & 3 \end{bmatrix} X(t) \text{ and } Y(0) = \begin{bmatrix} 1 \\ 0 \end{bmatrix}$$

Or

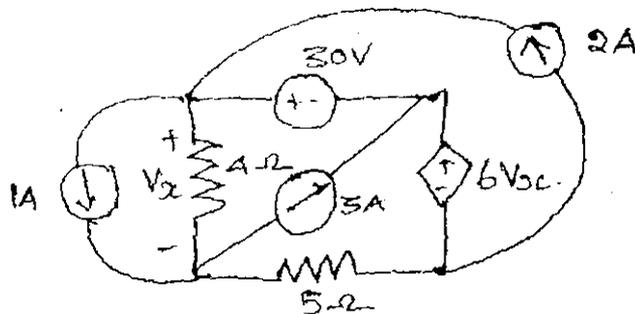- (b) Find the value of V_x in the circuit of figures shown below using Graph theory.



13. (a) Find the two foster realizations of $Z(S) = \frac{4(S^2 + 1)(S^2 + 16)}{S(S^2 + 4)}$.


Or

- (b) (i) Test whether the following polynomial is Hurwitz
 $S^4 + 2S^3 + 2S^2 + 6S + 10$. (8)
- (ii) Check the positive realness of the following function $\frac{(S^2 + 2S)}{(S^2 + 1)}$. (8)

14. (a) Synthesis the given transfer function $Z_{21} = \frac{1}{S^3 + 2S^2 + 2S + 2}$.

Or

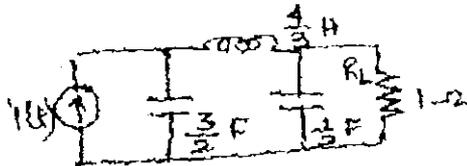- (b) Convert the given low pass filter in to high pass filter with following specifications : $\omega_c = 10^6$ rad/sec, $R_L = 500 \Omega$



15. (a) Design a second order Low-pass butter worth active filter with a cut off frequency of 4.5 KHZ with pass band gain 2.

Or

- (b) Design a high pass active filter with a cut off frequency of 15 KHZ with pass band gain 1.5.