

BE DEGREE EXAMINATIONS: OCTOBER / NOVEMBER-2008

Second Semester

ELECTRONICS AND COMMUNICATION ENGINEERING

U07EC201: Circuit Analysis

Time: Three Hours


Maximum marks: 100

Answer ALL Questions: -

PART A (20x 2= 40 Marks)


1. Value of source voltage E in Fig 1

- A) 12V
- B) 24V
- C) 30V
- D) 44V

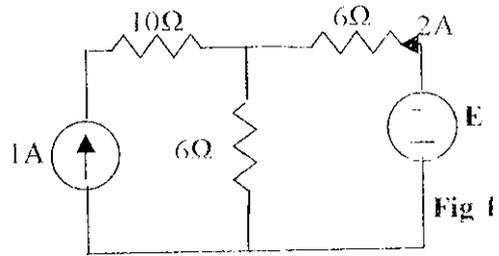


2. The value of resistance R in Ω in Fig 2

- A) 10
- B) 20
- C) 30
- D) 40

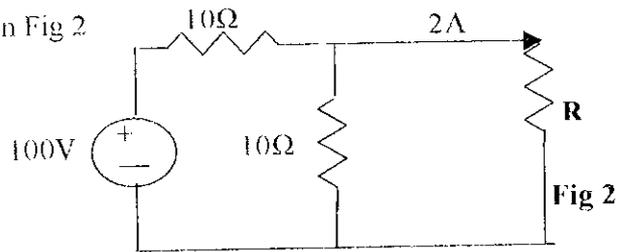

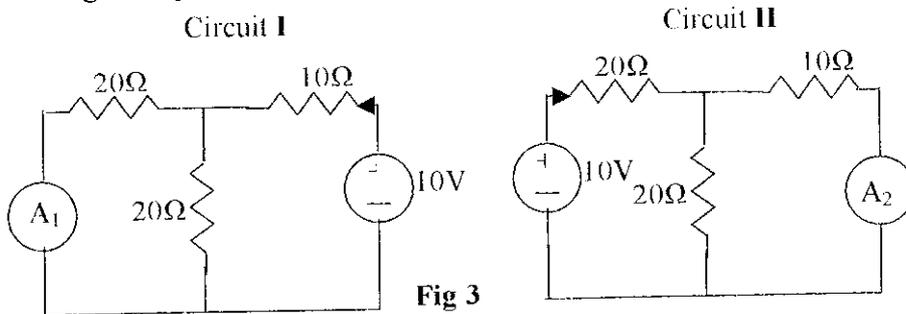3. Consider the circuits I and II in Fig 3, which of the following statements regarding the current flowing through the ammeters A_1 and A_2 is correct.



- A) The currents A_1 and A_2 are of same value and equal to 0.25A.
- B) The currents A_1 and A_2 are 0.25A and 2.5A respectively
- C) The currents A_1 and A_2 are of same value and equal to 2.5A.
- B) The currents A_1 and A_2 are 2.5A and 0.25A respectively

4. The current flowing through 120Ω resistor in the circuit shown in Fig 4

- A) 1A
- B) 2A
- C) 3A
- D) 4A

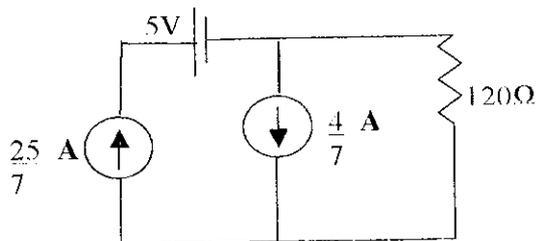


Fig 4

5. R_a, R_b, R_c are $20\Omega, 10\Omega, 10\Omega$ respectively. The resistances R_1, R_2 and R_3 are in ohms of an equivalent star connection as shown in Fig 5 is calculated as

- A) 2.5, 5, 5
- B) 5, 5, 2.5
- C) 5, 2.5, 5
- D) 2.5, 5, 2.5

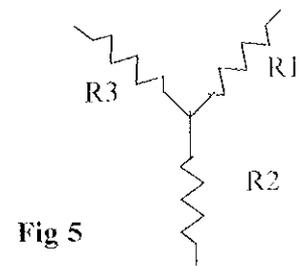
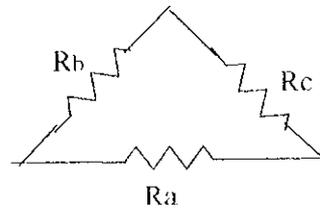


Fig 5

6. A network is said to be nonlinear if it does not satisfy

- A) Superposition condition
- B) homogeneity condition
- C) Both Superposition condition and homogeneity condition
- D) associative condition

7. The equivalent impedance between A and B in Fig 7

- A) 3Ω
- B) 3.2Ω
- C) 3.75Ω
- D) 20Ω

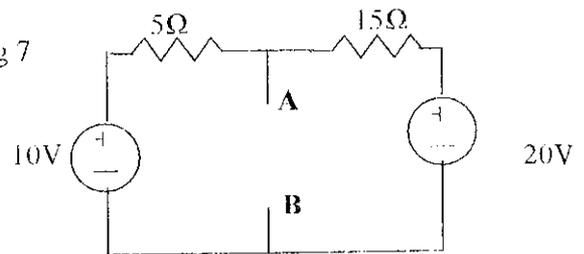


Fig 7

8. Regarding Norton's equivalent which of the following is not correct

- A) Norton's equivalent is the voltage equivalent of the network.
- B) Norton's equivalent is the current equivalent of the network.
- C) Norton's equivalent resistance is the same as the Thevenin's equivalent resistance.
- D) The load is connected in parallel Norton's equivalent resistance and Norton's equivalent source.

9. In the circuit shown in Fig 9, the voltage function is $v(t) = 150\sin\omega t$.

The average power in the resistance R will be

- A) $300W$.
- B) $450W$.
- C) $750W$.
- D) $700W$.

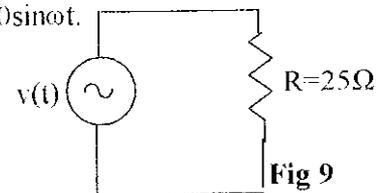


Fig 9

10. A series RLC circuit consisting of $R = 10\Omega, X_L = 20\Omega$ and $X_C = 20\Omega$ is connected across an ac supply of $100V$ (rms). The magnitude and phase angle of the voltage across inductance coil are respectively.

- A) $100V, \angle 90$
- B) $100V, \angle -90$
- C) $200V, \angle -90$
- D) $200V, \angle 90$

11. The series circuit in Fig 11 has a current $i = 2\cos 500t$ A,

The applied voltage will be

- A) $22.4 \sin(5000t + 63.4)V$
- B) $22.4 \cos(5000t - 63.4)V$
- C) $22.4 \sin(500t - 63.4)V$
- D) None of the above

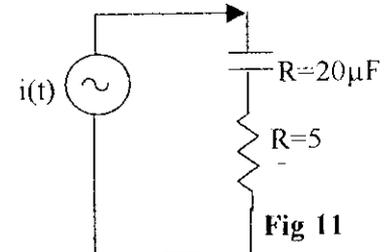


Fig 11

12. The emf in a circuit is given by $e = 100\sin 628t$ volts then the maximum value of voltage and frequency are

- A) $100V, 50Hz$
- B) $100V, 100Hz$
- C) $100\sqrt{2}V, 100Hz$
- D) $100\sqrt{2}V, 50Hz$

13. Find the value of Z in Fig 13, which is more appropriate to cause parallel resonance at $500Hz$.

- A) $125.00mH$
- B) $304.20\mu F$
- C) $2\mu F$
- D) $0.05\mu F$

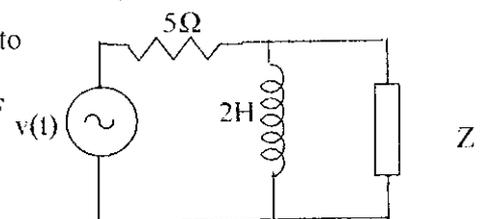


Fig 13

14. Transient currents are due to

- A) Voltage applied to the circuit. B) Resistance of circuit.
 C) Impedance of the circuit. D) Energy stored in inductor and capacitor

15. When testing a coil having a resistance of 10Ω , resonance occurred at 10MHz , value of capacitor was set at $500/20\text{ pF}$. The effective value of Q of the coil is

- A) 200 B) 254 C) 314 D) 542

16. For the network in Fig 16, switch S is closed at $t = 0$.

The capacitor is uncharged the value of current at $t = 0^+$

- A) 0 A B) 0.1A C) 0.01A D) 0.001A

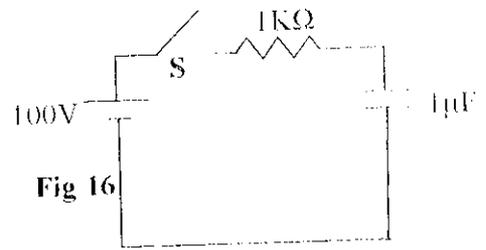


Fig 16

17. If there are 'b' branches and 'n' nodes, the number of equation is given by

- A) b B) b-n C) b + n + 1 D) b - n + 1

18. When a graph has 'b' branches and 'n' nodes, the number of chords is given by

- A) b B) b-n C) b + n + 1 D) b - n + 1

19. Two coupled coils $L_1 = 0.8\text{H}$ and $L_2 = 0.2\text{H}$ have a coupling coefficient $K = 0.9$. The mutual inductance M is

- A) 0.144H B) 0.23H C) 0.36H D) 0.43H

0.3H

20. The equivalent inductance of the parallel connection is

- A) 0.25H B) 0.32H C) 0.34H D) 0.38H

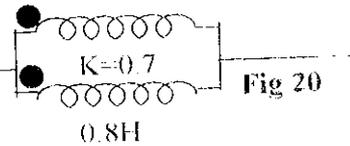


Fig 20

PART B (5x 12= 60 Marks)

21. (a) (i) State Kirchhoff's laws.

(4)

(ii) Find the currents in all the branches of the network in Fig 21 a

(8)

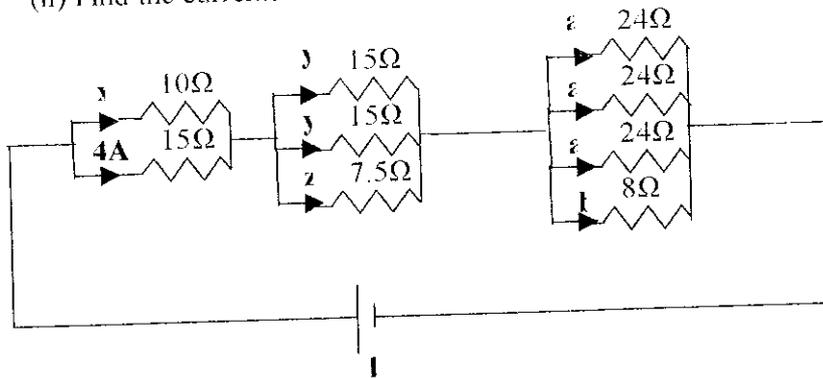


Fig 21 a

(OR)

21. (b) Determine the mesh currents in the circuit shown in Fig 21 b

(12)


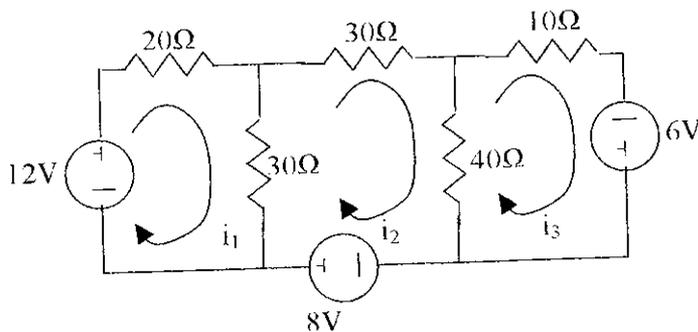


Fig 21 b

22. (a) (i) State and explain maximum power transfer theorem. (4)

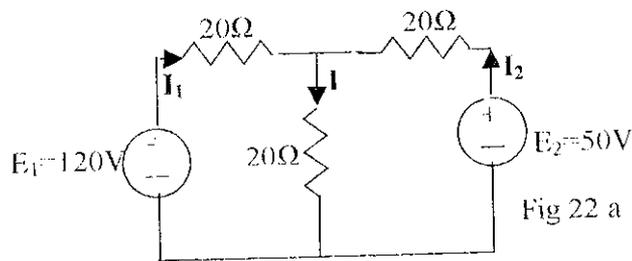
(ii) Determine the current I in the network shown in Fig 22 a using Thevenin's theorem. (8)



(OR)

22. (b) (i) State Norton's theorem. (2)

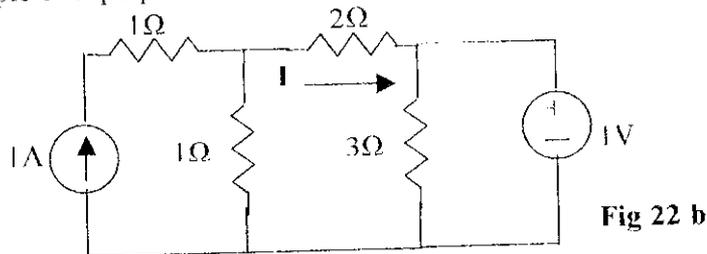(ii) Using the principle of superposition, find I in the circuit given in Fig 22 b (10)



23. (a) (i) Find the power delivered by the 60Hz ac generator to the load impedance in the circuit shown in Fig 23 a (8)

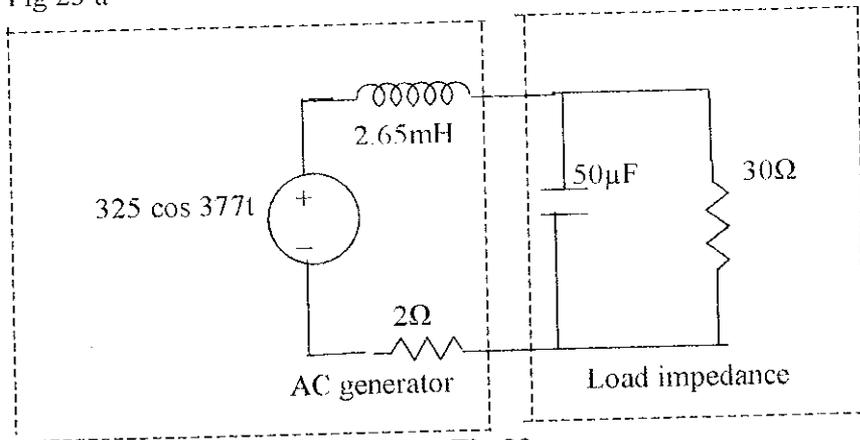


Fig 23 a

(ii) Find the two elements in a series circuit given that the current and total voltage are (4)
 $i(t) = 10\cos(5000t - 23.13)A$
 $v(t) = 10\cos(5000t + 30)V$

(OR)

23. (b) In the circuit shown in Fig 23 b, $Z_1 = 60\angle -30^\circ\Omega$ and $Z_2 = 40\angle 45^\circ\Omega$, calculate the total apparent power, real power, reactive power and power factor. (12)


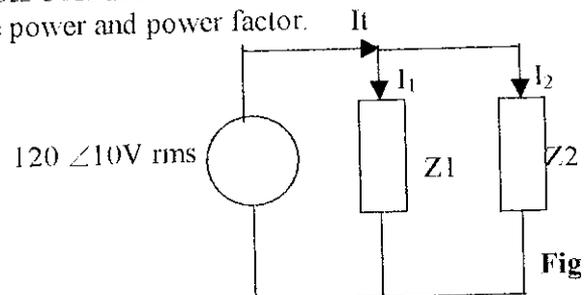



Fig 23 b

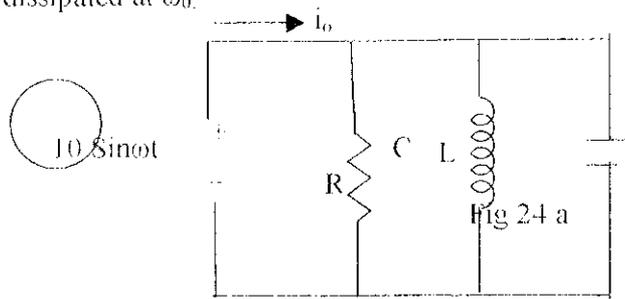24. (a) In a parallel RLC circuit shown in Fig 24 a. Let $R = 8K \Omega$, $L = 0.2mH$ and $C = 8\mu F$. Calculate resonant frequency, quality factor, bandwidth, half power frequencies ω_1 and ω_2 . Determine the power dissipated at ω_0 . (12)




(OR)

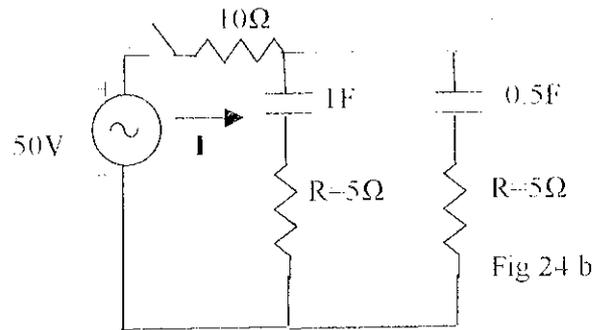24. (b) In the network shown in Fig 24 b switch is closed at $t = 0$ and there is no initial charge on either of the capacitors. Find the resulting current I .





25. (a) Find the drop across R_L . (12)

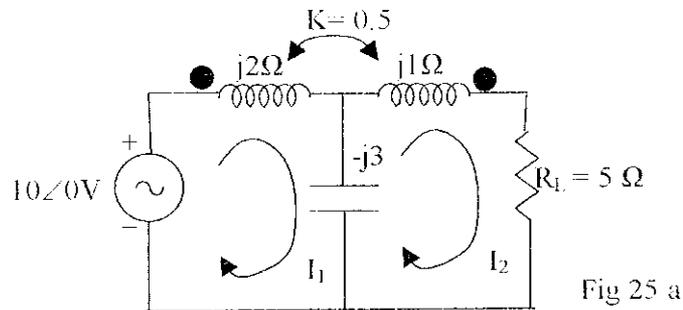

(OR)

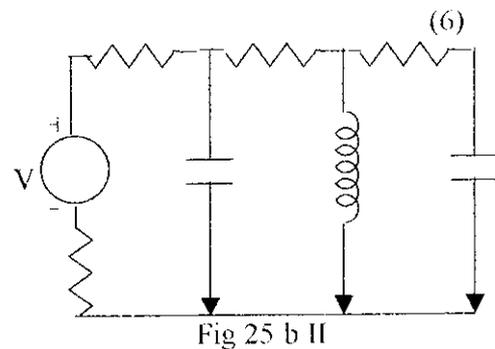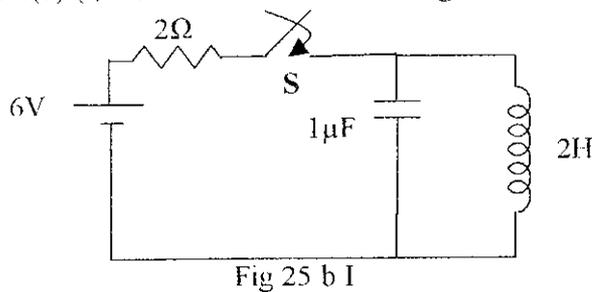25. (b) (i) Draw the dual circuit for Fig 25 b I (6)



- (ii) Draw the graph of the given network shown in Fig 25 b II (6)
