

B.E & B.TECH. DEGREE EXAMINATIONS: OCTOBER / NOVEMBER-2008

Second Semester

U07PH206: PHYSICS-II**(Common for Computer Science Engineering & Information Technology)****Time: Three Hours****Maximum marks: 100****PART A (20 x 1 = 20 Marks)****Answer ALL Questions:-**

- The equivalent resistance of the resistors 20Ω and 30Ω connected in parallel is
 - 12Ω
 - 6Ω
 - 50Ω
 - 10Ω
- There is a voltage drop of 100 volts across a resistance of 100Ω . How much Power will be consumed
 - 1000W
 - 100W
 - 10W
 - 0.1W
- The property of opposition to change in current is
 - Resistance
 - conductance
 - Inductance
 - capacitance
- How many nodes are there in fig: 1?
 - 6
 - 5
 - 3
 - 4

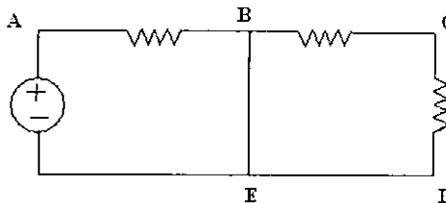


Fig: 1

- Maximum power is transferred from source to load when the load resistance R_L is equal to the source resistance R_S is
 - equal to the source resistance R_L
 - zero
 - greater than R_L
 - lesser than R_L
- Thevenin's theorem states that a circuit with two terminals can be replaced by an equivalent circuit consisting of a voltage source
 - in parallel with a resistance
 - in series with a resistance
 - in parallel with a current source
 - in series with a current source
 -
- The relation between the line voltage and phase voltage in star connection is
 - $V_L = \sqrt{3} V_{PH}$
 - $V_L = V_{PH}$
 - $V_L = \sqrt{2} V_{PH}$
 - $V_L = 2 V_{PH}$
- When two impedances are connected in parallel, their equivalent impedance is given by

- a) $Z_1 Z_2$ b) $Z_1 + Z_2$ c) $(Z_1 - Z_2) / (Z_1 + Z_2)$ d) $Z_1 Z_2 / (Z_1 + Z_2)$

9. Which statement is incorrect?

- a) A zener diode is a heavily doped p-n junction diode
- b) A zener diode has sharp breakdown voltage
- c) A zener diode is always forward biased
- d) In the breakdown region, the voltage across zener diode is constant

10. Law of mass action is given by

- a) $n_i = n_p$ b) $n_i^2 = n_p / n_o$ c) $n_i^2 = n_p$ d) $n_o n_i = n_p$

11. When a p-n junction is reverse biased, the barrier potential

- a) becomes zero b) remains constant c) is increased d) is decreased

12. Mass of the hole is

- a) infinite b) zero c) = electron mass d) = Proton mass

13. An inductor in a filter circuit allows -----

- a) direct current but blocks alternating current
- b) alternating current but blocks direct current
- c) both direct and alternating currents
- d) neither direct current nor alternating current

14. The current that flows in the collector in the absence of the input signal is

- a) zero signal collector current
- b) saturation collector current
- c) A.C. collector current
- d) cut off collector current

15. A waveshaping network which has no stable state is

- a) a schmitt trigger
- b) an astable multivibrator
- c) a monostable multivibrator
- d) a pulse position modulator

16. What is β of a transistor when α is 0.98

- a) 98 b) 0.98 c) 0.49 d) 49

17. In a binary ladder network of a DAC, the value of the smaller resistance is $5K\Omega$, what is the resistance value of the other resistance?

- a) $5K\Omega$ b) $10K\Omega$ c) $0.5K\Omega$ d) $50K\Omega$

18. A selective network which passes all the frequencies higher than cut off frequencies and attenuates all other frequencies is called as

- a) a low pass filter b) a high pass filter
- c) a band pass filter d) a band stop filter

19. The gain of an ideal OPAMP is

- a) unity b) zero c) 100 d) infinite

(OR)

- b) i) How are solids classified based on band theory? (6)
ii) What is a Zener diode? Explain its V-I characteristics and application as a voltage regulator with a suitable circuit diagram. (2+8)

24. a) With necessary diagrams, describe the following circuits
i) Full wave bridge rectifier (8)
ii) Common base transistor circuit (8)

(OR)

- b) Draw neat circuit diagrams of RC phase shift oscillator and Hartley oscillator and show how oscillations are sustained in these circuits. (8+8)

25. a) Discuss the following applications of OPAMP
i) Integrator
ii) Relaxation oscillator (8+8)

(OR)

- b) Show how an operational amplifier can be employed as a subtractor and an R-2R ladder digital-to-analog converter. (8+8)