

Register No: .....

**B.E DEGREE EXAMINATIONS: APR/MAY 2011**

Fourth Semester

**ELECTRONICS AND COMMUNICATION ENGINEERING**

U07EC401: Electronic Circuits II

**Time: Three Hours**

**Maximum Marks: 100**

**Answer ALL Questions:-**

**PART A (10 x 1 = 10 Marks)**

1. A gain of the amplifier with feedback is  
(a)  $A/(1-A\beta)$       (b)  $(1-A\beta)/A$       (c)  $(1-A)/A\beta$       (d)  $A\beta/(1-A)$
2. The value of input resistance in shunt-series feedback is  
(a)  $(1-A\beta)/R_i$       (b)  $R_i/(1-A\beta)$       (c)  $(1-R_i)/A\beta$       (d)  $A\beta/(1-R_i\beta)$
3. Energy stored in the tank circuit per cycle is  
(a)  $W_t=SV_t^2$       (b)  $W_t=C^2V_t$       (c)  $W_t=CV_t^2$       (d)  $W_t=C/V_t^2$
4. The Condition for Barkhausen Criteria is  
(a)  $A_v\beta=-1$       (b)  $A_v\beta=1$       (c)  $A_v\beta=0$       (d)  $A_v\beta=2$
5. The quality factor Q for capacitive circuit is  
(a)  $Q=(\omega/CR)$       (b)  $Q=(C/\omega R)$       (c)  $Q=\omega CR$       (d)  $Q=1/\omega CR$
6. Resonant frequency of an LC tank circuit is  
(a)  $f_r=1/2\pi\sqrt{LC}$       (b)  $f_r=2\pi/\sqrt{LC}$       (c)  $f_r=\sqrt{LC}/2\pi$       (d)  $f_r=2\pi\sqrt{LC}$
7. Duty cycle for symmetrical astable multivibrator is  
(a) 0.5      (b) 0.7      (c) 1      (d) 0.2
8. The expression for displacement error is  
(a)  $e_d=(T/\tau)_{\max}/\Delta$       (b)  $e_d=\Delta/(T/\tau)_{\max}$       (c)  $e_d= T/\tau$       (d)  $e_d= \tau/T$
9. In programmable UJT circuit the value of gate voltage  $V_G$  is  
(a)  $V_G=V_{BB}R_3/R_2+R_3$       (b)  $V_G=V_{BB}/R_2+R_3$       (c)  $V_G=V_{BB}R_3/R_2$       (d)  $V_G=R_3/R_2+R_3$
10. The maximum frequency of blocking oscillator is  
(a)  $f_{\max}=1/2T$       (b)  $f_{\max}=2T$       (c)  $f_{\max}=1/3T$       (d)  $f_{\max}=1/4T$

**PART B (10 x 2 = 20 Marks)**

11. List the advantages and disadvantages of negative feedback.
12. The gain of an amplifier is 100 with its bandwidth 10KHz. If 10% of negative feedback is applied, determine  $A_{vf}$  and  $B_{wf}$ .

13. Write the Brakhhausen Criterion.
14. What is piezo electric effect?
15. Write the advantages of tuned amplifiers.
16. Given  $L=250\mu\text{H}$  and  $C_{eq}=560\text{P}_f$ , find the resonant frequency of the tuned circuit.
17. What is meant by self starting astable mutivibrator?
18. What is Schmitt Trigger?
19. What is meant by blocking oscillators?
20. List the applications of pulse transformer.

**PART C (5 x 14 = 70 Marks)**

21. a) Discuss in detail about
  - (i) Voltage series feedback (7)
  - (ii) Current series feedback (7)

**(OR)**

  - b) Discuss in detail about
    - (i) Voltage shunt feedback (7)
    - (ii) Current shunt feedback (7)
22. a) Explain the working principle with neat diagram of
  - (i) Hartley oscillator (7)
  - (ii) Clapp oscillator (7)

**(OR)**

  - b) Explain briefly about
    - (i) Wein bridge oscillator (7)
    - (ii) Pierce oscillator (7)
- 23.a) Explain briefly about
  - (i) Single tuned amplifier (7)
  - (ii) Synchronously tuned amplifier (7)

**(OR)**

  - b) (i) Analyze power gain, power dissipation and efficiency of class C tuned amplifier. (7)
  - (ii) Explain the principle narrowband coil neutralization technique. (7)

- 24.a) (i) Explain the working principle of collector coupled astable multivibrator? (7)  
(ii) Explain the working principle of emitter coupled astable multivibrator? (7)

**(OR)**

- b) Briefly explain the working principle of  
(i) Diode clipper (7)  
(ii) Diode clamper (7)

25.a) Discuss in detail about astable blocking oscillator using Emitter timing.

**(OR)**

- b) (i) Discuss briefly about the function of UJT sawtooth generators. (7)  
(ii) Explain the working principle of bootstrap ramp generator. (7)

\*\*\*\*\*