

B.E., DEGREE EXAMINATIONS: NOV/DEC 2012

Fifth Semester

MECHANICAL ENGINEERING

ECE281 : Electronics and Microprocessor

Time: Three Hours

Maximum Marks: 100

Answer all the Questions:-

PART A (10 x 1 = 10 Marks)

1. Consider the diode operated under forward biased condition .The diode starts conducting ,when it's forward voltage exceeds -----
 - a) Breakdown voltage
 - b) Cut-in voltage
 - c) Threshold voltage
 - d) Break-over voltage
2. Voltage regulators keep a constant..... output voltage when the input or load varies within limits.
 - a) DC
 - b) AC
 - c) Ripple
 - d) Both AC and Ripple
3. In the active region of BJT, the collector-base junction is-biased, the base-emitter is-biased.
 - a) Forward, forward
 - b) Forward , reverse
 - c) Reverse ,forward
 - d) Reverse, reverse
4. The type of feedback used in feedback amplifier is.....
 - a) Negative
 - b) Positive
 - c) Positive & negative
 - d) Regenerative
5. Consider the given Binary number 101101, its equivalent octal number is-----.
 - a) 65
 - b) 55
 - c) 51
 - d) 45
6. How many flip-flops are required to design a modulo-6 up counter?
 - a) 3
 - b) 4
 - c) 5
 - d) 6
7. How many bits are supported by 8085 processor data bus ?
 - a) 16
 - b) 8
 - c) 32
 - d) 64
8. In 8085 processor , ALE is a _____ bus signal.
 - a) Data
 - b) Address
 - c) Control
 - d) DMA

(OR)

- b) Draw the circuit diagram of a synchronous counter using J-K flip-flop. In detail, explain its operation with the necessary timing diagram.

24. a) Explain the architecture of 8085 microprocessor in detail.

(OR)

- b) (i) Explain the various addressing modes of 8085 Microprocessor with an examples. (5)
(ii) Explain any five arithmetic instructions of 8085 Microprocessor with example. (9)

25. a) Explain how I/ O devices are interfaced to the microprocessor system in detail.

(OR)

- b) In detail, Explain the interfacing concepts of traffic light control system with associated assembly level program.
