

**M.E DEGREE EXAMINATIONS: NOV/DEC 2012**

Third Semester

**POWER ELECTRONICS & DRIVES**

PED555: Flexible Ac Transmission System

**Time: Three Hours**

**Maximum Marks: 100**

**Answer all the Questions:-**

**PART A (10 x 2 = 20 Marks)**

1. What are the different methods to control how of power in a parallel path in electrical power systems?
2. What are the factors which limit loading capability?
3. State objective of series compensation.
4. In order to control both active & reactive power flow explain how to inject a voltage in series with line?
5. Why VSC is preferred over CSC?
6. What are the different types of losses in STATCOM?
7. Give the block diagram for a generalized IPFC.
8. Explain how a UPFC is different than a simple VSC.
9. Give the objective of NGH-SSR damping scheme
10. Draw the basic control circuit of TCBR.

**PART B (5 x 16 = 80 Marks)**

11. a) (i) By controlling the magnitude of voltage explain how the reactive power control is possible? (8)
- (ii) What are the different parameters to control power flow in ac systems given their relative importance? (8)

**(OR)**

- b) Write short note on a) Thermal capability b) Dielectric capability c) Stability limit of a power system.

12. a) Explain with a neat sketch and waveforms the TCSC type of series controller.

**(OR)**

- b) Explain with a neat sketch and waveforms the SSSC type of series controller.

13. a) Explain the different Methods of controllable VAR Generator.

**(OR)**

b) (i) Explain the working principle & V – I characteristics of TCR. (8)

(ii) Explain the working principle & V – I characteristics of TSC. (8)

14. a) By means of an block diagram simulate a generalize IPFC which can be operated as a FACTS Controller.

**(OR)**

b) Explain in detail about the UPFC scheme used as a FACTS Controller.

15. a) Explain in detail the phenomenon of sub synchronous resonance (SSR) with an example

**(OR)**

b) (i) How TCBR is used to improve the transient stability. (8)

(ii) Explain in detail the working of Thyristor Controlled Voltage Regulator. (8)

\*\*\*\*\*