

Reg. No. :

**M 2455**

B.E./B.Tech. DEGREE EXAMINATION, APRIL/MAY 2008.

Third Semester

Mechatronics Engineering

EC 154 — DIGITAL ELECTRONICS

Time : Three hours

Maximum : 100 marks

Answer ALL questions.

PART A — (10 × 2 = 20 marks)

1. Convert the Boolean Expression.

$ABC + \overline{BCD} + A\overline{CD}$  to a standard SOP form.

2. Simplify the expression using K-map

$f(A, B, C, D) = \Sigma 0, 2, 3, 4, 6$ .

3. Give the logic circuit of a half subtractor.
4. Differentiate an encoder and decoder.
5. What is a sequential circuit?
6. Give the truth-table for a rising-edge triggered JK flip-flop.
7. What is meant by race and critical race?
8. What is a pulse mode sequential circuit?
9. Name the various blocks of an ASM chart.
10. What is the purpose of ASM chart?

PART B — (5 × 16 = 80 marks)

11. (a) (i) Simplify the Boolean function  
 $F(w, x, y, z) = \Sigma(0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$ .

- (ii) Implement the function

$$F = x'y + xy' + z \text{ with only NOR gates.}$$

Or

- (b) (i) Simplify using tabulation method

$$F = \Sigma(0, 1, 2, 8, 10, 11, 14, 15)$$

- (ii) Express the function as sum of minterms and a product of maxterm

$$F(A, B, C, D) = D(A' + B) + B'D$$

12. (a) (i) Implement a Fulladder using 2 half-adders.

- (ii) Implement the given function with a multiplexer

$$F(A, B, C, D) = \Sigma(0, 1, 3, 4, 8, 9, 15).$$

Or

- (b) (i) Design a digital circuit to convert the BCD to Excess 3 code

- (ii) Write notes on PLA.

13. (a) (i) Draw the logic diagram of a JK flip-flop and discuss its function deciding the characteristic table and hence its characteristic equation.

- (ii) What is a shift register? Explain serial in and serial out shift register.

Or

- (b) (i) What is meant by a synchronous counter?

- (ii) Explain the operation of a BCD ripple counter with suitable logic diagram using JK flip flop.

14. (a) Design an asynchronous circuit with one level input  $x$ . The circuit is to serve as a modulo 4 counter, which counts the number of times the value of  $x$  changes from 0 to 1 and ignores the value of  $x$  changing from 1 to 0.

Or

- (b) Realise the switching function with a static hazard-free two level AND-OR circuit.

(i)  $f(x_1, x_2, x_3, x_4) = x_1x_2 + x_1'x_3x_4$

(ii)  $f(x_1, x_2, x_3, x_4) = x_1'x_3 + x_2x_4 + x_1x_3'x_4'$ .

15. (a) Realise an ASM chart for the function of a T flip-flop.

Or

- (b) Given the state diagram, draw an equivalent ASM chart.

