

G 6028

M.E. DEGREE EXAMINATION, MAY/JUNE 2007.

Second Semester

Applied Electronics

AN 1651 — ANALYSIS AND DESIGN OF ANALOG INTEGRATED CIRCUITS

(Common to M.E. – VLSI Design)

(Regulation 2005)


Time : Three hours

Maximum : 100 marks

Answer ALL questions.

PART A — (10 × 2 = 20 marks)

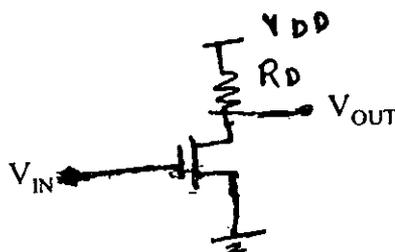1. Draw the small signal model of MOS transistor and define each parameter.
2. Find the drain current and the transconductance for an NMOS transistor operating with $V_{GS} = 2.5$ V, $V_{tn} = 1$ V, $K_n = 1$ mA/V².
3. What is an emitter follower circuit? Give an application for the same.
4. Define $S_{V_{ref}}^{V_{DD}}$ and its significance.
5. What are the various noise signals present in an operational amplifier?
6. Is "Slewing" – a large signal behaviour or small signal behaviour? Justify.
7. How does a basic XOR gate function as phase detector?
8. Calculate the input referred noise for a simple CS stage amplifier shown.



9. Why are active loads advantageous compared to passive loads?
10. Draw the circuit of a simple folded cascode amplifier. State any two of its features.


PART B — (5 × 16 = 80 marks)

11. (a) (i) Analyse the working of MOS in the various regions of operation. (8)
- (ii) Explain the short channel effects in MOS transistors. (8)

Or

- (b) (i) Discuss the effect of impact ionization on MOS transistors and draw the MOSFET representation including the effect. (6)
- (ii) Derive the complete small signal model for an NMOS transistor with $I_D = 120 \mu\text{A}$, $V_{SB} = 0.8 \text{ V}$, $V_{DS} = 2 \text{ V}$. The device parameters are $\phi_f = 0.3 \text{ V}$, $W = 12 \mu\text{m}$, $L = 2 \mu\text{m}$, $r = 0.5 \text{ V}^{1/2}$, $k^1 = 200 \mu\text{A/V}^2$, $\lambda = 0.02 \text{ V}^{-1}$, $t_{ox} = 100 \text{ angstroms}$, $\psi_0 = 0.6 \text{ V}$, $C_{sbo} = C_{dbo} = 10 \text{ fF}$. Overlap capacitance from gate to source and gate to drain is 1 fF . Assume $C_{gb} = 5 \text{ fF}$. (10)

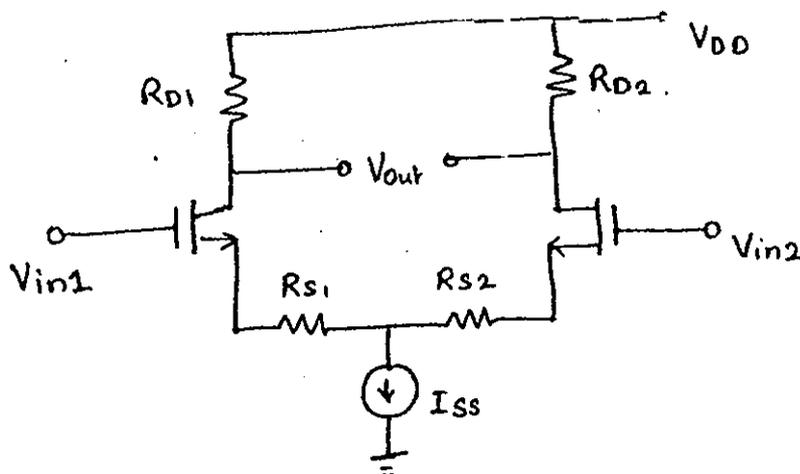12. (a) (i) Draw the circuit of a cascode current source and obtain the expression for $V_D \text{ min}$ and the output resistance. Compare its performance with folded cascode configuration. (8)
- (ii) Assuming no symmetry for the circuit shown below. Calculate the small signal voltage gain $V_{out}/(V_{in1} - V_{in2})$. (8)



Or

- (b) (i) Explain the effect of common mode noise on the differential gain due to mismatch in drain resistance and obtain expression for A_{CM-DM} . (8)
- (ii) Draw the circuit of a complementary class AB output stage using common-source output device and its small signal model. Also explain its transfer characteristics. (8)
13. (a) (i) Consider a CMOS Differential pair with current mirror load and discuss its frequency response. (8)
- (ii) Explain the effect of noise in operational amplifiers. (8)

Or

- (b) (i) Draw the circuit of a telescopic operational amplifier and compare its performance with other types. (10)
- (ii) Using the Miller approximation, calculate the -3 dB frequency of a common source transistor stage with following parameters :
 $R_S = 1 \text{ k}\Omega$, $I_D = 1 \text{ mA}$, $k' \frac{W}{L} = 100 \text{ mA/V}^2$, $f_T = 400 \text{ MHz}$ at
 $I_D = 1 \text{ mA}$, $C_{gd} = 0.5 \text{ pF}$, $C_{gb} = 0$, $R_L = 10 \text{ k}\Omega$. (6)
14. (a) (i) Explain the following application of PLL.
- (1) Skew reduction
- (2) Frequency synthesis. (5 + 5 = 10)
- (ii) Explain the working of two quadrant analog multiplier circuit. (6)

Or

- (b) (i) Discuss in detail the different sources of noise in integrated circuits and their characteristics. (10)
- (ii) Derive an equation for the lock-range and capture-range in PLL. (6)
15. (a) (i) What are current sink and current source? Draw the circuit of a Widlar current source and explain. (8)
- (ii) Explain the working of a class AB amplifier with floating current sources. State its application. (8)

Or

- (b) Write notes on MOS telescopic cascode operational amplifier and MOS active cascode operational amplifiers.