

B 2160

B.E./B.Tech. DEGREE EXAMINATION, MAY/JUNE 2007.

Third Semester

Electronics and Communication Engineering

EC 231 - NETWORK ANALYSIS AND SYNTHESIS


Time : Three hours

Maximum : 100 marks

Answer ALL questions.

PART A — (10 × 2 = 20 marks)

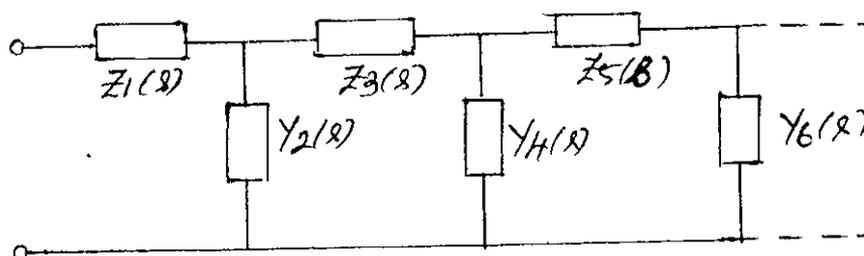1. What is a network element? Distinguish between active and passive elements.
2. A series RL circuit, with $R = 10 \Omega$ and $L = 1 \text{ H}$, has a 100 V source applied at $t = 0$. Find the current for $t > 0$.
3. Define state of a dynamical system.
4. Mention the limitations of PSPICE.
5. A polynomial $P(s)$ expressed in factored form is given by $P(s) = (s - 2)(s + 1)(s + 3)$. Check whether the polynomial is Hurwitz or not.
6. For the ladder network shown, represent the driving point impedance in the form of continued fraction.



7. Give the T and π configuration of low pass filter.
8. The cut-off frequency of an LPF with RC configuration is 500 Hz. Assuming $R = 500 \Omega$, find the value of C.
9. Draw the schematic diagram of an active high pass filter.
10. Mention the advantages of active filters.

PART B — (5 × 16 = 80 marks)

11. (a) (i) Define z-parameters of a two-port network and give the z-parameter model. (8)
- (ii) The following readings are obtained experimentally for an unknown two-port network. Compute the z-parameters. (8)

Output open	V_1	V_2	I_1	I_2
	300 V	60 V	10 A	0
Input open	30 V	40 V	0	3 A

Or

- (b) (i) In a series R-L circuit, the current and voltage are given as $i = 1 \cos(314t - 20^\circ)$, $v = 10 \cos(314t + 10^\circ)$. Find the values of R and L. (8)
- (ii) Obtain transmission parameters in terms of admittance parameters. (8)
12. (a) (i) Obtain the incidence matrix of the graph shown in Fig. 1. (6)


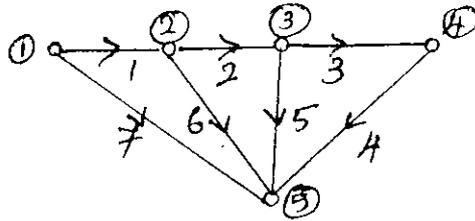


Fig.1.

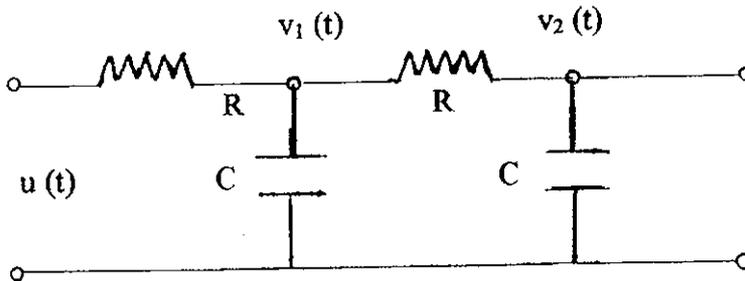- (ii) For the system shown in Fig.2, choose $v_1(t)$ and $v_2(t)$ as state variables and write down the state equations satisfied by them. Bring these equations in vector matrix form. (10)



$R = 1 \text{ M}\Omega, C = 1 \mu\text{F}$

Fig.2

Or

- (b) (i) For the circuit of Fig.3, write the PSPICE program. (8)

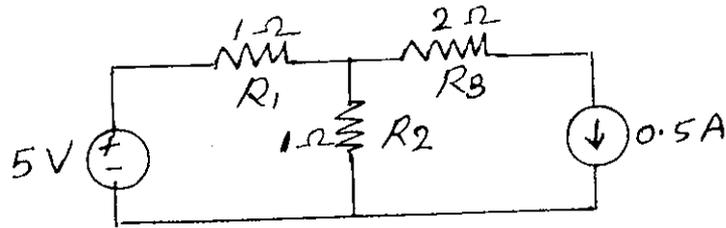


Fig.3

- (ii) Write the fundamental loop matrix of the network shown in Fig. 4. (8)

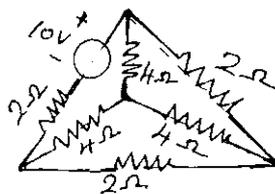


Fig.4

13. (a) (i) Test whether the polynomial $s^5 + s^3 + s$ is Hurwitz or not. (6)
- (ii) The driving point impedance of a one port LC network is given by $Z(s) = 10(s^2 + 4)(s^2 + 25) / s(s^2 + 9)$ Obtain the second Foster form. (10)

Or

- (b) (i) Check whether $Z(s) = 4s + 1/s + 2$ is a positive real function. (6)
- (ii) Synthesize the network having driving point impedance given by $Z(s) = (2s^5 + 10s^3 + 10s)(s^4 + 4s^2 + 3)$ in the first Cauer form. (10)
14. (a) Design a constant K-low pass filter having cut-off frequency 2.5 kHz and design resistance $R_0 = 700\ \Omega$. Also find the frequency at which this filter produces attenuation of 19.1 dB . Find its characteristic impedances and phase constant at pass band and stop or attenuation band. (16)

Or

- (b) Design a prototype band pass filter to match with a load of $600\ \Omega$ and to allow frequencies between 3 kHz and 6 kHz . (16)

15. (a) (i) Describe the realization of active second order Butterworth low pass filter. (8)
- (ii) Design an active second order Butterworth low pass filter with cut-off frequency of 1 kHz. (8)

Or

- (b) Draw and explain the schematic of a first and second order high pass filter. (16)
-

Time : T

1. Dr
(a)
(b)
2. Te
3. F
4. F
z
5. V
6. F
7. I
8. V
- 9.
- 10.