

C 3367

B.E./B.Tech. DEGREE EXAMINATION, MAY/JUNE 2007.

Second Semester

(Regulation 2004)

Computer Science and Engineering

PH 1157 — PHYSICS — II

(Common to Information Technology)

Time : Three hours

Maximum : 100 marks


Answer ALL questions.

PART A — (10 × 2 = 20 marks)

1. State Kirchoff's voltage law.
2. Three equal resistors are connected in parallel and yield an effective resistance of $3\ \Omega$. What is the value of each resistor?
3. Define Thevenin's impedance of a circuit.
4. State the Maximum Power Transfer theorem.
5. How are extrinsic semiconductors formed?
6. JFET is known as 'Unipolar transistor'. Why?
7. Calculate the ripple factor for a half-wave rectifier.
8. State the Barkhausen criterion for oscillators.
9. What is known as the common mode rejection ratio (CMRR) of a differential amplifier?
10. List any two linear, and any two non-linear applications of operational amplifiers.


PART B — (5 × 16 = 80 marks)

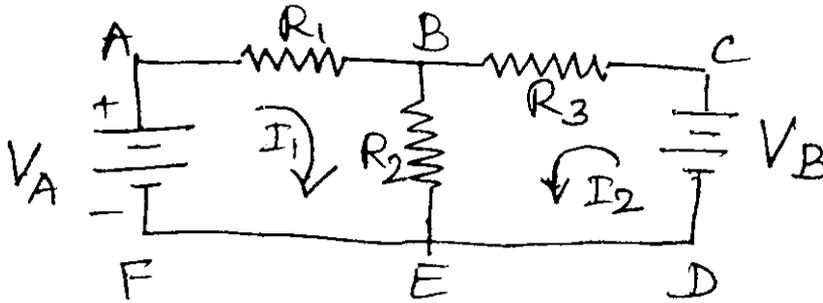11. (a) Using the loop current analysis, obtain the equations for the branch currents I_1 and I_2 of the following circuit.




Or

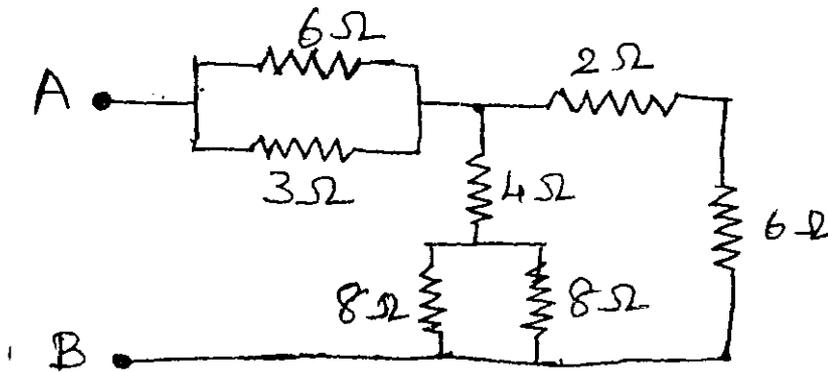- (b) Find the equivalent resistance of the network shown below between the terminals A and B.



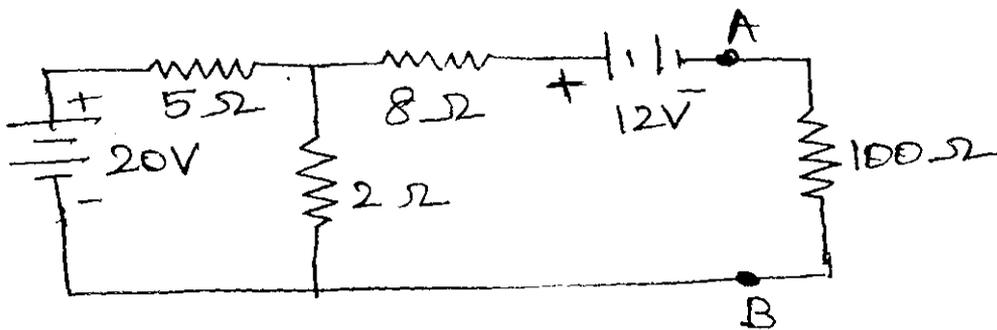12. (a) Find the current in the $100\ \Omega$ resistor connected across AB for the circuit shown below using Thevenin's theorem. (16)



Or

- (b) Explain the procedure for Delta to Star circuit conversions and obtain the relations between their resistances. (16)

- ch
13. (a) Discuss the working of a zener diode, its equivalent circuits, and its V-I characteristics. Also outline its application as a voltage regulator. (12 + 4)

Or

- (b) Explain the working of an N-channel MOSFET in its depletion and enhancement modes with necessary circuit diagrams for biasing.
14. (a) With necessary circuit diagram, discuss the working of a full wave rectifier with capacitor filter and obtain an expression for the ripple factor. (10 + 6)

Or

- (b) Explain the construction and working of a Colpitts oscillator. Also obtain expressions for the frequency and conditions of sustained oscillations. (8 + 4 + 4)
15. (a) Explain the working of an operational amplifier as an inverting summing amplifier and as a subtractor. (8 + 8)

Or

- (b) Discuss the following applications of an operational amplifier :
- (i) Differentiator. (8)
- (ii) Integrator. (8)
-