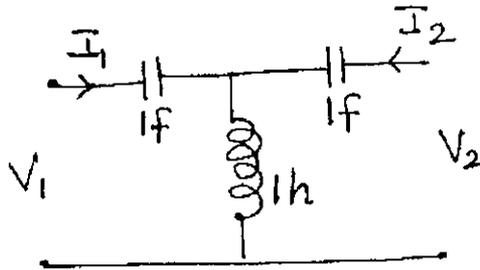





PART B — (5 × 16 = 80 marks)

11. (a) Find the Hybrid and ABCD parameters for the given network.



Or

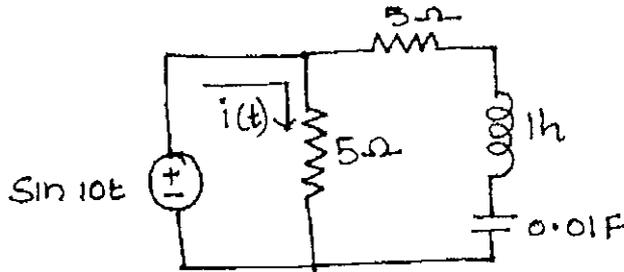- (b) Calculate the steady state current response of the network.




12. (a) Find the time response for the unit step input of a system given

$$\dot{X}(t) = \begin{bmatrix} 0 & 1 \\ -2 & -3 \end{bmatrix} X(t) + \begin{bmatrix} 0 \\ 5 \end{bmatrix} u(t)$$

$$Y(t) = \begin{bmatrix} 0 & 1 \\ -2 & 3 \end{bmatrix} X(t) \text{ and } X(0) = \begin{bmatrix} 1 \\ 0 \end{bmatrix}$$

Or

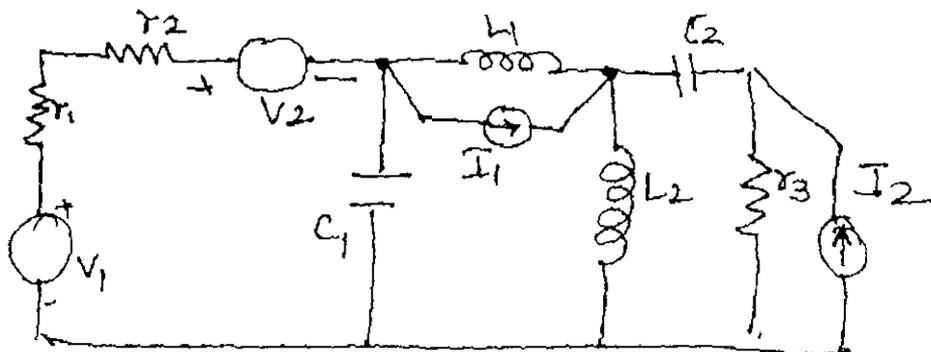- (b) Draw the oriented graph of the network shown below and write incidence matrix.



13. (a) Test the Hurwitz property of the following polynomial :

$$F(s) = s^7 + 2s^6 + 2s^5 + s^4 + 4s^3 + 8s^2 + 8s + 4.$$

Or

- (b) Realize the given driving point impedance function using Cauer forms (Cauer I and Cauer II)


$$Z(s) = \frac{4s^4 + 40s^2 + 36}{s^3 + 4s}.$$

14. (a) Synthesize a third order Butterworth low pass filter terminated in 1 ohm resistance having transfer function.

$$Z_{21} = \frac{1}{s^3 + 2s^2 + 2s + 1}.$$

Or

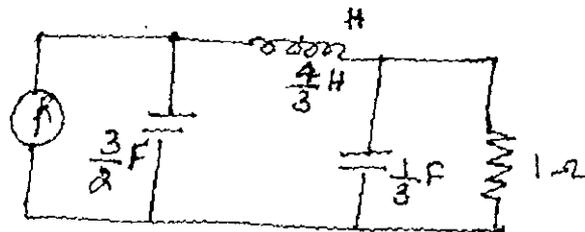- (b) (i) Convert a normalized third order low pass filter into High pass filter with  $\omega_c = 10^6$  rad/sec,  $R_L = 500 \Omega$ . (12)



- (ii) What is Normalization in filter design? (4)

15. (a) (i) Explain how Op-Amps are used as controlled sources. (10)

- (ii) List the characteristics of an Ideal Op-Amp. (6)

Or

- (b) Design a high pass active filter with a cut-off frequency of 10 kHz with pass band gain of 1.5.