

Reg. No. :

S 4031

B.E./B.Tech. DEGREE EXAMINATION, NOVEMBER/DECEMBER 2007.

Second Semester

Mechatronics Engineering

EC 1161 — ELECTRONIC DEVICES AND CIRCUITS

(Regulation 2004)

Time : Three hours

Maximum : 100 marks


Answer ALL questions.

PART A — (10 × 2 = 20 marks)

1. State Kirchoff's voltage and current law.
2. Express Z parameters in terms of Y parameters.
3. What is reverse saturation current in a diode?
4. For a transistor, the thermal resistance is 8°C/W for the ambient temperature T_A of 27°C . If the transistor dissipates 3 W of power, calculate the junction temperature, T_j .
5. What is the need for regulated power supply?
6. What is a voltage multiplier?
7. What are audio and radio oscillators? Distinguish them.
8. Give the hybrid model of a common emitter transistor.
9. List the ideal characteristics of op-amp.
10. What is a window detector?


PART B — (5 × 16 = 80 marks)

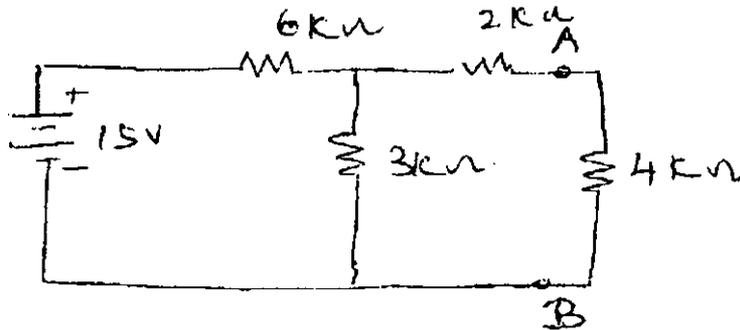11. (a) Thevenise the circuit shown below. Also determine the current through a load resistance R_L , if its value is $4\text{ k}\Omega$. (16)



Or

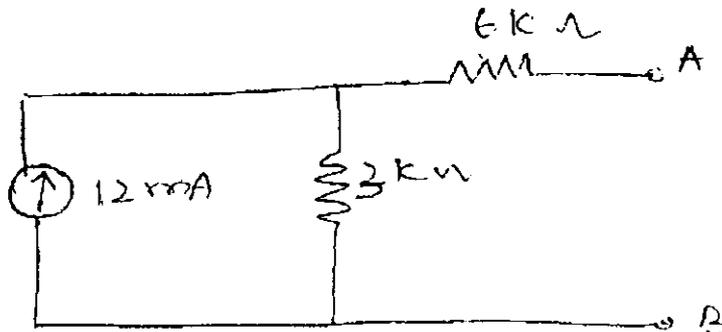- (b) (i) Find the Norton's equivalent circuit for the network shown below. (11)



- (ii) State superposition theorem. (5)

12. (a) Describe the construction and explain the operation of depletion, enhancement IGFET. Also draw the static characteristics.

Or

- (b) Draw the circuit of a CE transistor amplifier with self bias and explain its operation.

13. (a) Explain with circuit diagram, the operation of a Zener shunt regulator.

Or

- (b) Briefly explain the behaviour of PN junction diode in forward bias and reverse bias mode and draw its volt-ampere characteristics.

14. (a) Find the values of voltage gain, current gain, input resistance and power gain for a common emitter transistor amplifier, with $R_L = 1600\Omega$ and $R_S = 1000\Omega$. The transistor has the following set of h parameters ; $h_{ie} = 1100\Omega$ $h_{re} = 2.5 \times 10^{-4}$; $h_{fe} = 100$; $h_{oe} = 25 \mu A/V$.

Or

- (b) Draw a neat circuit diagram of a transistorised colpitt's oscillator with a suitable equivalent circuit, give the expressions for the following :
- Frequency of oscillation.
 - Minimum gain for sustained oscillations.
15. (a) Show with the help of circuit diagram an op-amp used as (i) scale changer (ii) phase shifter (iii) inverting adder and (iv) non-inverting adder. Draw an op-amp circuit whose output is $V_1 + V_2 - V_3 - V_4$.

Or

- (b) Draw and explain the operation of Astable multivibrator using OPAMP IC 741C.