



PART B — (5 × 16 = 80 marks)

11. (a) Explain the V-I characteristics of Bipolar Junction Transistor in CE configuration. (16)

Or

- (b) Explain the function of the following circuits with necessary mathematical expressions using OP-AMP. (4 × 4 = 16)

- (i) Differential amplifier
- (ii) Summer
- (iii) Integrator
- (iv) Differentiator.

12. (a) (i) With a neat diagram explain ADC. (12)

- (ii) What are the digital applications of signal conditioning? (4)

Or

- (b) Design a MOD-10 Decade Counter using JK-Flip Flops. (16)

13. (a) With the necessary diagram explain the working principle and applications of LVDT. (16)

Or

- (b) Write short notes on :

- (i) Ballast circuit. (5)

- (ii) Voltage Divider circuit. (5)

- (iii) Bridge circuit. (6)

14. (a) (i) With neat diagrams, explain any two types of temperature sensors. (12)

- (ii) Discuss the advantages and disadvantages of temperature sensors. (4)

Or

- (b) Write short notes on :

- (i) Indicating and recording devices. (8)

- (ii) Proximity sensors. (8)

15. (a) With a neat diagram explain the working principle of TRIAC and DIAC. (16)

Or

- (b) Explain in detail the computerized Data Acquisition and control in the textile processing industry. (16)