

B.E./B.Tech. DEGREE EXAMINATION, NOVEMBER/DECEMBER 2004.

Second Semester

Electronics and Communication Engineering

EC 142 — CIRCUIT THEORY

Time : Three hours

Maximum : 100 marks

Answer ALL questions.

PART A — (10 × 2 = 20 marks)

1. Find the rms value of $V(t)$.

$$V(t) = 50 \sin(100\pi t + 300).$$

2. State Kirchoff's laws.
3. A generator is having internal impedance $(4 + j5)$ ohm. Determine the required load impedance, for maximum power transfer.
4. Prove Tellegen's theorem for the circuit of Fig. 1.

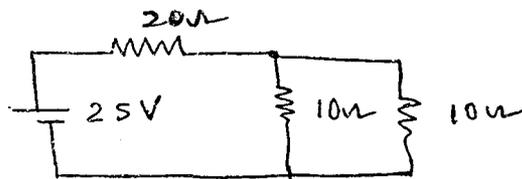


Fig. 1

5. Define quality factor Q of a coil.
6. A series circuit has $R = 10$ ohm $L = 1$ mH $C = 0.01$ μ F. Calculate the resonance Frequency in rad/sec.

7. Plot the impedance of (a) Capacitor (b) Resistor as function of frequency.
8. A circuit has 10 V supply with $R = 100 \text{ ohm}$ $L = 1 \text{ mH}$. What is the time constant of the circuit.
9. Find the dual of the circuit shown in Fig. 2.

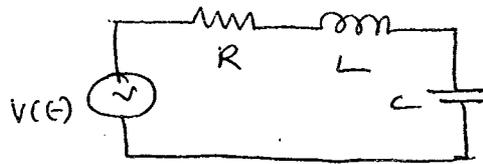


Fig. 2

10. Define (a) Tree (b) Branch of Network.

PART B — (5 × 16 = 80 marks)

11. (i) Determine the mesh currents I_1, I_2 and I_3 for the circuit shown in Fig. 3. (10)

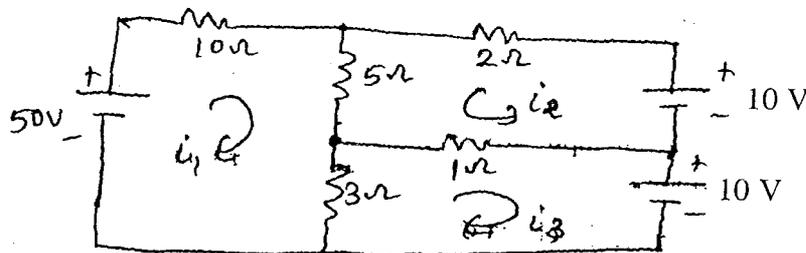


Fig. 3

- (ii) In the circuit shown in Fig. 4, find the value of current through 100Ω . (6)

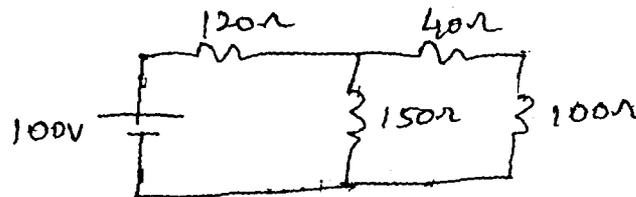


Fig. 4

2. (a) Find the thevenin's voltage and thevenin's resistance for the circuit of Fig. 5 at (a, b) .

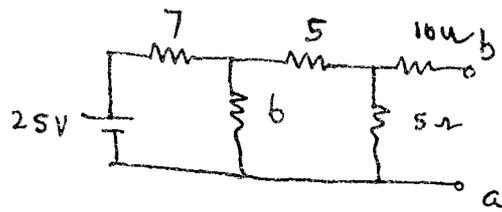


Fig. 5

Or

- (b) Using superposition theorem find the current in 10Ω resistor (Fig. 6)

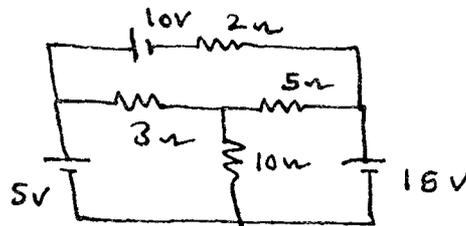


Fig. 6

13. (a) A coil of inductance 0.75 H and resistance 40Ω is a part of a series resonant circuit having a resonant frequency of 160 Hz if the supply voltage is 230 V , 50 Hz . Find (i) current (ii) power factor (iii) voltage across the coil.

Or

- (b) For the circuit of Fig. 7 find an expression for frequency of parallel resonance.

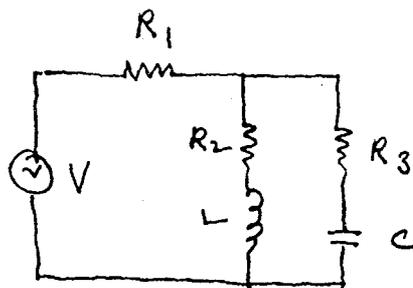


Fig. 7

14. (a) A 10 V supply is in series with $R = 10 \Omega$ and $C = 10 \mu\text{F}$ and a switcher. The switch is closed at $t = 0$. Calculate the voltage across the capacity after one time constant where (i) $V_c(0) = 0 \text{ V}$ (ii) $V_c(0) = 5 \text{ V}$.

Or

- (b) Explain
 (i) undamped
 (ii) over damped
 (iii) critically damped conditions of R-L-C series circuit.
 Also draw approximate responses in each case.

15. (a) (i) For the graph theorem in Fig. 8
 Find all possible Tree's of the network.

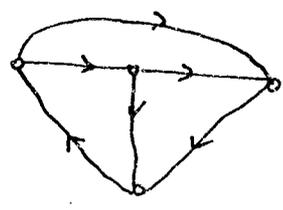


Fig. 8

- (ii) Find the dual of the network shown in Fig. 9.

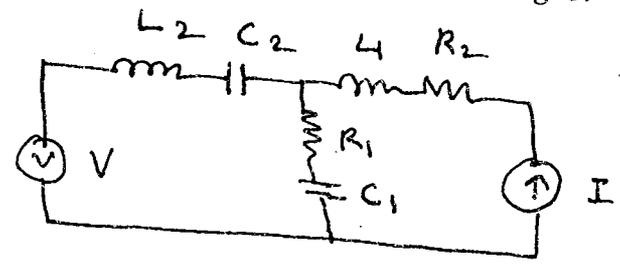


Fig. 9

Or

- (b) For the circuit shown in Fig. 10. Solve for branch currents using Tieset analysis.

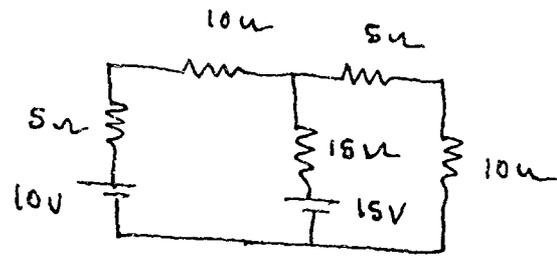


Fig. 10