

M.E DEGREE EXAMINATIONS: JUNE/JULY 2013

Second Semester

POWER ELECTRONICS AND DRIVES

PED506: Solid State DC Drives

Time: Three Hours

Maximum Marks: 100

Answer all the Questions:-

PART A (10 x 2 = 20 Marks)

1. Show the variation of load and temperature rise with time for a continuous duty type of load connected to an electric motor.
2. What are all the conditions to be satisfied for regenerative braking operation to take place?
3. List out the input supply performance parameters of a phase controlled drive.
4. Compare the circulating current mode and non circulating current mode dual converter.
5. Explain briefly with suitable diagram current limit control of dc choppers.
6. What do you mean by a multi phase chopper?
7. What are the advantages of closed loop control?
8. Draw the basic phase locked loop control system for the speed control of dc motor.
9. State the different methods of speed sensing.
10. Give the transfer function relating speed and armature current of a dc motor.

PART B (5 x 16 = 80 Marks)

11. a) (i) Explain the different classes of motor duty with diagram. (8)
(ii) Describe the components of load torques with necessary diagram. (8)

(OR)

- b) (i) A motor runs at a constant speed of 500rpm with a cyclic loading as given (8)
below;
250Nm for 15 minutes
350Nm for 20 minutes
100Nm for 15 minutes
No load for 10 Minutes

Determine the rating of a suitable motor.

- (ii) Explain the multi quadrant operation of a drive with one example. (8)

12. a) (i) Discuss in detail the principle of operation of a single phase full converter, (8)
feeding a separately excited dc motor, with relevant circuit diagrams and

waveforms. Assume the motor current is continuous

- (ii) A separately excited motor operating from a single phase half controlled bridge (8)
at a speed of 1400 rpm has an input voltage of $330 \sin 314t$ and back EMF of 80
volt. The SCR's are fired symmetrically at $\alpha = 30^\circ$ in every half cycle. The
armature has a resistance of 4 Ohms. Calculate the average armature current and
the motor torque.

(OR)

- b) Explain the operation of DC motor operating on three phase full converter with
relevant circuit diagrams and wave forms. Also derive the expression for speed
of a motor.

13. a) Explain the principle of operation of a Type - A chopper. Discuss in detail the
steady state analysis of Type -A chopper.

(OR)

- b) (i) A DC series motor is fed from a 600V source through a chopper. The DC motor (8)
has the following parameters: - $R_a=0.04\Omega$, $R_f=0.06 \Omega$, $K = 4 \times 10^{-3} \text{ N-m/ amp}^2$.
Average armature current of 300 amp is ripple free. For a duty cycle of 60%
determine: - (i) input power drawn from the source (ii) Motor speed and (iii)
Motor torque.

- (ii) Explain the operation of multiphase chopper. (8)

14. a) Explain the operation of a dc motor with closed loop speed control with inner
current loop and field weakening.

(OR)

- b) (i) Derive the transfer function of separately excited dc motor. (8)
(ii) Compare the performance of P, PI and PID controller response in a DC drive. (8)

15. a) What are the different types of firing angle control schemes used for the
converters? Explain any two of them in detail.

(OR)

- b) Describe the operation of Micro Computer based converter fed reversible dc
drive with the necessary block diagram and flow chart.
