

B 307

B.E./B.Tech. DEGREE EXAMINATION, NOVEMBER/DECEMBER 2005.

Fourth Semester

Electronics and Communication Engineering

EC 241 — ELECTRONIC CIRCUITS — II

Time : Three hours

Maximum : 100 marks

Answer ALL questions.

PART A — (10 × 2 = 20 marks)

1. What are the effects of negative feedback on gain and input impedance of an amplifier?
2. What is a negative resistance oscillator?
3. How does the crystal oscillator maintains stable frequency?
4. Why is it difficult to have a variable frequency operation with an RC phase-shift oscillator?
5. What are the drawbacks of LC oscillators?
6. What is the effect of Q on the resonance circuit?
7. What are the advantages of double tuned amplifier over single tuned amplifier?
8. Draw the circuit diagram of a monostable multivibrator (using transistors).
9. What are the applications of pulse transformers?
10. Draw the output response of a RC high-pass filter for a step input and a ramp input.

PART B — (5 × 16 = 80 marks)

11. (i) Describe briefly the general characteristics of negative feedback amplifier. (8)
- (ii) Draw the basic circuit of the voltage shunt feedback amplifier and describe the concepts involved in such an amplifier. (8)

12. (a) (i) With a circuit diagram, explain the principles involved in the Armstrong oscillator. (8)
- (ii) Describe the principles involved in the Twin-T network. (8)

Or

- (b) (i) Draw the circuit diagram of Wien bridge oscillator and explain its working principles. (8)
- (ii) Discuss briefly about the properties of quartz crystal. Draw the electrical equivalent circuit of the crystal and explain. (8)
13. (a) With a neat circuit diagram, explain the performance of single tuned amplifier.

Or

- (b) (i) Describe the principles involved in stagger tuned amplifier. (8)
- (ii) Discuss briefly about neutralization in tuned amplifiers. (8)
14. (a) Draw the circuit diagram of collector coupled astable multivibrator and explain its operation, with relevant waveforms.

Or

- (b) Draw the circuit diagram of a Schmitt trigger and explain its operation showing relevant input and output waveforms.
15. (a) With a neat circuit diagram and relevant waveforms, explain the performance of a triggered transistor blocking oscillator.

Or

- (b) With suitable circuit diagrams, explain the following :
- (i) UJT Sawtooth generator. (8)
- (ii) Miller Sawtooth generator. (8)
-