

**D 4513**

B.E./B.Tech. DEGREE EXAMINATION, MAY/JUNE 2007.

Annual Pattern — First Year

(Regulation 2004)

Mechanical Engineering

EE 1 X 02 — BASIC ELECTRICAL AND ELECTRONICS ENGINEERING

(Common to Aeronautical Engineering/Automobile Engineering/Production Engineering/Marine Engineering)

Time : Three hours

Maximum : 100 marks

Answer ALL questions.

PART A — (10 × 2 = 20 marks)

1. State Kirchoff's laws.
2. Define rms value.
3. Define voltage regulation of a transformer.
4. Why is a shunt motor called constant speed drive?
5. What is meant by synchronous speed?
6. What are the constructional differences between salient pole and cylindrical alternators?
7. What is a transducer?
8. What are minority and majority carriers in a semiconductor?
9. What are frequency synthesizers?
10. What is meant by modulation and demodulation?

PART B — (5 × 16 = 80 marks)

11. (a) (i) Find the current  $I$  which flows through  $10\ \Omega$  resistor in the circuit shown in Fig. 1. All resistances are in ohms. (8)

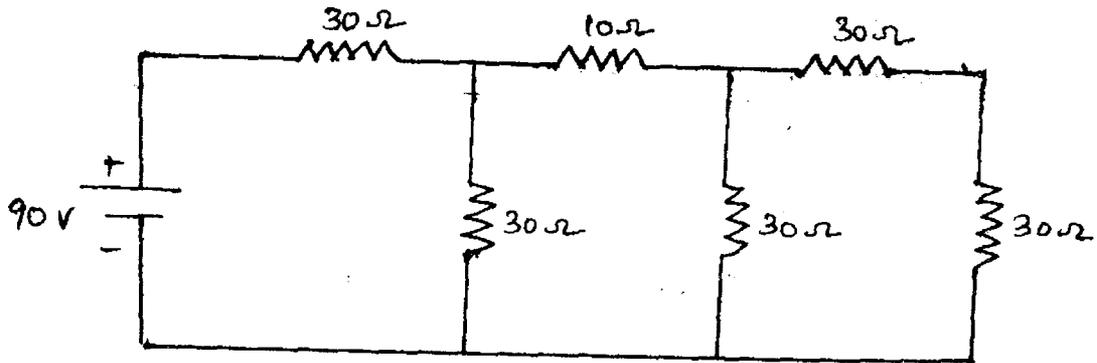


Fig. 1

- (ii) A resistance of 20 ohm and an inductance of 0.2 H and a capacitance of  $100\ \mu\text{F}$  are connected in series across 220 V, 50 Hz main. Determine (1) impedance (2) current taken from mains (3) power and power factor of the circuit. (8)

Or

- (b) What are the essentials of measuring instruments? Explain the construction and theory of operation of single phase induction type energymeter.
12. (a) (i) Derive the equation for induced emf of a dc machine.
- (ii) Explain how voltage is built up in a self excited generator. Draw relevant figures.

Or

- (b) Draw the circuit diagram and discuss the open circuit and short circuit tests on a transformer.
13. (a) Explain with the help of double field revolving theory, how starting torque is obtained in a split phase single phase induction motor.

Or

- (b) Starting from first principle develop the equivalent circuit of a three phase induction motor.

14. (a) Draw the circuit diagram of a full wave bridge rectifier network supplying a resistive load. Explain the operation of the network with relevant waveforms. Also obtain the rectification efficiency.

Or

- (b) Explain the output and input characteristics of a transistor in CB configuration.
15. (a) Draw the block diagram of a TV transmitter and TV receiver. Explain its working in brief.

Or

- (b) (i) What are the different types of modulation?  
(ii) Explain in brief AM transmitter using a block diagram.
-