

E 258

B.E./B.Tech. DEGREE EXAMINATION, NOVEMBER/DECEMBER 2003.

Third Semester

Computer Science and Engineering

CS 232 – DIGITAL SYSTEMS

Time : Three hours

Maximum : 100 marks

Answer ALL questions.

PART A — (10 × 2 = 20 marks)

1. Find the decimal equivalent of $(346)_7$.
2. Find the complement of $x + yz$.
3. Write down the truth table of a half subtractor.
4. Distinguish between positive logic and negative logic.
5. How will you convert a JK flip-flop into a D flip-flop?
6. When is a counter said to suffer from lockout?
7. Distinguish between synchronous and asynchronous sequential logic circuits.
8. What is a shift register?
9. When is a sequential machine said to be strongly connected?
10. What is static 1 hazard?

PART B — (5 × 16 = 80 marks)

11. (i) State and prove DeMorgan's theorem. (6)
- (ii) Determine the MSP (Minimum Sum of Product) form of $F(abcd) = \Sigma (0, 2, 4, 6, 8) + \Sigma_\phi (10, 11, 12, 13, 14, 15)$. (10)

12. (a) (i) Show that the NAND operation is not distributive over the AND operation. (8)
- (ii) Assuming that logic 1 is available, show that INHIBIT logic is functionally complete. (8)

Or

- (b) Explain how will build a 16 input MUX using only 4 input MUXs.
13. (a) Using JK flip-flops, design a parallel counter which counts in the sequence.
000, 111, 101, 110, 001, 010, 000, ...

Or

- (b) Draw and explain a block diagram of circuitry for two registers X and Y of three flip-flops each so that Y can be transferred into X or the 1's complement of Y can be transferred into X
14. (a) (i) Draw the state diagram of a JK flip-flop.
- (ii) Derive the state table of a serial binary adder. (6 + 10)

Or

- (b) The state table of a machine is given below :

PS	NS, Z	
	$x = 0$	$x = 1$
A	A, 0	B, 0
B	C, 0	B, 0
C	D, 0	B, 0
D	A, 0	B, 1

By constructing an adjacency map of the states, determine a good state assignment.

15. (a) Write an explanatory note on derivation of ASM charts and realisation of ASM charts.

Or

- (b) Show that dynamic hazards do not occur in two level AND-OR gate networks.