

B.E DEGREE EXAMINATIONS: DEC 2014

(Regulation 2009)

Second Semester

MECHATRONICS ENGINEERING

ECE280: Electronic Devices and Circuits


Time: Three Hours

Maximum Marks: 100

Answer all the Questions:-

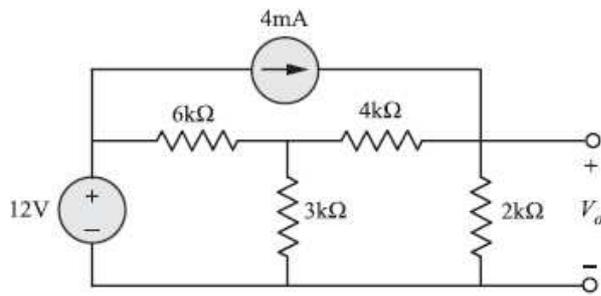
PART A (10 x 1 = 10 Marks)

- What is the condition for reciprocity in Z parameter?
 - $Z_{21}=Z_{12}$
 - $Z_{12}+Z_{21}=0$
 - $Z_{11}=Z_{22}$
 - $Z_{12}=Z_{22}$
- Kirchhoff's current law is applicable only to _____
 - junction in a network
 - closed loops in a network
 - electric circuits
 - electronic circuits
- In semi-conductor, the energy gap between valence and conduction band is about _____.
 - 15 eV
 - 100eV
 - 50eV
 - 1eV
- Gate – source junction in JFET is
 - Forward biased
 - Reverse biased
 - Unbiased
 - in breakdown region
- The ripple factor of half wave rectifier is _____.
 - 2
 - 1.21
 - 0.48
 - 2.5
- A Zener voltage regulator is used for _____ load currents.
 - High
 - Very high
 - Moderate
 - Small
- Closed loop gain of practical oscillators must be _____.
 - Less than 1
 - Greater than 1
 - Equal to 1
 - Equal to 0



(OR)

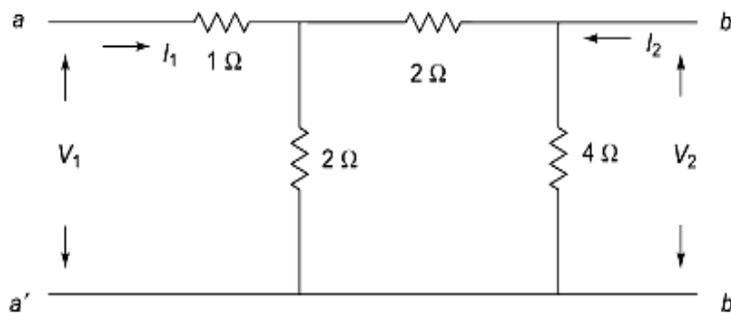- b) Find the h parameters of the given network.



22. a) (i) Compare intrinsic and extrinsic semi-conductors. (4)
 (ii) Explain the operation of pn junction diode in forward and reverse bias. (10)

(OR)

- b) Enumerate the operation and characteristics of Common Base Bi-polar junction transistor.

23. a) Define voltage regulator and hence elucidate the operation of Zener voltage regulator in detail.

(OR)

- b) Give the purpose of using diode rectifiers. Analyse the parameters of half wave rectifier.

24. a) Explain the working of common collector amplifier with neat diagram.

(OR)

- b) (i) State the Barkhausen criteria for oscillation. (2)
- (ii) Discuss the operation of high frequency Hartley oscillator (12)

25. a) (i) Explain how Op-amp works as Instrumentation amplifier (6)
- (ii) Explain the application of Op-amp as sign changer and subtractor. (8)

(OR)

- b) With neat sketches explain the functioning of astable multivibrator and hence derive the period and frequency of oscillation.
