

**B.E DEGREE EXAMINATIONS: DEC 2014**

(Regulation 2009)

Third Semester

**ELECTRICAL AND ELECTRONICS ENGINEERING**

EEE104: Electronic Devices and Circuits

**Time: Three Hours**

**Maximum Marks: 100**

**Answer all the Questions:-**

**PART A (10 x 1 = 10 Marks)**

1. A silicon pn junction in forward condition has a voltage drop closer to
  - a) 0.1 V
  - b) 0.7 V
  - c) 1.7 V
  - d) 2.1 V
2. In LED light is emitted because
  - a) Recombination of charge carriers take place
  - b) Diode gets heated up
  - c) Light falling on gets amplified
  - d) Light gets reflected due to lens action
3. The silicon transistor are more widely used than germanium transistors because
  - a) They have smaller leakage current.
  - b) They have better ability to dissipate heat
  - c) They have smaller depletion layer
  - d) They have larger current carrying capacity
4. An n-channel JFET has  $I_{DSS}=2\text{mA}$ , and  $V_p= -4\text{V}$ . Its transconductance  $g_m=(\text{in mA/V})$  for an applied gate to source voltage  $V_{GS}=-2\text{V}$  is
  - a) 0.25
  - b) 0.5
  - c) 0.75
  - d) 1
5. For a large values of ( $V_{DS}$ ), a FET – behaves as
  - a) Voltage controlled resistor
  - b) Current controlled current source
  - c) Voltage controlled current source
  - d) Current controlled resistor
6. A source follower using a FET usually has a voltage gain which is
  - a) greater than +100
  - b) slightly less than unity but positive
  - c) exactly unity but negative
  - d) about -10



- (i) Calculate the thermal equilibrium density of electrons and holes in the  $p$ -type region as well as both densities in the  $n$ -type region.
- (ii) Calculate the built-in potential of the p-n junction
- (iii) Calculate the built-in potential of the p-n junction at 400 K.

22. a) Explain the principle of operation and UJT and mention its applications.

**(OR)**

- b) (i) What are the applications of JFET? Explain JFET as VVR. (7)
- (ii) Explain the biasing technique for enhancement MOSFET. (7)

23. a) Derive the expression for current gain, input impedance and voltage gain of a CE Transistor Amplifier.

**(OR)**

b) Explain and analyse the low frequency response of RC coupled amplifiers.

- 24. a) (i) How can a cross over distortion be reduced? (2)
- (ii) Explain the working of differential amplifier and derive expression for CMRR. (12)

**(OR)**

b) Draw a neat circuit diagram and explain working of cascade amplifier and derive the expression for gain and frequency response.

- 25. a) (i) Calculate the gain without and with feedback for the FET amplifier circuit of Fig. 1 and the following circuit values:  $R_1 = 80 \text{ k } \Omega$ ,  $R_2 = 20 \text{ k } \Omega$ ,  $R_o = 10 \text{ k } \Omega$ ,  $R_D = 10 \text{ k } \Omega$  and  $g_m = 4000 \text{ } \mu\text{S}$ . (7)

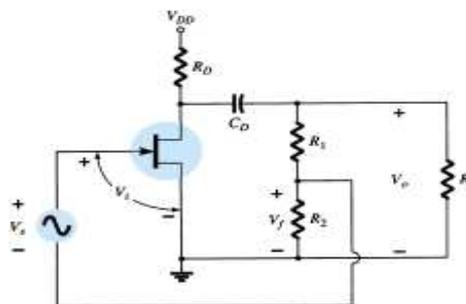


Fig 1

- (ii) Describe the operation of wein bridge oscillator. (7)

**(OR)**

b) Explain the principle of operation and derive the expression for the output in colpitts oscillator.

\*\*\*\*\*