

19. Define cyclo converter. [K₁]
20. Name the commutation techniques of thyristors used in cyclo converters. [K₁]

PART C (10 x 5 = 50 Marks)

21. Derive an expression for average output voltage, RMS output voltage and displacement factor of a single phase fully controlled converter. [K₂]
22. A single phase semi converter delivers power to RLE load with $R=5\Omega$, $L=10\text{mH}$ and $E=80\text{V}$. For a continuous conduction, find the average value of output current for a firing angle delay of 50° and 230V, 50Hz supply. [K₃]
23. Draw the circuit diagram and output waveforms of three phase full converter for the firing angle of 60° . [K₂]
24. Explain the Time Ratio Control of a DC chopper. [K₂]
25. Draw the various types of zero current switch topologies. [K₂]
26. A DC to DC chopper operates from a 48 V battery source into a resistive load of 240Ω . The frequency of the chopper is set to 250Hz. Determine the load power when on-time of the chopper is 1 ms? [K₃]
27. Draw the possible configurations of single phase voltage controllers and compare them. [K₂]
28. A single-phase full wave controller feeds power to a resistive load of 100Ω from a 230V, 50Hz supply. Calculate the rms output voltage, input power factor and the half cycle average current at delay angles $\alpha_1=\alpha_2=\alpha=90^\circ$ of both thyristors. [K₃]
29. Derive the output voltage equation of a cyclo converter. [K₂]
30. Explain the operation of single phase step down cyclo converter. [K₂]

PART D (2 x 10 = 20 Marks)

31. With neat circuit and waveforms explain the working of single-phase dual converter. [K₂]
32. Describe the operation of a three phase three wire AC voltage controller with neat power circuit and waveforms. [K₂]
