



**B.E DEGREE EXAMINATIONS: JUNE 2015**

(Regulation 2009)

Third Semester

**ELECTRONICS AND COMMUNICATION ENGINEERING**

ECE105- Electronic Circuits-I

**Time: Three Hours**

**Maximum Marks: 100**

**Answer all the Questions:-**

**PART A (10 x 1 = 10 Marks)**

- Why capacitive coupling is used to connect a signal to an amplifier?
  - To eliminate the noise
  - To maintain constant biasing
  - To get better efficiency
  - To improve gain of the amplifier
- Which is the most stable biasing circuit?
  - Fixed bias
  - Collector to base bias
  - Self bias
  - Voltage divider bias
- Which one of the following represents reverse voltage gain expression in CE amplifier?
  - $\frac{\Delta v_{be}}{\Delta i_b}$
  - $\frac{\Delta i_c}{\Delta i_b}$
  - $\frac{\Delta i_c}{\Delta v_{cc}}$
  - $\frac{\Delta v_{be}}{\Delta v_{ce}}$
- \_\_\_\_\_ is also called as source follower
  - Common gate stage
  - Common drain stage
  - Common source stage
  - Multistage amplifier
- The overall gain of the multistage amplifier is the \_\_\_\_\_.
  - Sum of individual stage gain
  - Difference of individual stage gain
  - Product of individual stage gain
  - Absolute value of individual stage gain
- Choose the percentage of efficiency in class B Amplifier.
  - 78.5%
  - 25% to 50%
  - 95%
  - 50 to 78.5%
- Which power amplifier gives minimum distortion?
  - Class A
  - Class B
  - Class C
  - Class AB

8. Which one of the following is not a type of SMPS?
- a) step down switching regulator                      b) step up switching regulator  
c) inverting switching regulator                      d) Non inverting switching regulator
9. In which region the transistor will operate to act as a switch?
- a) Cut off    b) Saturation  
c) Cut off and saturation                                      d) Active
10. What is the use of multistage amplifier?
- a) To decrease the amplification                      b) To improve the efficiency  
c) For impedance matching                                      d) To remove the noise

**PART B (10 x 2 = 20 Marks)**


11. What do you mean by thermal runaway?
12. Discuss on zero current drift in FET.
13. State Millers theorem.
14. Mention the advantages of h-parameters.
15. Define CMRR.
16. Define Sag in an amplifier.
17. Name two conditions to be satisfied by a complementary symmetry power stage.
18. What is crossover distortion in a power amplifier and how to eliminate it?
19. Define transformer utilization factor (T.U.F)
20. What is meant by peak inverse voltage?

**PART C (5 x 14 = 70 Marks)**

21. a) (i) Explain about the common source self bias and voltage divider bias for FET.                      (10)  
(ii) Show how a FET can be used as a VVR.    (4)

**(OR)**

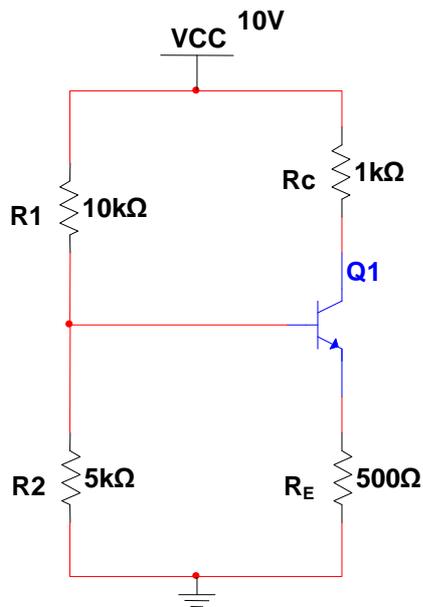- b) For the given circuit calculate  $V_E$ ,  $V_B$ ,  $I_B$ ,  $V_{CE}$  and  $I_C$ , where  $\beta = 100$  for the silicon transistor.



22. a) Draw the hybrid –  $\pi$  model for a common emitter transistor at high frequencies and derive the values of all the components in terms of h – parameter.

**(OR)**

- b) Explain about the common gate amplifier and derive its current gain, voltage gain, input impedance and output impedance expressions.

23. a) Explain the emitter coupled differential amplifier with neat diagram.

**(OR)**

- b) (i) Draw the cascode amplifier and explain in detail. (7)  
(ii) Illustrate the improving method of CMRR. (7)

24. a) Explain in detail about the operation of a class – B push pull power amplifier.

**(OR)**

- b) (i) Briefly explain the use of heat sink in power amplifiers. (6)  
(ii) Derive the expression for the power conversion efficiency of a class A power amplifier with resistive load. (8)

25. a) With necessary sketches explain the working of SMPS.

**(OR)**

- b) (i) A half wave rectifier circuit is supplied from the 230V, 50Hz supply with a (10) transformer having step down ratio of 3:1 to a resistive load of 10 K $\Omega$ . The diode forward resistance is 75  $\Omega$ , while transistor series resistance is 10  $\Omega$ . Calculate maximum, average and RMS value of current.
- (ii) Design a simple zener regulator to give a DC fixed output of 5 volt upto a load (4) current of 50 mA.

\*\*\*\*\*