



B.E DEGREE EXAMINATIONS: JUNE 2015

(Regulation 2013)

Second Semester

U13ECT201: CIRCUIT THEORY

(Common to ECE/EIE)

Time: Three Hours

Maximum Marks: 100

Answer all the Questions:-

PART A (10 x 1 = 10 Marks)

- The voltage across a resistance of 21Ω is $-2.4V$. The power absorbed by the resistor is
 - $+0.27W$
 - $-0.27W$
 - $2.7J$
 - $2.7W$
- Two resistors of $10k\Omega$ each are connected in parallel. The equivalent resistance is
- The maximum power transferred to a load by a source of $5V$ with a source resistance of 10Ω is
 - $2.5W$
 - $25W$
 - $0.625W$
 - $6.25W$
- A voltage source of $+7V$ has a resistance of 5Ω connected in series. The Norton equivalent current is
- The energy stored in a $1000\mu F$ capacitor at $t=50\mu s$ when the voltage applied across it is $1.5\cos(10^5t)$ volts is
 - $90.52J$
 - $90.52mJ$
 - $9.52\mu J$
 - $90.52\mu J$
- An AC voltage given by $v(t) = 5 \sin(2\pi 50t)$ is applied across an inductor of $10mH$. The phasor diagram is
- A resistance of 10Ω is connected in series with an inductance of $5mH$. The time constant of the circuit is
 - 50
 - 5×10^{-2}
 - 2
 - 0.5
- Signals which are discontinuous or have discontinuous derivatives are called
- A series resonant circuit has a bandwidth of $100Hz$ and contains $20mH$ inductance and $2\mu F$ capacitance. The resonant frequency is
 - $1000Hz$
 - $796Hz$
 - $79.6Hz$
 - $100Hz$

10. When the voltage and current in a circuit containing R, L and C is in phase, the circuit is in

PART B (10 x 2 = 20 Marks)

(Not more than 40 words)


11. A closed loop circuit contains 10V DC in series with three resistors of 5kΩ each. What is the voltage across each of the resistors?
12. What is a super mesh?
13. How to find the Thevenin equivalent voltage across the output terminals of a circuit?
14. Enumerate the functions that can be implemented in PSPICE.
15. Distinguish between impedance, admittance and susceptance.
16. Express the given impedance in polar form : $(4.255 + j4.929)\Omega$
17. What is the power absorbed in an RC circuit?
18. An AC current $i(t) = 5 \angle 90^\circ$ flows through an inductor of value 7H. Find the voltage across the inductor.
19. Define Q-factor.
20. Explain dot rule in linear transformer.

PART C (5 x 14 = 70 Marks)


(Not more than 400 words)

Q.No. 21 is Compulsory

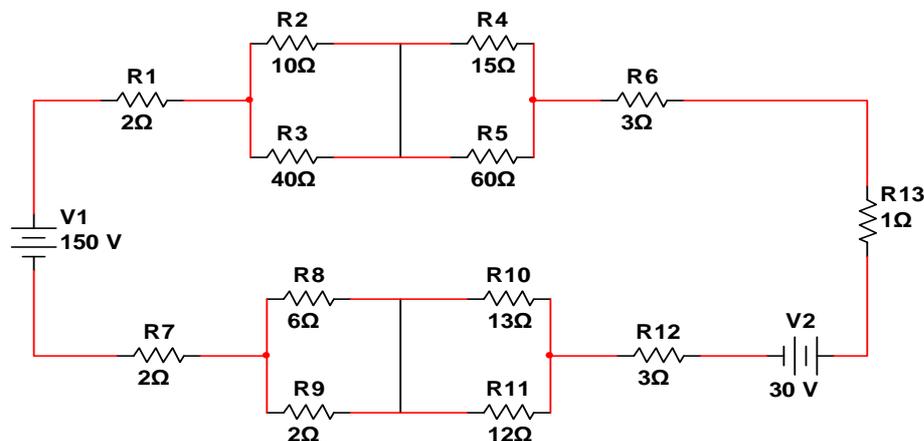21. Find the Thevenin equivalent circuit for output taken across R13.




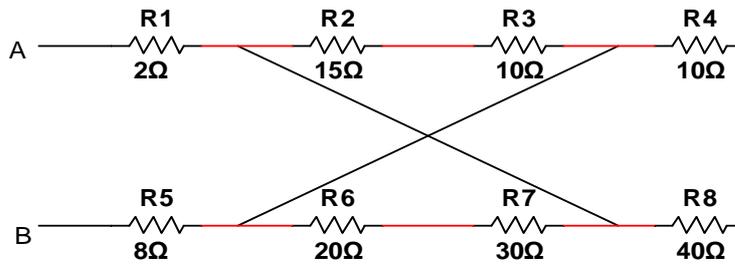22. a) If a DC voltage source with $V = 50$ volts is connected across terminals AB, prove that Kirchoff's voltage and current laws are satisfied.




(OR)

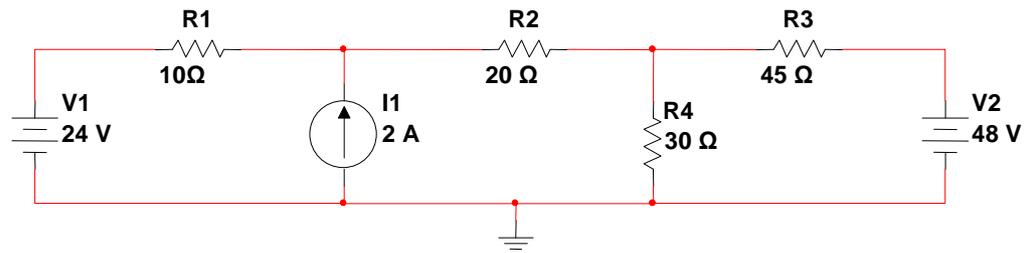
- b) (i) Find the power dissipated by each of the resistors in the circuit below:



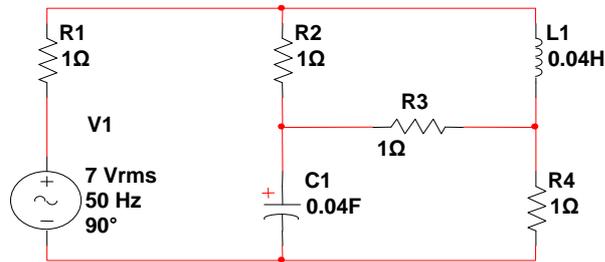23. a) (i) Write the node equations for the circuit given below: (4)




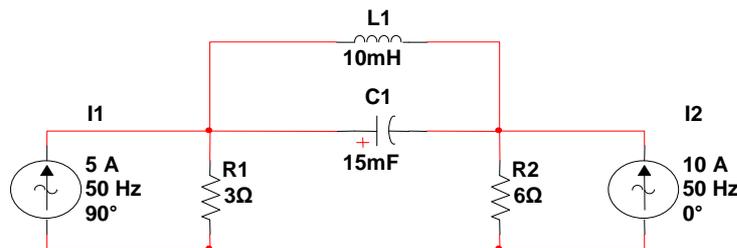- (ii) Compute the power dissipated by each of the elements in the circuit below: (10)



(OR)

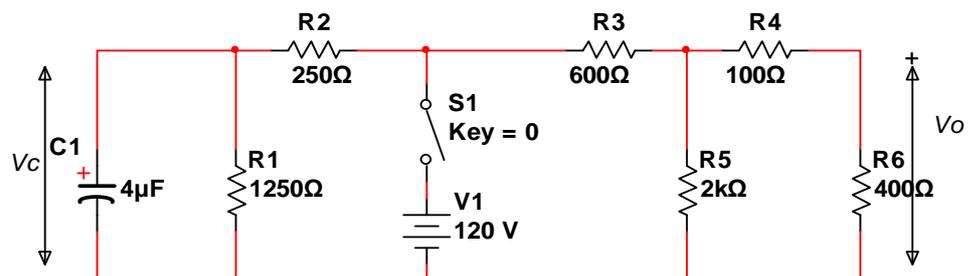- b) Using mesh analysis, find the voltage V_o , assuming the switch S1 closes at $t=0$.




24. a) (i) Given a series RLC circuit with $L = 10 \text{ H}$, $R = 3 \text{ k}\Omega$, $C = 4 \text{ }\mu\text{F}$, $i(0) = 1 \text{ mA}$, $v_c(0) = 0 \text{ V}$, find $i(t)$. (7)

(ii) Draw the source free RC circuit and find its response to $i = 50 \angle 45^\circ$ (7)

(OR)

b) Given a parallel RLC circuit with $L = 3 \text{ H}$, $R = 5 \text{ }\Omega$, $C = 2 \text{ }\mu\text{F}$, $v(0) = 5 \text{ V}$, $i(0) = 10 \text{ A}$, find the step response.

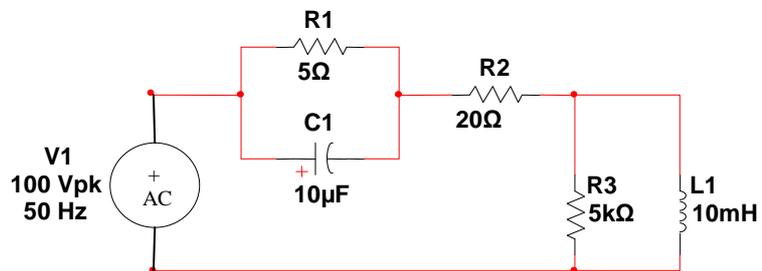
25. a) (i) Find the average power absorbed by each of the passive elements in the circuit below: (10)



(ii) Draw the T and π equivalent circuits of a linear transformer. (4)

(OR)

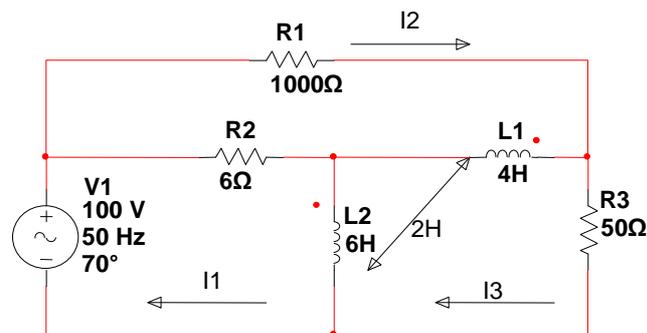b) (i) Write the mesh equations for the circuit given : (7)



(ii) With a neat diagram, explain the working of an ideal transformer. (7)
