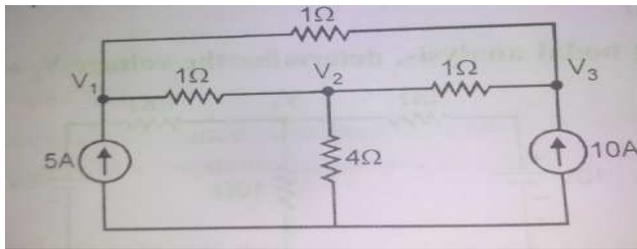


(OR)

- b) Find V_1 , V_2 , V_3 by the nodal method for the given circuit.



23. a) i) A resistor of 20Ω and an inductor of 0.2H and a capacitor of $100\mu\text{F}$ (10) are connected in series across $220\text{V}, 50\text{Hz}$ main. Determine
i) impedance ii) Current taken from mains iii) power iv) power factor.
ii) Define real and reactive power (4)

(OR)

- b) i) In a series RLC circuit, $R=24\Omega$, $L=191\text{mH}$ and $C=66.3\mu\text{F}$ given that (12) the supply voltage is $240\text{V}, 60\text{Hz}$, find (i) equivalent impedance
(ii) power factor (iii) current (iv) power and (v) reactive power.
ii) Define apparent power. (2)

24. a) Describe the working of a PN junction diode with neat diagram. Also explain its V-I characteristics.

(OR)

- b) Explain the operation of full wave bridge rectifier with neat sketch.

25. a) Explain the working principle of Wein bridge oscillator with the help of neat diagram.

(OR)

- b) Explain the working of op-amp non inverting amplifier. Derive the expression for its voltage gain.



