



**B.E DEGREE EXAMINATIONS: MAY 2015**

(Regulation 2013)

Fourth Semester

**MECHATRONICS ENGINEERING**

U13MCT405:Digital Electronics

**Time: Three Hours**

**Maximum Marks: 100**

**Answer all the Questions:-**

**PART A (10 x 1 = 10 Marks)**

- Which of the following expressions is in the sum-of-products (SOP) form?
  - $(A + B)(C + D)$
  - $(A)B(CD)$
  - $AB(CD)$
  - $AB + CD$
- A major advantage of ECL logic over TTL and CMOS is \_\_\_\_\_.
- To implement the expression  $\overline{A}BCD + A\overline{B}CD + ABC\overline{D}$ , it takes one OR gate and \_\_\_\_\_.
  - three AND gates and three inverters
  - three AND gates and four inverters
  - three AND gates
  - one AND gate
- Assume you have A, B, C, and D available but not their complements. The minimum number of 2-input NAND gates required to implement the equation  $X = \overline{A}\overline{B} + \overline{B}\overline{C}$  is \_\_\_\_\_.
- A BCD counter is a \_\_\_\_\_.
  - binary counter
  - full-modulus counter
  - decade counter
  - divide-by-10 counter
- Determine the output frequency for a frequency division circuit that contains 12 flip-flops with an input clock frequency of 20.48 MHz.
- The group of bits 11001 is serially shifted (right-most bit first) into a 5-bit parallel output shift register with an initial state 01110. After three clock pulses, the register contains \_\_\_\_\_.
  - 01110
  - 00001
  - 00101
  - 00110
- With a 200 kHz clock frequency, eight bits can be serially entered into a shift register in \_\_\_\_\_.



**(OR)**

- b) (i) What is race round condition? How is it avoided? (6)
- (ii) Draw the schematic diagram of master-slave JK Flip-flop and discuss how it prevents race around condition. (8)

24. a) Using JK flip-flops, design a synchronous counter which counts in the sequence, 000, 001, 010, 011, 100, 101, 110, 111, 000.

**(OR)**

- b) (i) Explain in detail about the types of shift registers with neat sketch. (10)
- (ii) Compare Moore and Mealy circuits. (4)

25. a) (i) Design a Full Adder using a suitable PROM (6)
- (ii) Implement the given functions using PROM (16)  $F1 = \sum (0, 1, 3, 4, 6, 7)$   $F2 = \sum (1, 2, 3, 5)$  (8)

**(OR)**

- b) (i) Write short note on semiconductor memories. (6)
- (ii) Categorize RAM and ROM and explain in detail. (8)

\*\*\*\*\*