



GENERAL INSTRUCTIONS TO THE CANDIDATES

1. Candidates are instructed to answer the questions as per Bloom's Taxonomy knowledge level ( $K_1$  to  $K_6$ )
2. Candidates are strictly instructed not to write anything in the question paper other than their roll number.
3. Candidates should search their pockets, desks and benches and handover to the Hall Superintendent/ Invigilator if any paper, book or note which they may find therein as soon as they enter the examination hall.
4. Candidates are not permitted to bring electronic watches with memory, laptop computers, personal systems, walkie-talkie sets, paging devices, mobile phones, cameras, recording systems or any other gadget / device /object that would be of unfair assistance to him / her.
5. Corrective measures as per KCT examination policies will be imposed for malpractice in the hall like copying from any papers, books or notes and attempting to elicit the answer from neighbours.

**B.E DEGREE EXAMINATIONS: JUNE 2015**

(Regulation 2014)

Second Semester

**MECHATRONICS ENGINEERING**

U14MCT 201: Electronic Devices and Circuits

**Time: Three Hours**

**Maximum Marks: 100**

**Answer all the Questions:-**

**PART A (10 x 1 = 10 Marks)**

1. In a forward biased pn junction diode, the sequence of events that describes the mechanism of current flow is [K<sub>1</sub>]  
 1. Current flow      2. Injection      3. Recombination of minority carriers      4. Subsequent diffusion  
 a) 3-2-4-1      b) 2-3-4-1  
 c) 4-3-2-1      d) 2-4-3-1
2. What is true about the breakdown voltage in a Zener diode? [K<sub>1</sub>]  
 a) It decreases when current increases.      b) It destroys the diode.  
 c) It equals the current times the resistance.      d) It is approximately constant.
3. For the following circuit find the value of  $R_{TH}$  [K<sub>2</sub>]






20. What is a multivibrator? [K<sub>2</sub>]

**Answer any FIVE Questions:-  
PART C (5 x 14 = 70 Marks)  
(Answer not more than 300 words)**

**Q.No. 21 is Compulsory**

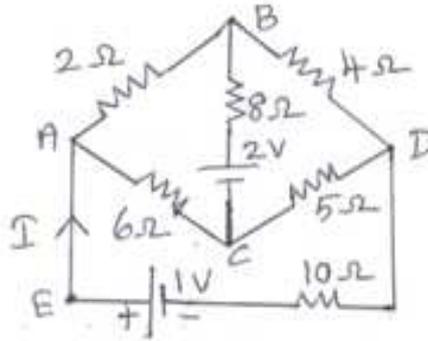
21. (i) Using Superposition theorem, obtain current EI in fig below. (12) [K<sub>3</sub>]



(ii) Define Diode dc resistance. (2) [K<sub>2</sub>]

22. (i) Discuss about the types of Clipper circuits. (7) [K<sub>2</sub>]

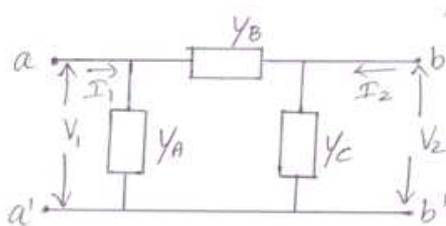(ii) Determine the Y parameters for the circuit shown in fig. (7) [K<sub>3</sub>]



23. (i) What are the essential conditions for transistor biasing? and describe about collector feedback biasing method. (10) [K<sub>2</sub>]

(ii) Draw the Characteristics of MOSFET. (4)

24. (i) Explain the function of the capacitor filter used in the rectifier. (7) [K<sub>2</sub>]

(ii) Explain how a Zener diode can be used as voltage regulator. (7)

25. (i) What are the important characteristics of a cascade amplifier? Write the circuit of cascade amplifier and determine an expression for its voltage gain in terms of its circuit parameters. (7) [K<sub>2</sub>]

(ii) Draw the circuit diagram of Colpitts oscillator and explain its working. (7)

26. (i) Explain how Op-amp acts as integrator and derive output voltage equation. (7) [K<sub>2</sub>]

(ii) Derive the expression for frequency of oscillation of RC Phase shift oscillator using Op-amp. (7)

\*\*\*\*\*