



M.E. DEGREE EXAMINATIONS: DEC 2015

(Regulation 2014)

Third Semester.

POWER ELECTRONICS AND DRIVES

P14PETE11: PWM Converters and Applications

Time: Three Hours

Maximum Marks: 100

Answer all the Questions:-

PART A (10 x 1 = 10 Marks)

1. Which is the correct sequence of converters starting from highest switching speed CO1 [K₂]
[A. DC-AC Inverter B. AC-DC converter C. DC-DC chopper
D. Step up Cycloconverter]
a) A-B-C-D b) A-C-D-B
c) B-D-C-A d) D-C-B-A
2. Line commutation is used in CO1 [K₂]
[A] Phase controlled rectifier [B] MOSFET chopper
[C] IGBT Inverter [D] TRIAC voltage controller
a) A and B b) B and C
c) B and D d) A and D
3. Reference for space vector PWM technique is CO2 [K₂]
a) Direct voltage b) Single phase alternating voltage
c) Three phase alternating voltage d) Two phase alternating voltage
4. A: Resonant converters have reduced losses; CO2 [K₂]
R: ZCS and ZVS have minimized switching losses
a) A and R are true and related b) A is true and R is not true
c) A is not true and R is true d) A and R are not true
5. Match the following CO1 [K₂]
[A. CSI, B. VSI, C. MLI],

- | | | |
|---|-----|-------------------|
| 17. State the effects of current ripples in inverter fed drives | CO2 | [K ₂] |
| 18. List the power factor correction techniques used for line side converters | CO3 | [K ₂] |
| 19. Identify the negative sequence harmonic components | CO3 | [K ₃] |
| 20. State the advantages of active filtering technique | CO3 | [K ₂] |

PART C (6 x 5 = 30 Marks)

- | | | |
|--|-----|-------------------|
| 21. Draw and Explain the operation of bridge inverter. | CO1 | [K ₂] |
| 22. Distinguish between VSI f and CSI | CO1 | [K ₃] |
| 23. Draw and explain the sine PWM technique. | CO2 | [K ₂] |
| 24. Describe the conduction and switching losses in PWM converters | CO2 | [K ₂] |
| 25. With block diagram, explain V/f control of induction motor drive | CO2 | [K ₂] |
| 26. How is the power factor improved in line side of converter? Describe a method. | CO3 | [K ₂] |

PART D (4 x 10 = 40 Marks)

- | | | |
|--|-----|-------------------|
| 27. With switching strategy, explain the space vector PWM technique | CO2 | [K ₂] |
| 28. Derive a dynamic model of PWM converter. | CO2 | [K ₃] |
| 29. Describe the estimation of current ripple and torque ripple in inverter fed drive. | CO2 | [K ₂] |
| 30. Draw and explain the principle of various types of active power filtering | CO3 | [K ₂] |
