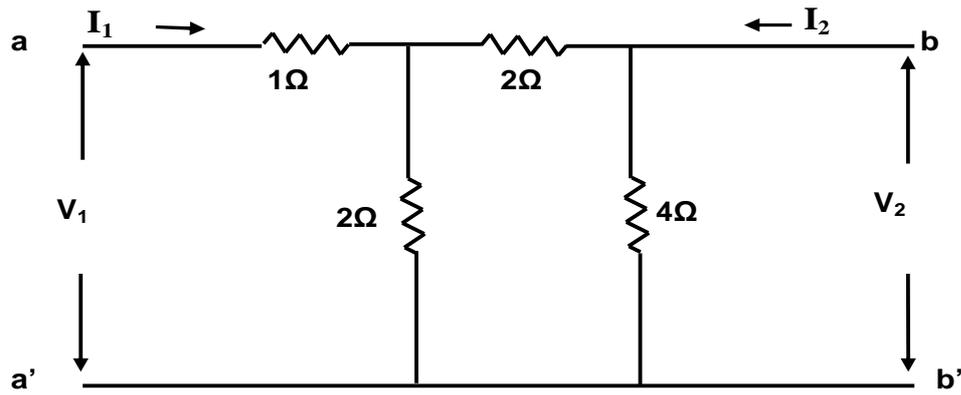
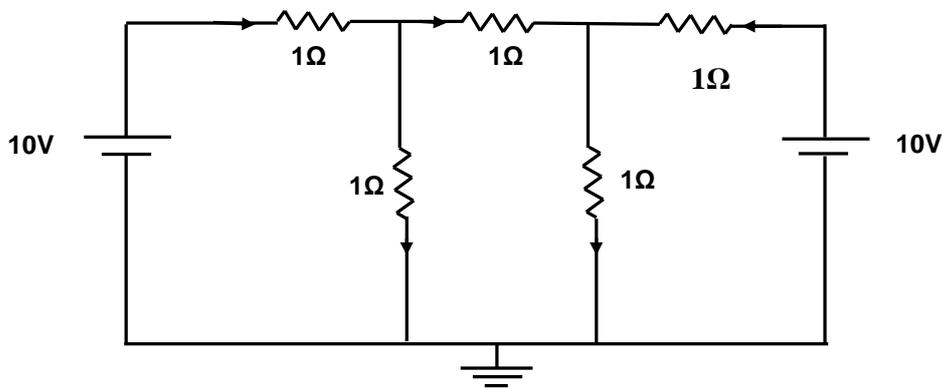


3. Time constant of series RC circuit is CO1 [K₁]
- a) $1/RC$ b) RC
 c) R/C d) C/R
4. When RL series circuit is connected to sinusoidal voltage source, the current changes in sequence from zero to [A. Peak value B. current at time constant C. steady state current] CO1 [K₂]
- a) A-B-C b) C-B-A
 c) B-A-C d) B-C-A
5. Match the following CO2 [K₂]
 [A. 'Z' parameter B. 'Y' parameter C. 'H' parameter D. 'ABCD' parameter];
 [1. Short circuit parameter 2. Transistor parameter 3. Transmission line parameter
 4. Open circuit parameter]
- a) A-2, B-1, C-3, D-4 b) A-3, B-4, C-1, D-2
 c) A-3, B-1, C-4, D-2 d) A-4, B-1, C-2, D-3
6. If the poles are repeated, then the function is said to be having _____ poles CO2 [K₂]
- a) Simple b) Dominant
 c) Multiple d) Finite
7. Match the following CO3 [K₂]
 [A. Series element of band pass filter B. Series element of band stop filter
 C. Series element of low pass filter D. Series element of high pass filter];
 [1. Inductor 2. Capacitor 3. Series combination of L and C 4. Parallel combination of L and C]
- a) A-2, B-1, C-3, D-4 b) A-3, B-4, C-1, D-2
 c) A-3, B-1, C-2, D-4 d) A-4, B-1, C-2, D-3
8. Assertion (A): In attenuator, the value of phase shift constant is zero CO3 [K₂]
 Reason (R): Attenuator is a pure resistive network.
- a) A&R are true and related b) A&R are true and not related
 c) A is true and R is false d) A is false and R is true
9. Functions with following property are called positive real functions CO3 [K₂]
 [A. Quotients, $P(s)$ and $Q(s)$ are real B. Poles and zeros lie in the left half of s-plane
 C. Poles and zeros lie in the right half of s-plane D. Poles and zeros are simple]
- a) A and C b) A, B and D
 c) C and D d) A, C and D
10. In RL network synthesis, the first Cauer form is obtained by the following sequence of process CO3 [K₂]
 [A. Removing the minimum real part of $Z(s)$ B. Removing pole at $s=0$
 C. Inverting the remaining function]



22. Determine the node voltages and loop currents for the given circuit using graph theory

CO1 [K₃]



23. Derive the expression for DC transient response of an RL series circuit. A series RL circuit with $R = 30 \Omega$ and $L = 15H$ has a constant voltage $V_S = 60 V$ applied at $t = 0$ by closing the switch. Determine the current, the voltage across the resistor and the voltage across inductor at $t = 0.5 \text{ sec}$.

CO1 [K₃]

24. Describe the properties of driving point functions and transfer functions.

CO2 [K₂]

25. Derive the equations for the design of constant K-High Pass Filter. Design and draw the T and π sections of a high pass filter having a cut-off frequency of 1 kHz with a load resistance of 600Ω .

CO3 [K₃]

26. The driving point impedance of a one port reactive network is given by

CO3 [K₃]

$$Z(S) = [5 (S^2+4) (S^2+25)] / [S (S^2+16)]$$

Obtain the first and second Foster networks.
