





19. Define cyclo converter. [K<sub>1</sub>]
20. Name the commutation techniques of thyristors used in cyclo converters. [K<sub>1</sub>]

**PART C (10 x 5 = 50 Marks)**

21. Derive an expression for average output voltage, RMS output voltage and displacement factor of a single phase fully controlled converter. [K<sub>2</sub>]
22. A single phase semi converter delivers power to RLE load with  $R=5\Omega$ ,  $L= 10\text{mH}$  and  $E=80\text{V}$ . For a continuous conduction, find the average value of output current for a firing angle delay of  $50^\circ$  and  $230\text{v}$ ,  $50\text{Hz}$  supply. [K<sub>3</sub>]
23. Draw the circuit diagram and output waveforms of three phase full converter for the firing angle of  $60^\circ$ . [K<sub>2</sub>]
24. Explain the Time Ratio Control of a DC chopper. [K<sub>2</sub>]
25. Draw the various types of zero current switch topologies. [K<sub>2</sub>]
26. A DC to DC chopper operates from a  $48\text{ V}$  battery source into a resistive load of  $240\Omega$ . The frequency of the chopper is set to  $250\text{Hz}$ . Determine the load power when on-time of the chopper is  $1\text{ ms}$ ? [K<sub>3</sub>]
27. Draw the possible configurations of single phase voltage controllers and compare them. [K<sub>2</sub>]
28. A single-phase full wave controller feeds power to a resistive load of  $100\ \Omega$  from a  $230\text{V}$ ,  $50\text{Hz}$  supply. Calculate the rms output voltage, input power factor and the half cycle average current at delay angles  $\alpha_1=\alpha_2=\alpha=90$  degree of both thyristors. [K<sub>3</sub>]
29. Derive the output voltage equation of a cyclo converter. [K<sub>2</sub>]
30. Explain the operation of single phase step down cyclo converter. [K<sub>2</sub>]

**PART D (2 x 10 = 20 Marks)**

31. With neat circuit and waveforms explain the working of single-phase dual converter. [K<sub>2</sub>]
32. Describe the operation of a three phase three wire AC voltage controller with neat power circuit and waveforms. [K<sub>2</sub>]

\*\*\*\*\*