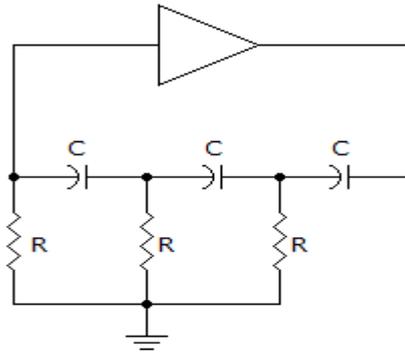





6. This circuit is a \_\_\_\_\_ oscillator.



7. A clipping circuit that clips the input at two identical levels during the positive and negative time periods is called a
- limiter
  - positive clipper
  - slicer
  - negative clipper
8. A Schmitt trigger is a comparator with \_\_\_\_\_ triggering points.
9. Which type of transformer is required to create a 180 degree input to a rectifier?
- center-tapped secondary
  - step-down secondary
  - stepped-up secondary
  - split winding primary
10. The dc current through each diode in a bridge rectifier equals \_\_\_\_\_ of the load current.

**PART B (10 x 2 = 20 Marks)**  
**(Not more than 40 words)**

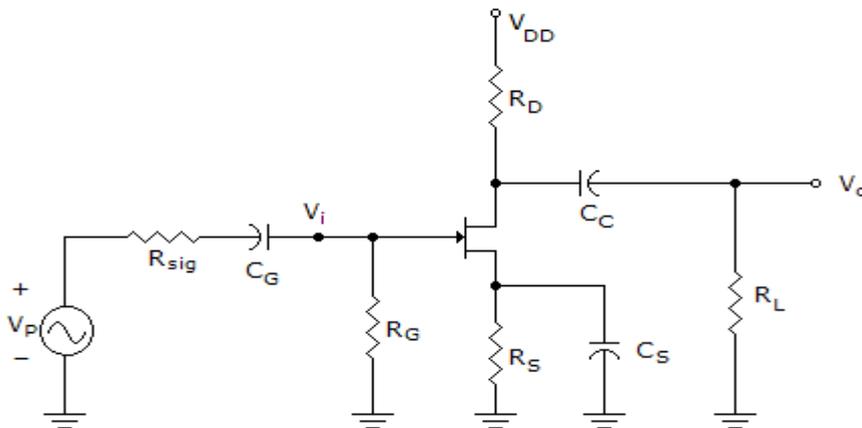
11. What are the advantages of negative feedback over positive feedback?
12. Determine the lower cutoff frequency of this network.



- |                                 |                                |                               |
|---------------------------------|--------------------------------|-------------------------------|
| $C_G = 100 \text{ pF}$          | $R_{sig} = 10 \text{ k}\Omega$ | $I_{DSS} = 8 \text{ mA}$      |
| $C_C = 0.5 \text{ }\mu\text{F}$ | $R_G = 1 \text{ m}\Omega$      | $V_p = -4 \text{ V}$          |
| $C_S = 2 \text{ }\mu\text{F}$   | $R_D = 4.7 \text{ k}\Omega$    | $r_d = \infty \text{ }\Omega$ |
|                                 | $R_S = 1 \text{ k}\Omega$      | $V_{DD} = 20 \text{ V}$       |
|                                 | $R_L = 2.2 \text{ k}\Omega$    |                               |

13. What are the Barkhausen criteria?
14. Draw a common collector amplifier and its equivalent circuit.
15. What is a synchronously tuned amplifier?
16. Define line regulation and load regulation of a voltage regulator.

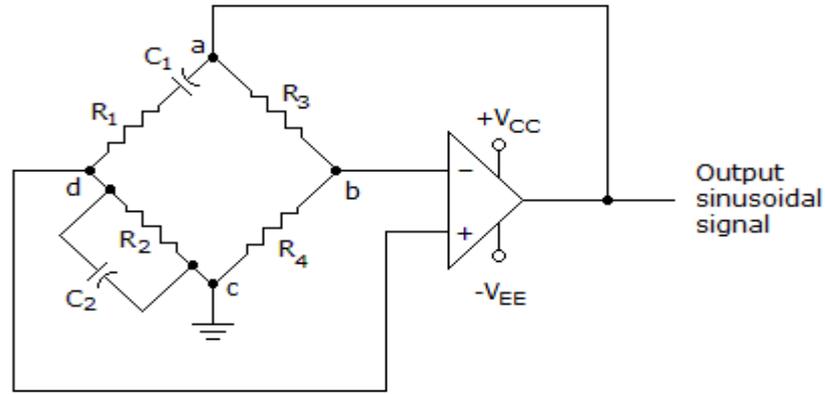17. Calculate the value of  $C_1 = C_2$  for the Wien bridge oscillator to operate at a frequency of 20 kHz. Assume  $R_1 = R_2 = 50 \text{ k}\Omega$  and  $R_3 = 3R_4 = 600 \Omega$ ?




18. Why are commutating capacitors used in bistable multivibrator?  
 19. Write notes on diode shunt clipper.  
 20. How can the linearity of current sweep generators be improved?

**PART C (5 x 14 = 70 Marks)**  
**(Not more than 400 words)**

**Q.No. 21 is Compulsory**

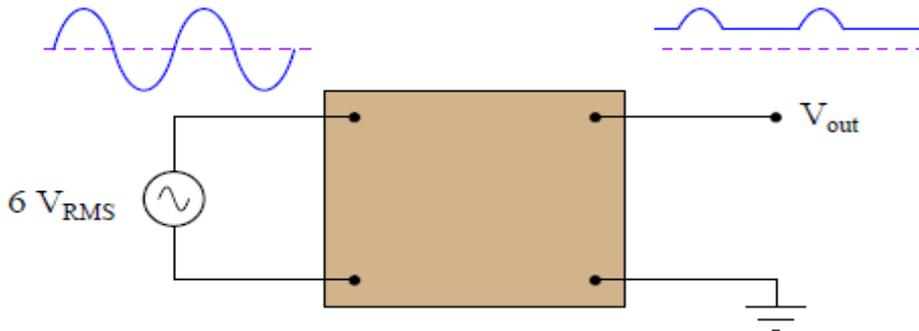21. (i) Design an electronic circuit to perform the following. (9)



- (ii) Give reason: Thermal runaway is of importance in BJT amplifier but not so in FET amplifier. (5)
22. a) Discuss and derive for the low frequency response of BJT in all the modes. (OR)  
 b) Draw and explain the two biasing circuit of JFET and also find Q point using mathematical and graphical methods.
23. a) Design a classAB push-pull large signal amplifiers as the interface stage between a signal generator and low impedance load. This large signal amplifiers should be capable of delivering a maximum of 1 watt 10 a100hm load. Use Fig 1 in the large signal amplifiers. Design constraints use TIP31 and TIP32 BJT transistors. Assume that the sinasoidar 1/D source has a source impedance of 500hm. Use a 10 0hm power resistor as the load to the large signal amplifiers. Use 20volt supply voltages.Use 1/P coupling capacitors to block DC.

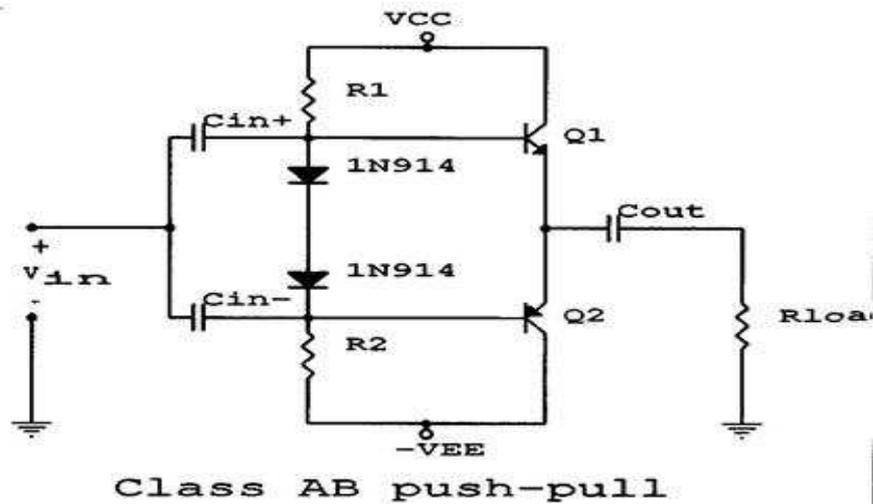


Fig.1

(OR)

- b) Discuss in details the biasing of Darlington amplifier in detail and also elaborate on DC and AC analyses.

24. a) Design the following negative feedback amplifier circuits with the available data.

(i) voltage-series (ii) voltage-shunt (iii) current-series feedback and (iv) current-shunt

Data given:  $A=100$ ,  $R_i=10\text{ K}\Omega$ ,  $R_O=20\text{ K}\Omega$  and  $\beta=0.1$ .

(OR)

- b) (i) Draw the circuit diagram of a pierce crystal oscillator and explain its operation. 4  
(ii) Draw the circuit diagram of Hartley Oscillator and explain its operation. Obtain 10 the expression for its frequency of oscillations.

25. a) Discuss in detail the following for a switched mode power supply

- (i) Working principle with circuit  
(ii) Applications

(OR)

- b) Design a full wave rectifier as dc power supply with a  $1\text{ k}\Omega$  load that operates from a  $120\text{ V}_{\text{rms}}$ ,  $60\text{ Hz}$  supply through a 10 to 1 step down transformer. The capacitor is connected to parallel to the load to provide the peak to peak ripple voltage of 2% of the peak output. The diodes have  $0.7\text{ V}$  turn on voltage.

- A) Draw a complete rectifier circuit to design.  
B) Specify the peak voltage that must appear across the transformer secondary.  
C) Find peak value of the rectified voltage across the load.  
D) Find average output voltage.  
E) Find required value of the filter capacitor  
F) Find required diode PIV rating.  
G) Calculate the peak diode current.

\*\*\*\*\*