



M.E DEGREE EXAMINATIONS:JUNE 2017

(Regulation 2015)

Second Semester

COMMUNICATION SYSTEMS

P15COTE14: RF System Design

COURSE OUTCOMES

CO1: Describe The various passive and active components for radio frequency circuits

CO2: Analyze micro strip line filters

CO3: Analyze the biasing methods for RF amplifiers

CO4: Compare the various RF oscillators for their performance.

CO5: Design matching networks using smith charts

Time: Three Hours

Maximum Marks: 100

Answer all the Questions:-

PART A (10 x 1 = 10 Marks)

1. Assertion (A):The transceiver is a RF system CO1 [K₄]
Reason (R):Since it has a transmitter and receiver
 - a) Both A and R are individually true and R is the correct explanation for A
 - b) A is true but R is false
 - c) Both A and R individually true but R is not correct explanation of A
 - d) A is false but R is true

2. The frequency range of Very high frequency is CO1 [K₂]
 - a) 300-3000 MHz
 - b) 3000-30000 MHz
 - c) 30-300 MHz
 - d) 3-30MHz

3. A type of Resonant filter is CO2 [K₂]
 - a) Butter worth filter
 - b) Active filter
 - c) Digital filter
 - d) Passive filter

4. Matching list I with list II and select the correct answer using the codes given below CO2 [K₃]
the list

List I	List II
A. Insertion loss IL	1 RF filter
B. Shape factor	2. elliptic filter

Answer any TWO Questions

PART D (2 x 10 = 20 Marks)

31. analyze a low pass filter and obtain $H(\omega)$ and $\alpha(\omega)$ and draw the attenuation profile of the low pass filter. CO2 [K₃]
32. Describe with figures and equations High frequency resistors, High frequency capacitors and high frequency inductors. CO1 [K₂]
33. Describe Stability considerations and Constant gain circles concepts in RF amplifier Design CO3 [K₂]
