



B.E/B.TECH DEGREE EXAMINATIONS: JUNE 2017

(Regulation 2015)

Second Semester

U15EET211: BASICS OF ELECTRICAL AND ELECTRONICS ENGINEERING

(Common to AE / ME / AUE / BIO)

COURSE OUTCOMES:

- CO1:** Acquire the basic knowledge of fundamental laws of circuit elements. (K2)
CO2: Define various magnetic field concepts. (K2)
CO3: Understand relationships among current, voltage and power in AC circuits. (K2)
CO4: Understand the characteristics of various electrical machines. (K2)
CO5: Understand the characteristics of basic electronic devices and their applications. (K2)
CO6: Verify the truth table of digital logic gates. (K2)

Time: Three Hours

Maximum Marks: 100

Answer all the Questions:-

PART A (10 x 1 = 10 Marks)

1. Match the following

CO1 [K₂]

List I	List II
A. Conductance	i. farad
B. Energy	ii. watts
C. Capacitance	iii. mho
D. Power	iv. joules

- | | A | B | C | D |
|----|-----|-----|-----|----|
| a) | iv | iii | ii | i |
| b) | iii | iv | i | ii |
| c) | ii | i | iii | iv |
| d) | i | iv | iii | ii |

2. Electrical appliances are connected in parallel because it

CO1 [K₂]

- | | |
|----------------------------------|--|
| a) is a simple circuit | b) draws less current |
| c) results in reduced power loss | d) makes the operation of appliances independent of each other |

PART B (10 x 2 = 20 Marks)
(Answer not more than 40 words)

- | | |
|--|-----------------------|
| 11. State Ohm's law. | CO1 [K ₂] |
| 12. List out the properties of series electric circuits. | CO1 [K ₂] |
| 13. A bar magnet whose length and width are 4m and 2m respectively. Its magnetic flux density is 0.12T. Find the magnetic flux produced. | CO2 [K ₂] |
| 14. Compare magnetic circuit with electric circuit. | CO2 [K ₂] |
| 15. Define RMS value. | CO3 [K ₂] |
| 16. An alternating current is given as $i(t) = 300\sin(157t + \pi/3)$. Find the maximum current and time period. | CO3 [K ₂] |
| 17. What is back emf? | CO4 [K ₂] |
| 18. Why transformers are rated in KVA? | CO4 [K ₂] |
| 19. Mention the applications of diodes. | CO5 [K ₂] |
| 20. Draw the logic diagram of EX-OR gate with its truth table. | CO6 [K ₂] |

Answer any FIVE Questions:-

PART C (5 x 14 = 70 Marks)
(Answer not more than 300 words)

Q.No. 21 is Compulsory

- | | |
|---|-----------------------|
| 21. Derive the capacitance of the parallel plates separated by
(i) Dielectric medium. (6)
(ii) Dielectric medium with partly air. (8) | CO1 [K ₂] |
| 22. (i) State and explain the laws of Electromagnetic induction. (7)
(ii) Discuss magnetic hysteresis with necessary diagram. (7) | CO2 [K ₂] |
| 23. Prove that Form factor of pure ac sinusoidal wave is 1.11. | CO3 [K ₂] |
| 24. i) Explain the construction and working principle of DC motor. (10)
ii) Compare squirrel cage and slip ring induction motor. (4) | CO4 [K ₂] |

25. (i) Explain the operation of PN junction diode with its V-I characteristics. (7) CO5 [K₂]
(ii) Discuss the characteristics of BJT in CE configuration. (7)
26. A 230V, 50Hz AC supply is applied to a series circuit having 2.5Ω resistance, 0.06H inductance and 6.8μF capacitance. Find (i) Impedance (ii) Current (iii) Phase angle (iv) Power factor (v) Power consumed. CO3 [K₂]
27. Illustrate and explain the working principle of Half wave and Full wave rectifier. CO5 [K₂]
