



**B.E / B.TECH DEGREE EXAMINATIONS: JUNE 2017**

(Regulation 2015)

Second Semester

**U15EET212 : ELECTRICAL AND ELECTRONIC CIRCUITS**

(Common to CSE / IT)

**COURSE OUTCOMES:**

- CO1:** Define & identify the basic electrical quantities and also able to calculate approximately the voltage, current parameters in DC circuits using basic laws.
- CO2:** Understand the phasor representation of various AC circuit parameters and acquire knowledge on fundamentals of three phase ac circuits.
- CO3:** Differentiate the various semiconductor diodes and rectifiers
- CO4:** Summarize the characteristics of different types of transistors
- CO5:** Apply the achieved basic knowledge about oscillators and op-amp to different dc applications.

**Time: Three Hours**

**Maximum Marks: 100**

**Answer all the Questions:-**

**PART A (10 x 1 = 10 Marks)**

1. Match the following CO1 [K<sub>2</sub>]
- |                |              |  |
|----------------|--------------|--|
| A. Resistance  | 1. Watt hour |  |
| B. Conductance | 2. Mho       |  |
| C. Energy      | 3. Ohm       |  |
- a) A-1, B-2, C-3 b) A-3, B-2, C-1
- c) A-3, B-1, C-2 d) A-2, B-3, C-1
2. Identify the element for which Ohm's Law is not applicable CO1 [K<sub>1</sub>]
- a) Iron box b) Motor winding
- c) Diode d) Incandescent bulb
3. Assertion (A): Power factor depends on the load. CO2 [K<sub>3</sub>]
- Reason (R): Active power consumption of the load is due to the resistance.
- a) A and R are true and related b) A is true and R is not true
- c) A is not true and R is true d) A and R are not true

4. For sinusoidal voltage, arrange the following in sequence of values with increasing order; CO2 [K<sub>2</sub>]  
 A. Average value B. RMS value C. Peak value
- a) B-C-A b) A-B-C  
 c) C-B-A d) B-A-C
5. Identify the devices operating in forward conduction mode CO3 [K<sub>2</sub>]  
 [A. Half wave rectifier B. Full wave rectifier C. Zener regulator]
- a) A and B b) A and C  
 c) B and C d) A and D
6. Assertion (A): The output ripple frequency of full wave rectifier is 100 Hz for the input CO3 [K<sub>2</sub>]  
 supply of 50 Hz.
- Reason (R): In full wave rectifier, both the half cycles appear in the output.
- a) A and R are true and related b) A is true and R is not true  
 c) A is not true and R is true d) A and R are not true
7. Identify the current controlled devices CO4 [K<sub>1</sub>]  
 A. MOSFET B. SCR C. BJT
- a) A and B b) A and C  
 c) B and C d) A and D
8. Match the following for transistors CO4 [K<sub>2</sub>]
- |                     |                             |
|---------------------|-----------------------------|
| A. CE configuration | 1. Impedance matching       |
| B. CB configuration | 2. Audio frequency circuits |
| C. CC configuration | 3. High frequency circuits  |
- a) A-2, B-3, C-1 b) A-1, B-3, C-2  
 c) A-3, B-2, C-1 d) A-3, B-1, C-2
9. \_\_\_\_\_ is operating as a source CO5 [K<sub>2</sub>]
- a) Amplifier b) Oscillator  
 c) Rectifier d) Comparator
10. Identify the correct sequence for increasing circuit complexity CO5 [K<sub>2</sub>]  
 [A. Transistor Amplifier B. Operational amplifier C. Integrator]
- a) B-C-A b) A-B-C  
 c) C-B-A d) B-A-C

**PART B (10 x 2 = 20 Marks)**

**(Answer not more than 40 words)**

11. Two resistors of  $2\Omega$  and  $4\Omega$  are connected in series to a battery of  $12V$ . Calculate the power consumed in  $4\Omega$  resistor CO1 [K<sub>3</sub>]
12. State Kirchhoff's current Law CO1 [K<sub>1</sub>]
13. Define RMS value of alternating voltage CO2 [K<sub>1</sub>]
14. Calculate the power factor of an AC circuit with a load of impedance,  $3+4j\Omega$  CO2 [K<sub>3</sub>]
15. Draw the V-I characteristics of PN junction diode CO3 [K<sub>2</sub>]
16. List the applications of optical diodes CO3 [K<sub>3</sub>]
17. What is meant by biasing of transistor? CO4 [K<sub>2</sub>]
18. Give examples for voltage controlled devices CO4 [K<sub>1</sub>]
19. Draw the circuit of LC feedback oscillator CO5 [K<sub>2</sub>]
20. State the applications of operational amplifiers CO5 [K<sub>3</sub>]


**Answer any FIVE Questions:-**

**PART C (5 x 14 = 70 Marks)**

**(Answer not more than 300 words)**

**Q.No. 21 is Compulsory**

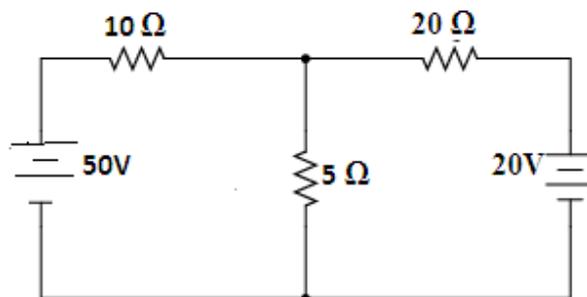21. (i) Two filament lamps of resistances  $100\Omega$  and  $200\Omega$  are connected in parallel and supplied from  $200V$  source. Calculate the power consumed by the  $100\Omega$  lamp. (10) CO1 [K<sub>3</sub>]  
(ii) Write the equations for three phase voltages (4) CO2 [K<sub>2</sub>]
22. Determine the current flowing through  $5\Omega$  resistor using loop current method. CO1 [K<sub>3</sub>]



23. Describe the resonance in series RLC circuit with relevant diagrams and equations CO2 [K<sub>2</sub>]
24. Draw the circuit of full wave rectifier and explain the operation with waveforms CO3 [K<sub>2</sub>]

- |     |   |      |     |                   |
|-----|---|------|-----|-------------------|
| 25. | (i) Describe common emitter amplifier with circuit diagram              | (10) | CO4 | [K <sub>2</sub> ] |
|     | (ii) Draw the structure of MOSFET                                       | (4)  | CO4 | [K <sub>2</sub> ] |
| 26. | (i) Draw the circuit and explain the operation of relaxation oscillator | (7)  | CO5 | [K <sub>2</sub> ] |
|     | (ii) Describe the operation of circuit and differentiator               | (7)  | CO5 | [K <sub>2</sub> ] |
| 27. | Compare   |      |     |                   |
|     | (i) Diode and SCR   | (7)  | CO3 | [K <sub>3</sub> ] |
|     | (ii) Amplifier and oscillator   | (7)  | CO5 |                   |

\*\*\*\*\*