



B.E DEGREE EXAMINATIONS: MAY 2017

(Regulation 2015)

Fourth Semester

ELECTRONICS AND INSTRUMENTATION ENGINEERING

U15EIT404 :Digital Fundamentals and Circuits

COURSE OUTCOMES

- CO1:** Comprehend the knowledge of numeration systems and logic families
CO2: Demonstrate an understanding of minimizing logic circuits using Boolean operations
CO3: Understand principles, operations and design combinational logic circuits
CO4: Describe the operating concepts of sequential logic circuits
CO5: Analyze and design Finite state machines and memories

Time: Three Hours

Maximum Marks: 100

Answer all the Questions:-

PART A (10 x 1 = 10 Marks)

1. Matching type item

CO1 [K₂]

List I	List II
A. The gates required to build a half adder	i. 100
B. Hexadecimal equivalent of 256_{10}	ii. $(1010\ 0011)_2$
C. Convert $A3_H$	iii. EX-OR gate and AND gate
D. Add $(1\ 0\ 1\ 0)_2$ and $(0\ 0\ 1\ 1)_2$	iv. 1101

- | | A | B | C | D |
|----|-----|----|-----|----|
| a) | ii | i | iii | iv |
| b) | iii | iv | ii | i |
| c) | ii | iv | iii | i |
| d) | iii | i | ii | iv |

2. MIN term M_0 is represented as

CO1 [K₁]

- | | |
|-------------------|---------------|
| a) $A' + B' + C'$ | b) $A.B.C$ |
| c) $A+B+C$ | d) $A'.B'.C'$ |

3. Boolean function of full adder is given by CO2 [K₁]
 1.) $S=A'B'C+A'BC'+AB'C'+ABC$
 2) $C=AB+BC+CA$
 3) $S=AB'C+A'BC'+AB'C'+ABC'$
 4) $C=AB+BC+CA$
 a) 1,3 b) 1,4
 c) 1,2 d) 2,3
4. A binary code in which a number changes from successive number by only one bit CO2 [K₂]
 a) Excess 3 Code b) Gray Code
 c) BCD Code d) Binary Code
5. With regard to a D latch, CO3 [K₂]
 Assertion (A): the Q output follows D input when clock enable is low
 Reason (R): the Q output follows D input when clock enable is high
 a) Both A and R are Individually true and R is the correct explanation of A b) Both A and R are Individually true but R is not the correct explanation of A
 c) A is true but R is false d) A is false but R is true
6. A Combinational circuit that converts 'n' number of input lines to a maximum of 2^n output lines is CO3 [K₁]
 a) Encoder b) Multiplexer
 c) Decoder d) Comparator
7. How is JK flip-flop is made to toggle when CO4 [K₁]
 1) J=1 and K=1
 2) J=1 and K=0
 3) J=0 and K=0
 4) J= 0 and K=1
 a) 2-3-4-1 b) 1-3-2-4
 c) 3-4-2-1 d) 4-1-3-2
8. EPROM contents can be erased by exposing it to CO5 [K₁]
 a) Ultraviolet rays b) Infrared rays
 c) Burst of microwaves d) Intense heat radiations
9. Assertion (A): In asynchronous two states can be changed simultaneously CO5 [K₂]
 Reason (R): In synchronous two states can be changed simultaneously
 a) Both A and R are Individually true and R is the correct explanation of A b) Both A and R are Individually true but R is not the correct explanation of A
 c) A is true but R is false d) A is false but R is true

10. 4 bit magnitude comparator has A = 1011, B= 1001 determine which output is true CO4 [K₁]
- a) A > B b) A=B
- c) A < B d) Understand

PART B (10 x 2 = 20 Marks)

(Answer not more than 40 words)

11. What is binary equivalent of decimal number (46)₁₀ CO1 [K₂]
12. Add the following numbers i) 11₂+11₂ ii) 110₂+100₂ CO1 [K₂]
13. Simplify the following Boolean expression into one literal. CO2 [K₃]
 $A'BC+BC+AC$
14. State De-Morgan's theorem. CO2 [K₂]
15. Construct a full adder circuit using two half adder circuits. CO3 [K₃]
16. Implement the following function using 8:1 multiplexer CO3 [K₃]
 $F(A,B,C,D) = \sum m(1,3,4,8,9,15)$
17. Compare asynchronous sequential circuit with synchronous sequential circuit CO4 [K₂]
18. What is static 1 Hazard and static 0 Hazard CO4 [K₂]
19. Draw the logic diagram of static RAM cell CO5 [K₂]
20. Draw the block diagram of PAL and PLA and compare the working of two. CO5 [K₃]

Answer any FIVE Questions:-

PART C (5 x 14 = 70 Marks)

(Answer not more than 300 words)

Q.No. 21 is Compulsory

21. i) Draw and Explain the block diagram of a 4-bit BCD adder to add the contents of two (10) CO3 [K₃]
 register
- ii) Implement the following function using only the NAND gates (4)
 $F = A(CD + B) + BC'$
22. i) Subtract (11100)₂ with (101011)₂ (7) CO1 [K₃]
- ii) Implement the following function using NOR gate. (7)
 $Y = (A+C)(A+D')(A+B+C)$
23. Minimize the given terms using $F(a,b,c,d) = \sum m(0,1,2,5,6,7,8,9,10,14)$ CO2 [K₄]


24. i) Express the Boolean function $F = XY + X'Z$ as POS and realize with NOR gate. (7) CO2 [K₄]

ii) Convert the following function to Canonical POS. (7)

$$F(X,Y,Z) = (X'+Y)(X'+Z)$$

25. Draw and Explain the block diagram of a 4-bit parallel adder / subtractor to add the contents of two register CO3 [K₃]

 26. Analysis the following sequential circuit and obtain the state diagram for the same as shown in Figure 1 CO4 [K₄]



27. i) A combinational circuit is defined by the functions. (8) CO5 [K₄]
 $F1 = \sum m(3,5,7), F2 = \sum m(4,5,7)$. Implement the circuit with a PLA having 3 inputs, 3 product term and 2 output term.

ii) Using eight 64X8 ROM chips with an enable input and a decoder, construct a 512X8 ROM (6)
