



B.E DEGREE EXAMINATIONS: MAY 2017

(Regulation 2015)

Fourth Semester

MECHATRONICS ENGINEERING

U15MCT404: Digital Electronics and Microprocessor

COURSE OUTCOMES

- CO1:** Use number systems, Boolean algebra and explain various digital logic families.
CO2: Apply basic logic gates to form simple circuits and can simplify logic circuits using K- Map technique.
CO3: Design combinational logic circuits using logic Gates and explain simple memory systems.
CO4: Design flip flops and realize one flip flop using the other.
CO5: Design counters and construct their timing diagrams.
CO6: Explain the architecture of 8085 microprocessor and their peripheral ICs (8255, 8279 and 8251 A).
CO7: Write assembly language program for 8085 for the given application.
CO8: Explain the memory Mapping and I/O devices.

Time: Three Hours

Maximum Marks: 100

Answer all the Questions:-

PART A (10 x 1 = 10 Marks)

1. Matching type item with multiple choice code

CO1 [K₂]

| List I | | List II | |
|----------------------|--|------------|--|
| A. $(122)_8$ | | i. 1808 | |
| B. $(4AEF8)_{16}$ | | ii. 1414 | |
| C. $(10110000110)_2$ | | iii. 82 | |
| D. $(3420)_8$ | | iv. 306936 | |

- | | A | B | C | D |
|----|-----|----|-----|----|
| a) | ii | i | iii | iv |
| b) | iii | iv | ii | i |
| c) | ii | iv | iii | i |
| d) | iii | i | ii | Iv |

2. A group of 4 adjacent 1's in a K-map is called CO2 [K₁]
a) Nibble b) Quad
c) Octet d) Pairs
3. Indicate which of the following logic gates can be used to realize all possible combinational logic functions CO3 [K₂]
1. OR Gates only
2. NAND gates only
3. EX-OR gates only
4. NOR gates only
a) 1,3 b) 1,4
c) 1,2 d) 2,4
4. How many Flip-Flop are required for mod-16 counter CO4 [K₂]
a) 5 b) 6
c) 3 d) 4
5. Assertion (A): State machine is a synchronous circuit CO5 [K₂]
Reason (R): In Moore machine, the output is a function of present state
a) Both A and R are Individually true and R is the correct explanation of A b) Both A and R are Individually true but R is not the correct explanation of A
c) A is true but R is false d) A is false but R is true
6. The 8279 programmable keyboard / display interface is CO6 [K₁]
a) 40 Pin Device b) 20 Pin Device
c) 30 Pin Device d) 45 Pin Device
7. There are different types of memory CO8 [K₂]
1. RAM
2. ROM
3. PROM
4. EEPROM
Order in terms of number of switches used in construction of these memories.
a) 2-3-4-1 b) 1-3-2-4
c) 3-4-2-1 d) 4-1-3-2
8. MVI C,50 belongs to _____ addressing mode CO7 [K₁]
a) Immediate b) Direct
c) Implied d) Register Indirect

9. Assertion (A): Microprocessor places the 16 bit address on the address bus CO8 [K₂]
Reason (R): Microprocessor sends a pulse called Memory Read as the control signal
- a) Both A and R are Individually true and R is the correct explanation of A b) Both A and R are Individually true but R is not the correct explanation of A
c) A is true but R is false d) A is false but R is true
10. When a subroutine is called, the address of the instruction following the CALL instruction is stored in the CO7 [K₂]
- a) Stack Pointer b) Accumulator
c) Program Counter d) Stack

PART B (10 x 2 = 20 Marks)

(Answer not more than 40 words)

11. Subtract 1101101 from 10110 using 1's complement CO1 [K₂]
12. List down rules of simplification for karnaugh maps. CO2 [K₁]
13. List out the classification of combinational logic. CO3 [K₁]
14. How is a J-K flip-flop made to toggle? CO4 [K₃]
15. Draw a typical 3 bit ripple counter's state diagram. CO5 [K₁]
16. List the functions performed by 8255 Chip. CO6 [K₁]
17. Compare CALL and PUSH instruction. CO7 [K₂]
18. Write an assembly language program to add two numbers of 8 bit length. CO7 [K₃]
19. What is meant by address mapping? CO8 [K₂]
20. List the I/O mode in 8255. CO6 [K₂]

Answer any FIVE Questions:-

PART C (5 x 14 = 70 Marks)

(Answer not more than 300 words)

Q.No. 21 is Compulsory

21. a. Perform the subtraction of 101010 - 1111 using 2's complement (4) CO1 [K₃]
b. convert each pair of decimal number to BCD and add (10) CO1 [K₃]
- i)(65)₁₀ +(58)₁₀
ii)(113)₁₀+(101)₁₀

22. Using k-map method obtain the minimal SOP and POS expressions for the function (14) CO2 [K₂]
 $F(x,y,z,w) = \sum (1,3,4,5,6,7,9,12,13)$
23. Design and construct a 4-bit carry look ahead adder. (14) CO3 [K₃]
24. i) Realize D flip flop using SR flip flop (4) CO4 [K₂]
ii) Explain the construction of clocked SR flip flop with truth table. (10) CO4 [K₃]
25. Design and construct a asynchronous decade counter. Implement the design using JK flip-flop CO5 [K₃]
26. Explain the architecture of 8085 with block diagram CO6 [K₂]
27. Interface two numbers of 16 KB EPROM and one number of 8 KB RAM with 8085 microprocessor using memory mapped I/O. CO8 [K₃]
