



4. Match List I with List II

CO2 [K<sub>2</sub>]

List I	List II
A. The input impedance of common source stage	1. The input device and cascode device need not be of the same type
B. Folded cascode structure	2. a property of cascode structure
C. A high output impedance is	3. Large signal behaviour
D. Input –output characteristics of amplifier	4. $Z_{in} = 1 / [ C_{GS} + (1 + g_m R_D) C_{GD} ] s$

- |    | A   | B  | C   | D  |
|----|-----|----|-----|----|
| a) | ii  | i  | iii | iv |
| b) | iii | iv | ii  | i  |
| c) | ii  | iv | iii | i  |
| d) | iii | i  | ii  | iv |

5. Assertion (A): Less feedback is applied so that gain crossover moves closer to origin CO4 [K<sub>2</sub>]

Reason (R): The gain crossover must occur well before the phase crossover for stable system

- |   |   |
|---|---|
| a) Both A and R are Individually true and R is the correct explanation of A | b) Both A and R are Individually true but R is not the correct explanation of A |
| c) A is true but R is false   | d) A is false but R is true   |

6. The current voltage feedback network CO3 [K<sub>2</sub>]

- |  |   |
|--|---|
| a) Samples the output voltage and returns the feedback signal as voltage | Senses the output current and returns voltage |
| c) Senses the output voltage and returns current                         | Senses the output current and returns current |

7. The stability of a feedback system is dependent on CO3 [K<sub>2</sub>]

1. Number of poles in the system
2. Number of stages in the system
3. Number of devices used in the system
4. Load condition.

- |        |        |
|--------|--------|
| a) 1,3 | b) 1,4 |
| c) 1,2 | d) 2,3 |

8. Assertion: The op amp topology with differential output doesn't suffer in terms of stability of feedback system CO4 [K<sub>3</sub>]  
Reason: The differential output topology has a mirror pole.
- a) Both A and R are Individually true and R is the correct explanation of A      b) Both A and R are Individually true but R is not the correct explanation of A
- c) A is true but R is false      d) A is false but R is true
9. The quantity that play an important role in feedback system making the closed loop gain insensitive to variations in device parameters is ----- CO3 [K<sub>2</sub>]
- a) bandwidth      Loop gain  $A\beta$
- c) Terminal impedance      Pole frequency
10. Determination of transfer function for analyzing frequency response of an amplifier involves CO4 [K<sub>2</sub>]
1. Identify all of the capacitance in the circuit
  2. Fixing appropriate nodes in the circuit
  3. Surmise the transfer function
  4. Associating one pole with each node
- a) 2-3-4-1      b) 2-1-4-3
- c) 3-4-2-1      d) 4-1-3-2

**PART B (10 x 2 = 20 Marks)**

11. How do we generate copies of reference current which does not allow dependencies on process and temperature? Justify. CO1 [K<sub>4</sub>]
12. Write the significance of bandgap voltage reference. CO1 [K<sub>2</sub>]
13. Draw the small signal equivalent circuit of source follower and write the expression for voltage gain. CO2 [K<sub>2</sub>]
14. Compute the zero  $S_Z$  which arises from the direct coupling of the input to the output through  $C_{GD}$  in CS stage with help of suitable circuit. CO2 [K<sub>3</sub>]
15. List the types of noise and its effect on analog circuits. CO2 [K<sub>2</sub>]
16. Draw the simple implementations of four types of feedback amplifiers. CO3 [K<sub>2</sub>]
17. Write the expression for the input referred noise voltage per unit bandwidth of telescopic op-amp. CO3 [K<sub>2</sub>]
18. What are the advantages of folded cascade operational amplifier. CO4 [K<sub>2</sub>]
19. What are the two approaches to be followed in order to achieve stability in operational amplifier. CO4 [K<sub>2</sub>]
20. Write the significance of pole splitting and zero cancellation in two stage op amp. CO4 [K<sub>2</sub>]

**PART C (6 x 5 = 30 Marks)**

- |   |     |                   |
|---|-----|-------------------|
| 21. Discuss on constant $G_m$ biasing.  | CO1 | [K <sub>2</sub> ] |
| 22. With schematic and expressions explain MOS cascode current mirror.  | CO1 | [K <sub>2</sub> ] |
| 23. For common gate stage calculate the input impedance and write why $Z_{in}$ becomes independent of $C_L$ as capacitance increases. | CO2 | [K <sub>3</sub> ] |
| 24. State Millers theorem and illustrate how it can be applied to a circuit with an Example.  | CO3 | [K <sub>2</sub> ] |
| 25. Illustrate the technique for eliminating or moving right half plane zero in two stage CMOS op amp.                                | CO3 | [K <sub>3</sub> ] |
| 26. Discuss the concepts of gain and phase margins with respect to stability.   | CO4 | [K <sub>3</sub> ] |

**Answer any FOUR Questions**

**PART D (4 x 10 = 40 Marks)**

- |  |     |                   |
|--|-----|-------------------|
| 27. Design a self-biased $V_{BE}$ referenced bias circuit with necessary diagrams and test the supply independence of output currents. | CO1 | [K <sub>3</sub> ] |
| 28. Discuss the high frequency behavior of Differential amplifier with active current source load.                                     | CO2 | [K <sub>2</sub> ] |
| 29. Analyze the telescopic op- amp with circuit schematic and estimate the relative position of the poles.                             | CO3 | [K <sub>2</sub> ] |
| 30. i) Discuss the noise models of the various integrated circuit components. (4)  | CO2 | [K <sub>2</sub> ] |
| ii) Analyze the slewing characteristics of two stage operational amplifier circuit. (6)  | CO3 | [K <sub>2</sub> ] |
| 31. Explain & Analyze the Miller frequency compensation technique for two stage operational amplifier in detail.                       | CO4 | [K <sub>2</sub> ] |

\*\*\*\*\*