



B.E DEGREE EXAMINATIONS: MAY 2018

(Regulation 2015)

Fourth Semester

MECHATRONICS

U15MCT404: Digital Electronics and Microprocessor

COURSE OUTCOMES

- CO1:** Use number systems, Boolean algebra and explain various digital logic families
- CO2:** Apply basic logic gates to form simple circuits and can simplify logic circuits using K- Map technique
- CO3:** Design combinational logic circuits using logic Gates and explain simple memory systems.
- CO4:** Design flip flops and realize one flip flop using the other.
- CO5:** Design counters and construct their timing diagrams.
- CO6:** Explain the architecture of 8085 microprocessor and their peripheral ICs (8255, 8279 and 8251 A).
- CO7:** Write assembly language program for 8085 for the given application
- CO8:** Explain the memory Mapping and I/O devices.

Time: Three Hours

Maximum Marks: 100

Answer all the Questions:-

PART A (10 x 1 = 10 Marks)

1. Matching type item with multiple choice code

CO1 [K₂]

List I		List II	
A. $(X + Y)(X + Z)$		i. $(231)_8$	
B. $(153)_{10}$		ii. $(734)_8$	
C. $(1DC)_{16}$		iii. $X+YZ$	
D. $X + (Y + Z)$		iv. $(X + Y) + Z$	

- | | A | B | C | D |
|----|-----|----|-----|----|
| a) | ii | i | iii | iv |
| b) | iii | iv | ii | i |
| c) | ii | iv | iii | i |
| d) | iii | i | ii | iv |

2. The digital logic family which has minimum power dissipation is CO1 [K₂]
- a) TTL b) DTL
c) RTL d) CMOS

3. Consider the following registers: CO6 [K₂]
1. Accumulator and flag register
 2. B and C register
 3. D and E register
 4. H and L register

Which of these 8-bit registers of 8085 microprocessor can be paired together to make a 16-bit register?

- a) 1,2,3 b) 3,4
c) 2,3,4 d) 1,2,3

4. If $F(A, B, C) = \Sigma(1,3,5)$, then $\bar{F}(A, B, C)$ CO2 [K₂]
- a) $\Pi(1,3,5)$ b) $\Pi(0,2,4,6,7)$
c) $\Sigma(1,3,5)$ d) $\Sigma(0,2,4,6,7)$

5. Assertion (A): A flip-flop or latch is a circuit that has two stable states CO5 [K₂]
Reason (R): A flip-flop is a device which stores a single bit of data
- a) Both A and R are Individually true and R is the correct explanation of A b) Both A and R are Individually true but R is not the correct explanation of A
c) A is true but R is false d) A is false but R is true

6. For JK flipflop $J = 0, K=1$, the output after clock pulse will be CO4 [K₂]
- a) no change b) high impedance
c) 1 d) 0

7. Consider the following statements. CO3 [K₂]
1. State the problem.
 2. Assign letter symbols for input and output variable.
 3. Obtain simplified Boolean function for each output and draw the logic circuit.
 4. Determine the input variables and required output variables.
 5. Draw the truth table that defines the required relation between inputs and outputs.

Answer any FIVE Questions:-
PART C (5 x 14 = 70 Marks)
(Answer not more than 300 words)

Q.No. 21 is Compulsory

21. a) Obtain minimal expression for the following function and implement it in Universal logic CO2 [K₂]
 $F = \sum m(0,1,9,15,24,29,30) + d(8,11,31)$
22. Design a combinational circuit to convert Binary number to gray code. CO3 [K₂]
23. i) Design a half subtractor. (4) CO3 [K₂]
ii) Implement the function $F(A,B,C,D) = \sum m(0,1,3,4,8,9,15)$ using 8 to 1 multiplexer. (10)
24. i) Design a circuit to Convert JK flip flop into D flip flop. (10) CO4 [K₂]
ii) Write an assembly language program to subtract the contents of memory location 4001H from the memory location 4000H and place the result in memory location 4200H. (4) CO7 [K₂]
25. Design a 3 bit synchronous up counter. CO5 [K₂]
26. Elucidate the architecture of 8085 microprocessor. CO6 [K₂]
27. Interface two numbers of 8KB EPROM and one number of 4KB RAM with 8085 Microprocessor. Explain the interface diagram and allocate binary addresses to memory ICs. CO8 [K₃]
