



B.E DEGREE EXAMINATIONS: MAY 2018

(Regulation 2015)

Fifth Semester

ELECTRICAL AND ELECTRONICS ENGINEERING

U15EET502: Power Electronics

COURSE OUTCOMES

- CO1:** Describe the structure, operation and characteristics of power semi conductor devices.
CO2: Choose the protection and drives circuit for power electronic devices.
CO3: Illustrate the circuit and modes of operation of power converters.
CO4: Analyze the performance parameters of power converters.
CO5: Describe the voltage control and harmonic control strategies for power converters.
CO6: Select the power converter for specific applications.

Time: Three Hours

Maximum Marks: 100

Answer all the Questions:-

PART A (10 x 1 = 10 Marks)

1. Matching type item with multiple choice code

CO1 [K₂]

Type of Device	Characteristics
A. BJT	i. High Power
B. MOSFET	ii . Current Controlled device
C. IGBT	iii. Voltage Controlled device
D. SCR	iv. High Cost

- | | A | B | C | D |
|----|-----|-----|-----|----|
| a) | ii | i | iii | iv |
| b) | iii | iv | ii | i |
| c) | ii | iii | iv | i |
| d) | iii | i | ii | iv |

2. The converter that is suitable for four quadrant operation is

CO6 [K₁]

- | | |
|-------------------|--------------------------------|
| a) Full converter | b) Semi converter |
| c) Dual Converter | d) SCR phase control converter |

3. In which of the following devices the secondary breakdown does not occurs CO1 [K₂]
- | | | |
|-------|----------|--------|
| 1.BJT | 2.MOSFET | 3.IGBT |
|-------|----------|--------|
- a) 1,3 b) 1,4
- c) 1,2 d) 2,3
4. Which device has low conduction loss CO2 [K₁]
- a) BJT b) IGBT
- c) MOSFET d) SCR
5. Assertion : MOSFET is a Voltage controlled device CO2 [K₂]
Reason: It is because MOSFET has high Input Impedance
- a) Both A and R are Individually true and R is the correct explanation of A b) Both A and R are Individually true but R is not the correct explanation of A
- c) A is true but R is false d) A is false but R is true
6. For an SCR , dv/dt protection is achieved the use of ____ in ____ with SCR CO2 [K₂]
- a) RL, series b) RC, Parallel
- c) L, Series d) L, Parallel
7. Arrange the following devices from less to high switching loss CO1 [K₂]
- | | | |
|--------|----------|--------|
| 1. BJT | 2.MOSFET | 3.IGBT |
|--------|----------|--------|
- a) 1-2-3 b) 1-3-2
- c) 3-2-1 d) 2-3-1
8. If holding current of a SCR is 2 mA then latching current should be CO4 [K₂]
- a) 0.01 A b) 0.002 A
- c) 0.009 A d) 0.02
9. Assertion (A):Cycloconveters can be used for Induction motor speed control CO6 [K₂]
Reason (R): Variable Frequency output is not possible in Cycloconverters
- a) Both A and R are Individually true and R is the correct explanation of A b) Both A and R are Individually true but R is not the correct explanation of A
- c) A is true but R is false d) A is false but R is true
10. Which power electronic circuit is used for DC to DC conversion CO3 [K₁]
- a) Chopper b) Converter
- c) Inverter d) Cycloconverter

PART B (10 x 2 = 20 Marks)
(Answer not more than 40 words)

- | | | |
|---|-----|-------------------|
| 11. Distinguish between latching and holding current in SCR. | CO1 | [K ₂] |
| 12. What is need for Electrical isolation? What are types of Isolation Circuits? | CO2 | [K ₂] |
| 13. Define Displacement factor. | CO4 | [K ₁] |
| 14. How rectification and inversion are possible in phase controlled thyristor converter? | CO5 | [K ₂] |
| 15. Differentiate between constant and variable frequency control strategies in Choppers. | CO5 | [K ₂] |
| 16. What is duty cycle in DC choppers? | CO6 | [K ₂] |
| 17. Differentiate between VSI and CSI. | CO5 | [K ₁] |
| 18. List the different methods of controlling the output voltage in inverters. | CO3 | [K ₁] |
| 19. What is the difference between on line and offline UPS? | CO6 | [K ₂] |
| 20. Give some applications of Cycloconverters. | CO6 | [K ₁] |

Answer any FIVE Questions:-

PART C (5 x 14 = 70 Marks)
(Answer not more than 300 words)

Q.No. 21 is Compulsory

- | | | |
|--|-----|-------------------|
| 21. Explain the operation of 3 Φ full converter and draw the waveforms of output voltage, source current, load current and firing pulses for firing angle 60° | CO3 | [K ₂] |
| 22. Draw the basic structure of IGBT and explain its switching characteristics. | CO1 | [K ₂] |
| 23. With necessary circuit and waveforms explain the principle of operation of 1 Φ Full Converter with RL load in continuous conduction mode. Derive the expressions for V_{DC} and V_{RMS} for R load. | CO4 | [K ₃] |
| 24. Explain the working of Step up chopper with circuit and waveforms. Derive the expression for average output voltage. | CO3 | [K ₃] |
| 25. Explain Various pulse width modulation techniques used to control the output voltage of inverters. | CO5 | [K ₂] |
| 26. With neat sketches explain the operation of Step down Cycloconverter. | CO6 | [K ₂] |
| 27. Explain with neat diagrams and waveforms, three phase voltage source inverter in 180° conduction mode. Also obtain the expression for RMS value of output voltage. | CO5 | [K ₂] |
