



**B.E DEGREE EXAMINATIONS: NOV/DEC 2022**

(Regulation 2018)

Third Semester

**ELECTRICAL AND ELECTRONICS ENGINEERING**

U18EEI3203T: Analog Electronics and Linear Integrated Circuits

**COURSE OUTCOMES**

- CO1:** Understand the characteristics and applications of various semiconductor devices.  
**CO2:** Gain knowledge about small signal analysis of BJT and FET amplifiers.  
**CO3:** Analyze large signal amplifier and oscillator circuits.  
**CO4:** Design and analyze the linear applications of Op-amp and Familiarize with the concept of IC based voltage regulator and signal conversion circuits  
**CO5:** Apply the knowledge of semiconductor devices to design analog circuits for various applications using simulation software tools and hardware.

**Time: Three Hours**

**Maximum Marks: 100**

**Answer all the Questions:-**

**PART A (10 x 2 = 20 Marks)**

**(Answer not more than 40 words)**

- |   |     |                   |
|---|-----|-------------------|
| 1. Classify Field Effect transistor.                              | CO1 | [K <sub>2</sub> ] |
| 2. Draw the VI characteristics of Zener diode.                    | CO1 | [K <sub>2</sub> ] |
| 3. What is the need for biasing a Transistor?                     | CO2 | [K <sub>2</sub> ] |
| 4. Draw the Voltage divider bias circuit for Transistor.          | CO2 | [K <sub>2</sub> ] |
| 5. Classify Large signal amplifiers.                              | CO3 | [K <sub>2</sub> ] |
| 6. List the advantages of Negative feedback in amplifier circuit. | CO3 | [K <sub>2</sub> ] |
| 7. Compare Inverting and Non-inverting Amplifier.                 | CO4 | [K <sub>2</sub> ] |
| 8. What is common mode rejection ratio?                           | CO4 | [K <sub>2</sub> ] |
| 9. Draw the pin diagram of IC 555.                                | CO5 | [K <sub>2</sub> ] |
| 10. List the applications of LM 317 IC.                           | CO5 | [K <sub>2</sub> ] |

**Answer any FIVE Questions:-**

**PART B (5 x 16 = 80 Marks)**

**(Answer not more than 400 words)**

- |  |    |     |                   |
|--|----|-----|-------------------|
| 11. a) With neat diagram explain full wave rectifier with necessary wave form. | 16 | CO1 | [K <sub>2</sub> ] |
| 12. a) Draw and explain hybrid model of CE amplifier with necessary Equation.  | 16 | CO2 | [K <sub>3</sub> ] |

- 13. a) With neat explain the operation of RC phase shift oscillator with necessary wave form and equations. 16 CO3 [K<sub>2</sub>]
- 14. a) Construct op-amplifier based instrumentational amplifier and explain its operation. 16 CO4 [K<sub>2</sub>]
- 15. a) Draw the functional block of Astable multivibrator and draw the VI characteristics along with their application. 16 CO5 [K<sub>2</sub>]
- 16. a) Explain the principle of operation for JFET and draw the V-I characteristics. 16 CO1 [K<sub>2</sub>]

\*\*\*\*\*