



M.E DEGREE EXAMINATIONS: DEC 2022

(Regulation 2018)

First Semester

EMBEDDED SYSTEMS TECHNOLOGIES

P18EST1001: Advanced Digital System Design

COURSE OUTCOMES

After successful completion of this course, the students should be able to:

- CO1:** Apply the Design procedure of Clocked synchronous and asynchronous sequential circuits for developing simple digital system
- CO2:** Analyze the Clocked synchronous sequential circuits and asynchronous sequential circuits in digital system
- CO3:** Understand the basic and advanced concepts in testing of digital circuits
- CO4:** Apply the techniques to design synchronous sequential circuit using programmable devices
- CO5:** Familiarize basics and programming of VHDL for digital circuit design

Time: Three Hours

Maximum Marks: 100

Answer all the Questions:-

PART A (10 x 1 = 10 Marks)

1. Find the correct sequence for analysis of synchronous sequential circuit: CO1 [K₂]
 1. State diagram
 2. State table
 3. Equations for the outputs and the flip-flop inputs.
 4. Circuit diagram

a) 4-2-3-1	b) 2-1-3-4
c) 1-2-3-4	d) 4-3-2-1

2. Reduced state table with 7 states require _____ flip flops to design state machine. CO1 [K₂]

a) 7	b) 8
c) 3	d) 4

3. Hazard is due to CO2 [K₂]

a) Unequal delay	b) Transitions in the circuit
c) AND gate	d) NOR gate

4. Matching type item with multiple choice code

CO3 [K₂]

List I	List II
A. Asynchronous Sequential Machine	i. input and state
B. Synchronous sequential circuit	ii. input
C. Mealy circuit	iii. Fundamental mode operation
D. Moore circuit	iv. Flip Flop required

- a) A-i; B-ii; C-iii; D-iv b) A-iii; B-iv; C-i; D-ii
c) A-iv; B-ii; C-iii; D-i d) A-iii; B-ii; C-i; D-iv

5. _____ is not fault type.

CO3 [K₂]

- a) s-a-0 b) s-a-1
c) bridging d) Weak wire

6. BIST stands for

CO3 [K₂]

- a) Built In Self Test b) Built In Stuck at Test
c) Bridge In Self Test d) Bridge In Stuck at Test

7. Assertion (A): FPGA is programmable device.
Reason (R): VHDL can be used to program the FPGA.

CO4 [K₂]

- a) Both A and R are Individually true and R is correct explanation of A b) Both A and R are Individually true and R is not correct explanation of A
c) A is true but R is false d) A is false but R is true

8. Programmable AND & Programmable OR used in _____.

CO4 [K₂]

- a) CPLD b) FPGA
c) PLA d) PAL

9. Find the correct statement:

CO5 [K₂]

- VHDL is Hardware Description language
- <= is signal assignment operator
- Process is sequential statement
- VHDL is non-IEEE standard language

- a) 1 and 2 only b) 1 and 3 only
c) 1, 2 and 4 only d) 3 and 4 only

10. In VHDL, _____ is used in process statement.

CO5 [K₃]


- a) entity b) architecture
c) Sensitivity list d) Event list

PART B (10 x 2 = 20 Marks)

- | | |
|--|-----------------------|
| 11. Draw a sample of state diagram. | CO1 [K ₂] |
| 12. Justify the need for state table reduction. | CO1 [K ₄] |
| 13. Write the importance of fundamental mode in Asynchronous sequential circuit. | CO2 [K ₁] |
| 14. Differentiate static and dynamic hazard. | CO2 [K ₂] |
| 15. Justify how Yield of IC fabrication is related with testing. | CO3 [K ₄] |
| 16. Write the features of BIST in latest ICs. | CO3 [K ₂] |
| 17. What is meant by GAL? | CO4 [K ₄] |
| 18. Implement XOR gate using LUT method. | CO4 [K ₃] |
| 19. Write VHDL program for half adder using data flow modelling. | CO5 [K ₃] |
| 20. Why concurrent statements are called so? | CO5 [K ₂] |

PART C (6 x 5 = 30 Marks)

- | | |
|---|-----------------------|
| 21. Draw the reduced state diagram for the following state diagram using equivalent state method. | CO1 [K ₅] |
|---|-----------------------|

 


- | | |
|--|-----------------------|
| 22. Illustrate non-critical race condition with suitable example. | CO2 [K ₃] |
| 23. Discuss the working of BIST with suitable clock diagram. | CO3 [K ₂] |
| 24. Design and implement the following Boolean relation using PLA with neat diagram. | CO4 [K ₅] |
| 25. Design and implement full subtractor in VHDL. | CO5 [K ₅] |

26. Describe any four concurrent statements of VHDL with suitable example for each. CO5 [K₂]


Answer any FOUR Questions
PART D (4 x 10 = 40 Marks)

 27. Analyze the following synchronous sequential circuit with state table and state diagram. CO1 [K₄]



28. Design state machine for book vending machine for the following specifications. CO2 [K₆]
Cost of the book is Rs.15. Machine can accept either Rs.20 or Rs.5 currency notes. Machine dispenses one book and change Rs.5 when Rs. 20 is inserted; and dispenses book alone when three Rs.5 currency notes are inserted.

 29. Determine the test vector for the faults 2:sa0; 10:sa1; 11:sa0 in the given combinational circuit using path sensitization method. CO3 [K₅]



30. Describe the functional block diagram for CLB used in Xilinx 3000 FPGA device with neat sketch. CO4 [K₂]

31. Design and implement 8 bit UP counter in VHDL using any one type of modelling. CO5 [K₅]
