



B.E DEGREE EXAMINATIONS: APRIL / MAY 2023

(Regulation 2018)

Sixth Semester

ELECTRICAL AND ELECTRONICS ENGINEERING

U18EEI6204: Solid State Drives

COURSE OUTCOMES

- CO1:** Compare various types of loads, quadrants of operation and characteristics of motors.
CO2: Design power converter circuits for DC and AC motor drives.
CO3: Describe the speed control schemes for DC and AC motor drives.
CO4: Choose the motor drives for appropriate applications.
CO5: Simulate AC and DC drive circuits using software tool.

Time: Three Hours

Maximum Marks: 100

Answer all the Questions:-

PART A (10 x 2 = 20 Marks)

(Answer not more than 40 words)

- | | |
|--|-----------------------|
| 1. List the merits of solid-state drives. | CO4 [K ₂] |
| 2. Write the torque balance equation of electrical drive system. | CO1 [K ₂] |
| 3. State the performance parameters of AC- DC converter fed DC motor drives. | CO2 [K ₃] |
| 4. Single phase dual converter is operated for separately excited DC motor on circulating current mode. Firing angle of converter 1 is $\alpha_1 = 45^\circ$. Calculate the firing angle for converter 2. | CO2 [K ₂] |
| 5. Choose two quadrant DC- DC converters for DC motors. | CO3 [K ₃] |
| 6. The voltage of a solar PV module is 48V . A DC motor requires 60V input. For the simulation of the DC motor drive, calculate the duty ratio of the DC-DC converter to be used between solar PV module and DC motor. | CO5 [K ₃] |
| 7. Justify the need for constant V/f ratio control for induction motor drive. | CO3 [K ₂] |
| 8. State the merits of vector control of induction motor. | CO3 [K ₃] |
| 9. List the applications of PMSM drives. | CO4 [K ₂] |
| 10. Identify the simulation tools for electrical drives. | CO5 [K ₂] |

Answer any FIVE Questions:-
PART B (5 x 16 = 80 Marks)
(Answer not more than 400 words)

- | | | | | | |
|-----|----|---|---|-----|-------------------|
| 11. | a) | Illustrate the elements of electric drive system. | 8 | CO1 | [K ₂] |
| | b) | Classify the classes of motor duty with load curve, temperature curve and example. | 8 | CO1 | [K ₂] |
| 12. | a) | Draw the circuit and waveforms of three phase fully controlled converter fed separately excited DC motor for the firing angle of 60° . | 8 | CO2 | [K ₃] |
| | b) | A 220V, 20A, 1000 rpm separately excited DC motor has R_a = 0.2Ω and fed from single phase half- controlled converter with input supply of 240V rms, 50 Hz . Calculate the firing angle of the converter to operate the motor at 500 rpm and rated load torque. | 8 | CO2 | [K ₃] |
| 13. | a) | With circuit diagram, explain the operation of DC motor fed from step down chopper on time ratio control. | 8 | CO3 | [K ₂] |
| | b) | Draw the circuit and explain the quadrants of operation of class E chopper fed DC motor. | 8 | CO3 | [K ₂] |
| 14. | a) | Describe the stator voltage control method for three phase induction motor. | 8 | CO3 | [K ₂] |
| | b) | With circuit diagram, explain a slip power recovery scheme of induction motor. | 8 | CO2 | [K ₂] |
| 15. | a) | Compare VSI fed induction motor and CSI fed induction motor. | 8 | CO4 | [K ₂] |
| | b) | Describe constant V/f control of synchronous motor drive. | 8 | CO3 | [K ₂] |
| 16. | a) | Draw the block diagram of BLDC motor drive and explain the operation. | 8 | CO2 | [K ₂] |
| | b) | Explain the process and drives used for steel rolling mill. | 8 | CO4 | [K ₂] |
