



B.E. DEGREE EXAMINATIONS: APRIL / MAY 2023

(Regulation 2018A)

Fourth Semester

MECHATRONICS ENGINEERING

U18MCT4103: Digital Electronics and Microprocessor

COURSE OUTCOMES

- CO1:** Use number systems, Boolean algebra and explain various digital logic families.
CO2: Apply basic logic gates to design simple circuits and simplify logic circuits using K- Map.
CO3: Design various combinational and sequential circuits.
CO4: Explain the architecture of 8085 microprocessor.
CO5: Develop assembly language program for 8085 for the given application.
CO6: Construct interface for memory and I/O devices.

Time: Three Hours

Maximum Marks: 100

**Answer all the Questions:-
 PART A (10 x 2 = 20 Marks)
 (Answer not more than 40 words)**

- | | | |
|--|-----|-------------------|
| 1. Subtract the number 1000_B from 0011_B using 2's complement. | CO1 | [K ₃] |
| 2. Implement an AND gate using NOR gates. | CO2 | [K ₃] |
| 3. How does a carry look-ahead adder reduce propagation delay? | CO3 | [K ₂] |
| 4. Distinguish between PROM and PLA. | CO3 | [K ₂] |
| 5. Explain race-around condition in JK flipflop. | CO3 | [K ₂] |
| 6. Obtain the characteristic equation of T flipflop. | CO3 | [K ₂] |
| 7. Categorize the maskable and non-maskable interrupts in 8085. | CO4 | [K ₂] |
| 8. Write two instructions of 8085 that moves a byte from location 8000_H to accumulator using indirect addressing. | CO5 | [K ₃] |
| 9. Which control signals of 8085 are used in data transfer from peripheral (I/O) devices? | CO6 | [K ₂] |
| 10. Differentiate between synchronous and asynchronous data transfer in serial communication. | CO6 | [K ₃] |

Answer any FIVE Questions:-
PART B (5 x 16 = 80 Marks)
(Answer not more than 400 words)

11. a) Implement a 2-input NAND gate using CMOS logic and explain the working. 8 CO1 [K₂]
b) Using K-map, determine the minimal sum and minimal product for the given function: $f(x, y, z) = \sum m(2, 4, 5, 6, 7)$ 8 CO2 [K₃]
12. a) Implement a parallel adder to add two 3-bit binary numbers. 8 CO3 [K₃]
b) Realize the given function using multiplexer: $f(x, y, z) = \sum m(2, 3, 4, 5, 7)$ 8 CO3 [K₃]
13. a) Explain how edge triggering is implemented with D flipflop as example. 8 CO3 [K₂]
b) Design and implement a 3-bit binary ripple down counter using JK flipflops. 8 CO3 [K₃]
Give the schematics and state table.
14. a) Enumerate the registers present in 8085 microprocessor and explain the function of each. 8 CO4 [K₂]
b) Write an assembly language program for 8085 to add two decimal numbers 43_D and 59_D and store the result in memory. 8 CO5 [K₃]
15. a) Design an interface for the peripheral IC 8255 with the 8085 microprocessor. 10 CO6 [K₃]
Ensure that the address space is partitioned appropriately with all requisite pins connected.
b) Briefly explain the architecture and function of 8255 IC. 6 CO6 [K₂]
16. a) Implement a 4-bit ring counter with schematics and state table. 8 CO3 [K₃]
b) Explain the function of 8279 IC with a block diagram. 8 CO6 [K₂]
