



B.E. DEGREE EXAMINATIONS: APRIL / MAY 2023

(Regulation 2018)

Second Semester

COMPUTER SCIENCE AND ENGINEERING

U18CSI2202: Digital Logic and Microprocessor

COURSE OUTCOMES

- CO1:** Demonstrate how the logic gates and minimization techniques work.
CO2: Design a combinational circuit for performing arithmetic functions.
CO3: Analyze and study a few sequential circuits.
CO4: Develop programming code with 8086 for the basic problems.
CO5: Perform interfacing of 8086 with peripherals.

Time: Three Hours

Maximum Marks: 100

Answer all the Questions:-
PART A (10 x 2 = 20 Marks)
(Answer not more than 40 words)

- | | |
|--|-----------------------|
| 1. Draw a 8x1 MUX circuit. | CO1 [K ₂] |
| 2. Find the complement of the function $x'yz' + x'y'z$ by using DeMorgan's law. | CO1 [K ₂] |
| 3. How do you convert a JK-FF to a T-FF? | CO2 [K ₂] |
| 4. What is the need for clear and preset inputs? | CO2 [K ₁] |
| 5. Illustrate the circuit diagram of a MOD-10 counter. | CO3 [K ₂] |
| 6. Differentiate between combinational and sequential circuits. | CO3 [K ₂] |
| 7. When you add the two hex numbers 38 and 2F, what is the result of status flags of 8086? | CO4 [K ₂] |
| 8. What does interrupting a Microprocessor mean? What are types of Interrupts present in 8086? | CO4 [K ₁] |
| 9. Outline the use of 8251 USART. | CO5 [K ₂] |
| 10. Mention the two different operation modes of keyboards. | CO5 [K ₁] |

Answer any FIVE Questions:-
PART B (5 x 16 = 80 Marks)
(Answer not more than 400 words)

- | | | | | | |
|-----|----|--|----|-----|-------------------|
| 11. | a) | Design a Binary to gray code converter. | 8 | CO1 | [K ₂] |
| | b) | Simplify $F = \sum(2, 3, 4, 5, 7, 8, 10, 13, 15)$ using Karnaugh map and express the answer in SOP form. Implement the same using only NAND gates. | 8 | CO1 | [K ₂] |
| 12. | a) | Design a 4-bit ripple counter using T-FF. | 8 | CO2 | [K ₂] |
| | b) | Explain how you design a 4-bit Ring counter. | 8 | CO2 | [K ₂] |
| 13. | | Illustrate the working of a Successive approximation A/D converter. | 16 | CO3 | [K ₂] |
| 14. | a) | Enumerate on the different Data Transfer Instructions of 8086. | 8 | CO4 | [K ₂] |
| | b) | Illustrate the various Addressing modes of 8086. | 8 | CO4 | [K ₂] |
| 15. | a) | Summarize the Architecture of 8086 Microprocessor. | 10 | CO4 | [K ₂] |
| | b) | Write an assembly language program for calculating the factorial of a number using 8086 microprocessor. | 6 | CO4 | [K ₂] |
| 16. | | Explain the function of 8257 DMA controller. | 16 | CO5 | [K ₂] |
