



B.TECH. DEGREE EXAMINATIONS: APRIL / MAY 2023

(Regulation 2018)

Second Semester

BIOTECHNOLOGY

U18EEI2208: Basic Electrical and Electronics Engineering

COURSE OUTCOMES

CO1: Solving basic DC and AC circuits.

CO2: Select suitable DC machine for given application.

CO3: Select suitable AC machine for given application.

CO4: Characterize logic gates, semiconductor devices according to their applications.

CO5: Identify electronic components and use them to design simple circuits.

Time: Three Hours

Maximum Marks: 100

Answer all the Questions:-

PART A (10 x 2 = 20 Marks)

(Answer not more than 40 words)

- | | | |
|--|-----|-------------------|
| 1. State Kirchhoff's laws. | CO1 | [K ₂] |
| 2. Find the current through a 50Ω resistor connected to a 20V DC supply. | CO1 | [K ₂] |
| 3. Define Form Factor. | CO2 | [K ₂] |
| 4. Define RMS value. | CO2 | [K ₂] |
| 5. State the working principle of a DC Generator. | CO3 | [K ₂] |
| 6. State Fleming's Left-Hand Rule. | CO3 | [K ₂] |
| 7. Define a rectifier and write the types of rectifiers. | CO4 | [K ₂] |
| 8. Draw the symbol of Zener diode and mention its terminals. | CO4 | [K ₂] |
| 9. State De Morgan's Theorem. | CO5 | [K ₂] |
| 10. Prove that $(A + B)' A = A$. | CO5 | [K ₃] |

Answer any FIVE Questions:-

PART B (5 x 16 = 80 Marks)

(Answer not more than 400 words)

- | | | | |
|--|---|-----|-------------------|
| 11. a) Two resistors of 10Ω and 5Ω are connected in parallel. If the total current in the circuit is 20Amps. Find the current through each resistor. | 8 | CO1 | [K ₃] |
|--|---|-----|-------------------|

- b) Determine the unknown voltage V and unknown resistor R in the circuit in Figure 1 using KVL. 8 CO1 [K₃]

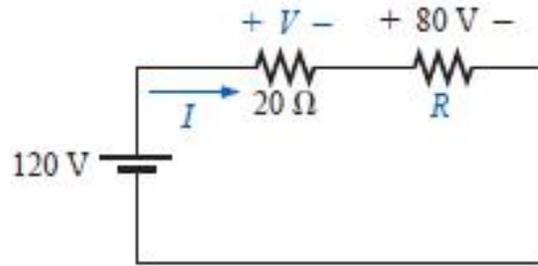


Figure 1

12. Determine the current through various resistors in the circuit given in Figure 2 using Mesh Analysis. 16 CO1 [K₃]

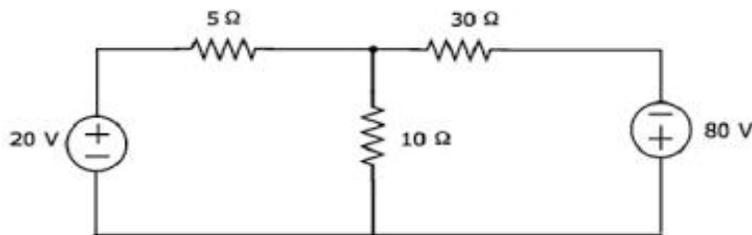


Figure 2

13. a) With a neat circuit diagram and relevant phasor diagram explain the series RLC Circuit. 10 CO2 [K₂]
 b) Derive an expression for the average value of a sinusoidal voltage. 6 CO2 [K₂]
14. a) With a neat diagram explain the construction and working of a Single-Phase Transformer. 12 CO3 [K₂]
 b) Mention the various types of DC Generators. 4 CO3 [K₂]
15. With neat circuit diagram and waveforms explain the working of full wave rectifier circuit. 16 CO4 [K₃]
16. a) Define full adder, write its truth table, derive the equations for sum and carry and draw the circuit. 10 CO5 [K₃]
 b) Determine the Decimal and Octal equivalent of binary number 11101. 6 CO5 [K₃]
